

# An introduction to RF receivers for radio astronomy

*2025 DARA February Training School*

Tinus Stander

Carl and Emily Fuchs Institute for Microelectronics

Dept. EEC Engineering, University of Pretoria

[tinus.stander@up.ac.za](mailto:tinus.stander@up.ac.za)


# Agenda

- RF Basics
- Noise & Distortion
- Components and Connections
- Important RF circuits
- Receiver architectures
- RF measurement equipment

# RF Basics
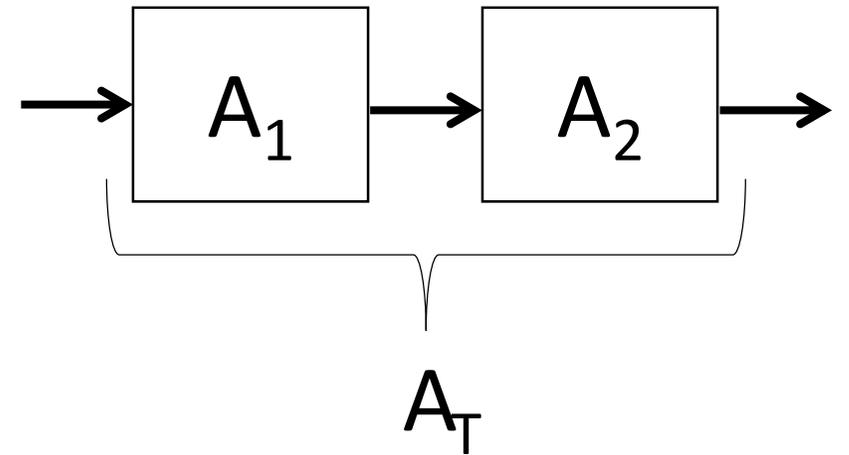
# The Decibel (dB)

- Used wherever we have a ratio
  - Usually loss or gain
- $A_T = A_1 \times A_2$
- Power:  $A_x \text{ (dB)} = 10\log(A_x)$
- Voltage / Current / S-parameters:  
 $A_x \text{ (dB)} = 20\log(A_x)$
- $A_T \text{ (dB)} = A_1 \text{ (dB)} + A_2 \text{ (dB)}$
- $A > 0 \text{ dB}$  : gain
- $A < 0 \text{ dB}$  : loss



# The S-parameter (Scattering Matrix)

- Incident and reflected voltage wave relationships
  - Frequency variant
  - Complex
- All ports terminated  $Z_0$ 
  - Characteristic impedance of system
- Important ones for  $N = 2$ :
  - $S_{21}$ : Forward transmission
  - $S_{11}$ : Input reflection
  - $S_{22}$ : Output reflection
  - $S_{12}$ : Reverse transmission
- Reciprocal:  $S_{21} = S_{12}$


$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & & & \vdots \\ S_{N1} & \cdots & & S_{NN} \\ \vdots & & & \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}$$

$$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0 \text{ for } k \neq j}$$

$$[S] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

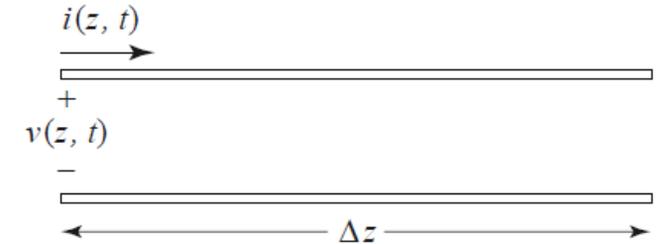
# Wires and Interconnects

- DC approximation:  $i(z=0) = i(z = z_x)$ ,  $v(z=0)=v(z=z_x)$
- Non-negligible other effects:
  - Inductance
  - Resistance
  - Stray capacitance (get to that with TX lines)
- Lumped Element approximation:  $z_x \ll \lambda/10 \rightarrow \lambda/20$






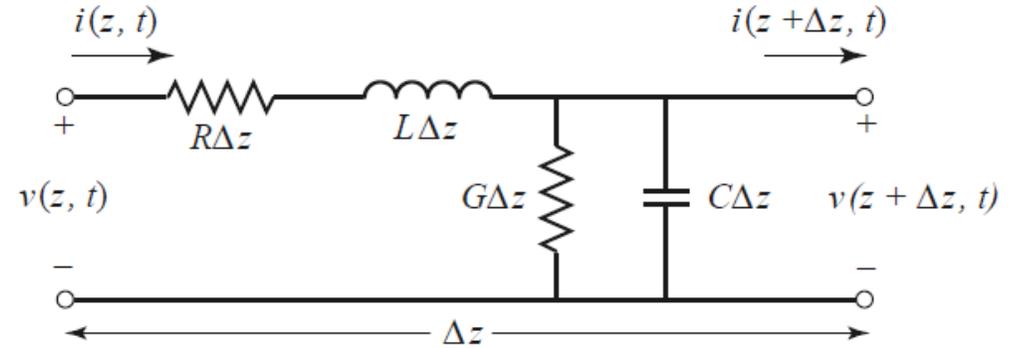
# Transmission Lines

- Wave propagating along medium
  - $v(z,t)$ ,  $i(z,t)$
  - Finite phase shift
- Medium characteristics
  - $Z_0$ ,  $\beta$ ,  $\alpha$
  - Reflection
- TEM modes
  - Nondispersive, 2+ conductors
- TE, TM modes
  - Dispersive, 1+ conductor



$$v_p = \frac{\omega}{\beta} = \lambda f, \quad Z_0 = \sqrt{\frac{L}{C}}, \quad \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}}$$
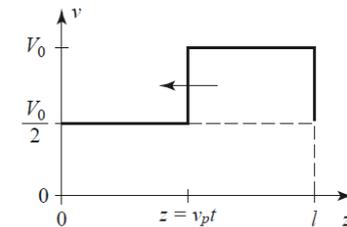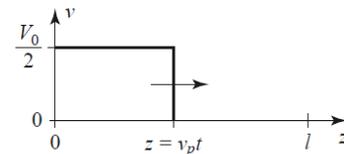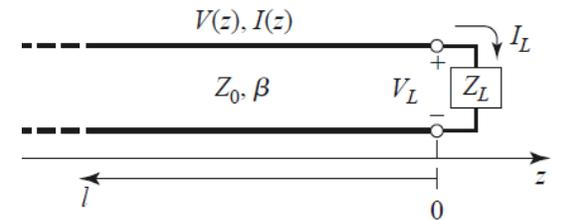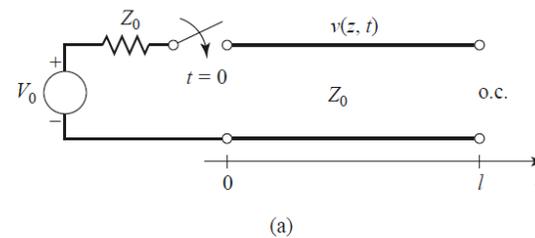
$$\alpha \simeq \frac{1}{2} \left( R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) = \frac{1}{2} \left( \frac{R}{Z_0} + GZ_0 \right)$$




# Impedance matching

- Maximum power delivery between matched source and load
- Sometimes a specific source impedance is sought
  - We'll get to that later
- In cases of mismatch: impedance matching network

$$Z_{\text{in}} = Z_0 \frac{1 + \Gamma_{\ell} e^{-2j\beta l}}{1 - \Gamma_{\ell} e^{-2j\beta l}} = Z_0 \frac{Z_{\ell} + jZ_0 \tan \beta l}{Z_0 + jZ_{\ell} \tan \beta l},$$


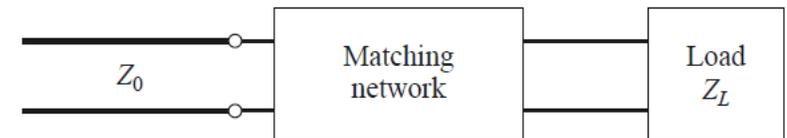
$$\Gamma_{\ell} = \frac{Z_{\ell} - Z_0}{Z_{\ell} + Z_0}.$$



Noise

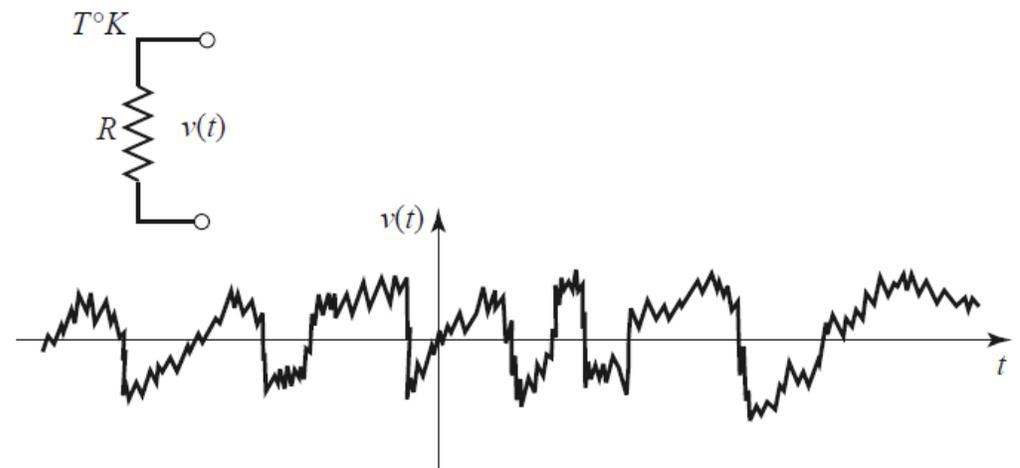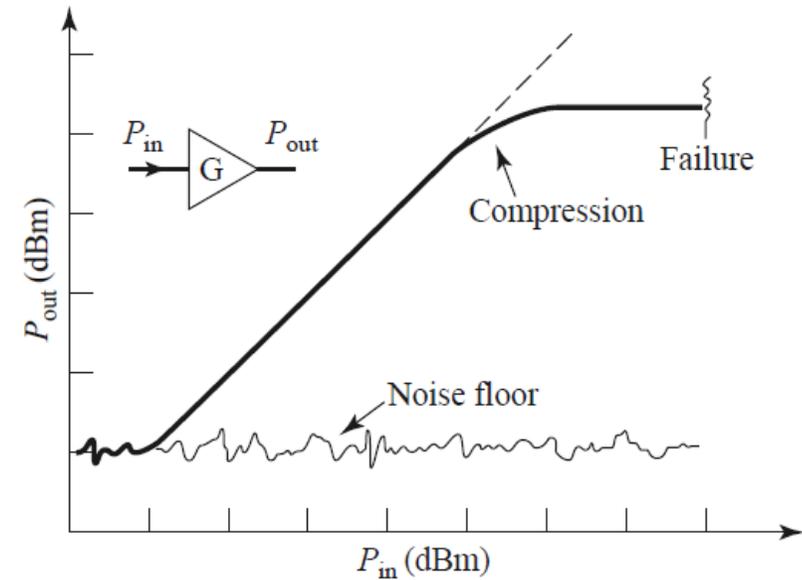
# General principles (1)

- Random variation
  - Internal: charge carriers
    - Thermal noise (Johnson / Nyquist)
    - Shot noise
    - Flicker (1/f) noise
  - External: physical phenomenon
    - Thermal emissions, cosmic background
    - Sources = interferers, not noise
  - Flat spectrum = “white noise”
    - Zero average, nonzero RMS
- Limits dynamic range
  - Other end: compression / distortion



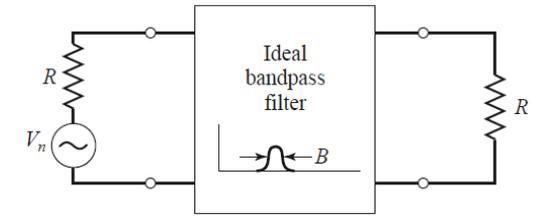
# General principles (2)



- Link between noise and temperature
- Planck blackbody
  - Rayleigh-Jeans approx. okay, except
    - $f > 1 \text{ THz}$ ,  $K \ll 300\text{K}$
- Equivalent noise temperature
- Used for noise-generating components
- Used for antennas



$$V_n = \sqrt{4kTBR}.$$

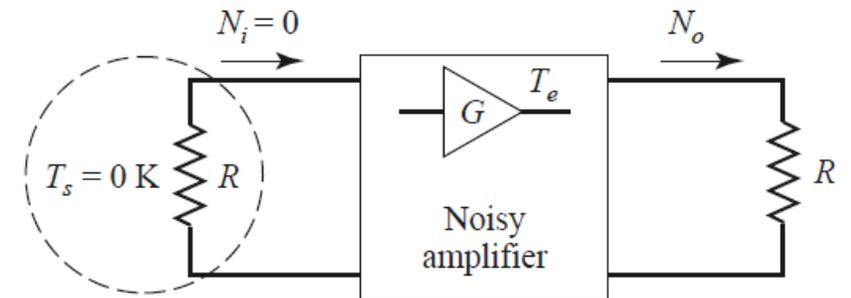


(a)

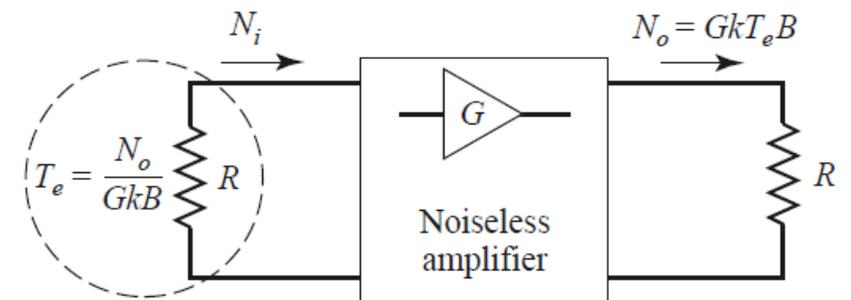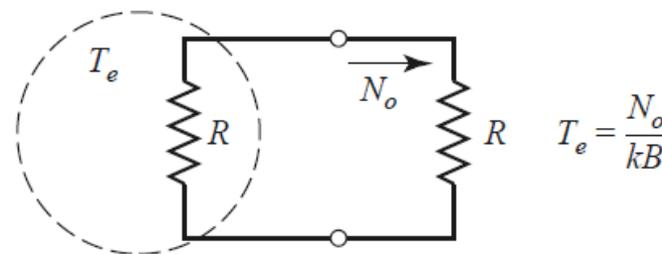

(b)
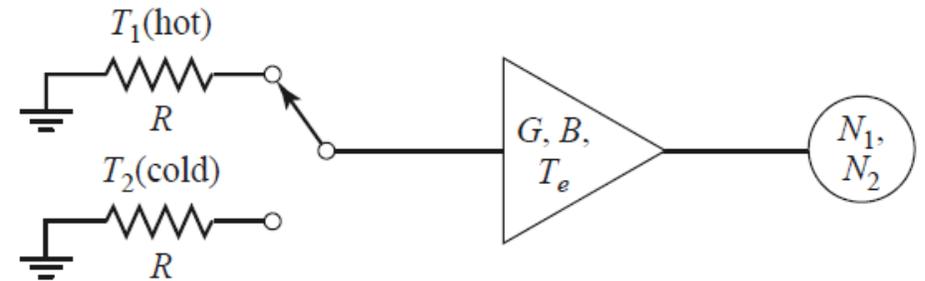
# Noise Measurement

- Y-factor method
- Switch between “hot” and “cold” loads
- Need  $Y \gg 1$ 
  - $T_1 \gg T_2$
  - $T_1, T_2 \gg T_e$
- Re-write i.t.o. ENR:  $T_1/T_2$ 
  - ENR tables provided in noise sources




$$N_1 = GkT_1B + GkT_eB, \quad Y = \frac{N_1}{N_2} = \frac{T_1 + T_e}{T_2 + T_e} > 1,$$
$$N_2 = GkT_2B + GkT_eB,$$

$$T_e = \frac{T_1 - YT_2}{Y - 1},$$
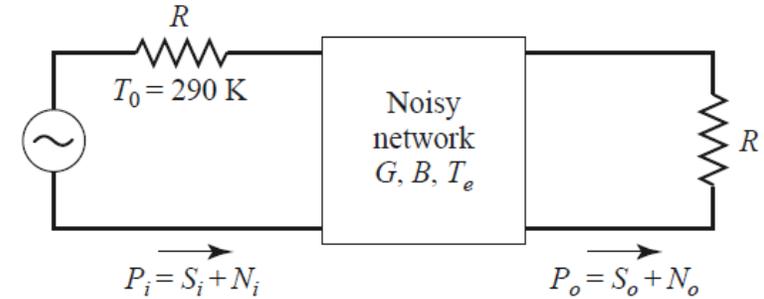
# Noise Figure


- Measure of  $\text{SNR}_i/\text{SNR}_o, > 1$
- Nomenclature:
  - F = Noise Factor, linear
  - NF = Noise Figure, dB
- Defined for:
  - Matched load input
  - Reference  $T_0$ 
    - Else: stick to  $T_e$
    - Or:  $T_A$ , for antenna front-end.
- Passive, lossy components:
  - $\text{IL} = F$
  - Can apply to mismatch too: gain lower



$$F = \frac{S_i/N_i}{S_o/N_o} \geq 1,$$


$$F = \frac{S_i}{kT_0B} \frac{kGB(T_0 + T_e)}{GS_i} = 1 + \frac{T_e}{T_0} \geq 1.$$

$$T_e = (F - 1)T_0.$$

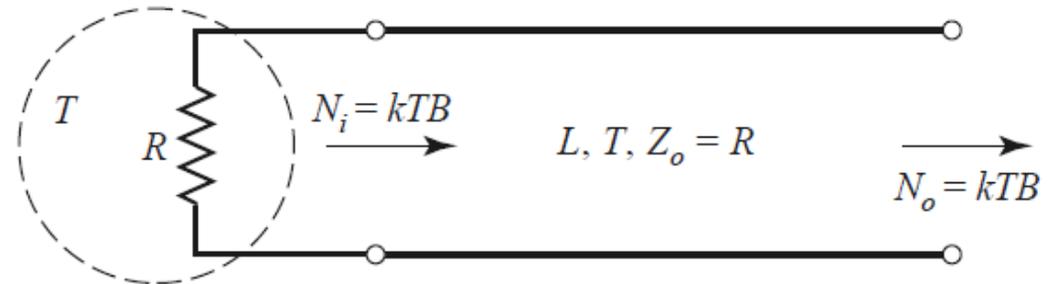
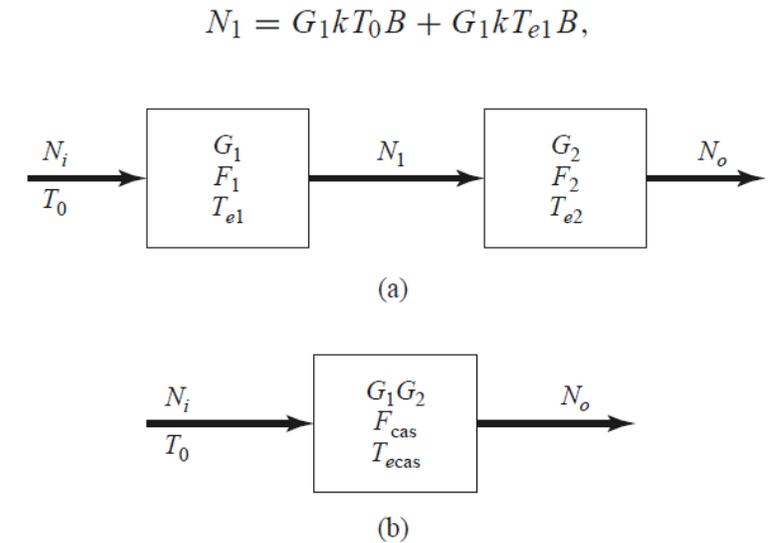
# NF in Cascaded Systems

- Amplifiers amplify gain AND noise!
  - $\text{SNR}_i/\text{SNR}_o$  increases down the chain
  - F increases
- Subsequent noise contribution mitigated by prior gain stages...
- First stage NF dominant in system!
  - Want  $T_A$  low as well.
- Use T, not NF, to avoid  $T \neq T_0$



$$N_o = G_2 N_1 + G_2 k T_{e2} B$$


$$= G_1 G_2 k B \left( T_0 + T_{e1} + \frac{1}{G_1} T_{e2} \right).$$

$$T_{\text{cas}} = T_{e1} + \frac{T_{e2}}{G_1} + \frac{T_{e3}}{G_1 G_2} + \dots,$$

$$F_{\text{cas}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots.$$

# NF of mismatched amplifiers

- F increases with mismatch

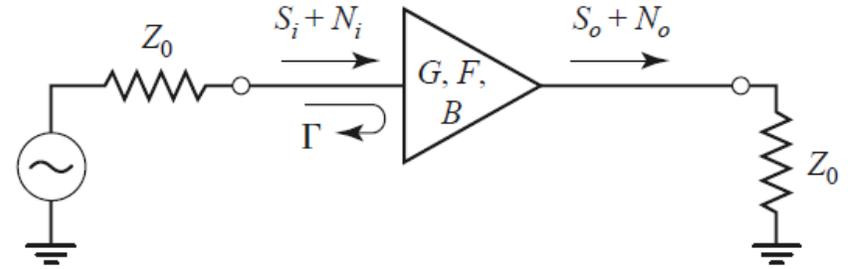


$$N_o = kT_0 GB (1 - |\Gamma|^2) + kT_0 (F - 1) GB$$



$$F_m = \frac{S_i N_o}{S_o N_i} = 1 + \frac{F - 1}{1 - |\Gamma|^2}.$$
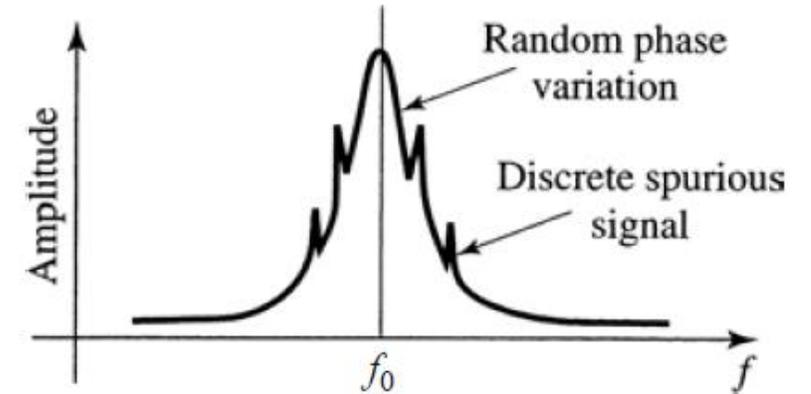
# Phase noise

- Random variation of tone  $f_0$ 
  - Frequency or phase variation
  - Increase noise power
  - Error in downconversion
- Expressed in dBc/Hz @ offset  $f_m$
- Spectrum described by Leeson's model
  - For oscillators with resonators of Q.
    - High Q reduces L
- $f_\alpha$  corner frequency of  $1/f$ 
  - Transistor dependent
- Far out: amplifier NF



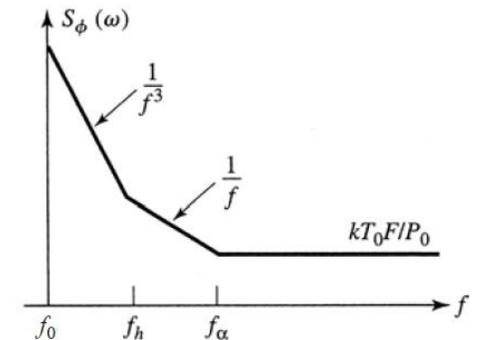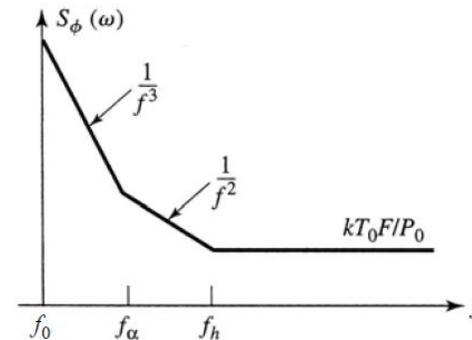
$$S_\phi(\omega) = \frac{kT_0 F}{P_0} \left( \frac{K \omega_0^2 \omega_\alpha}{4Q_0^2 \Delta\omega^3} + \frac{\omega_0^2}{4Q_0^2 \Delta\omega^2} + \frac{K \omega_\alpha}{\Delta\omega} + 1 \right)$$


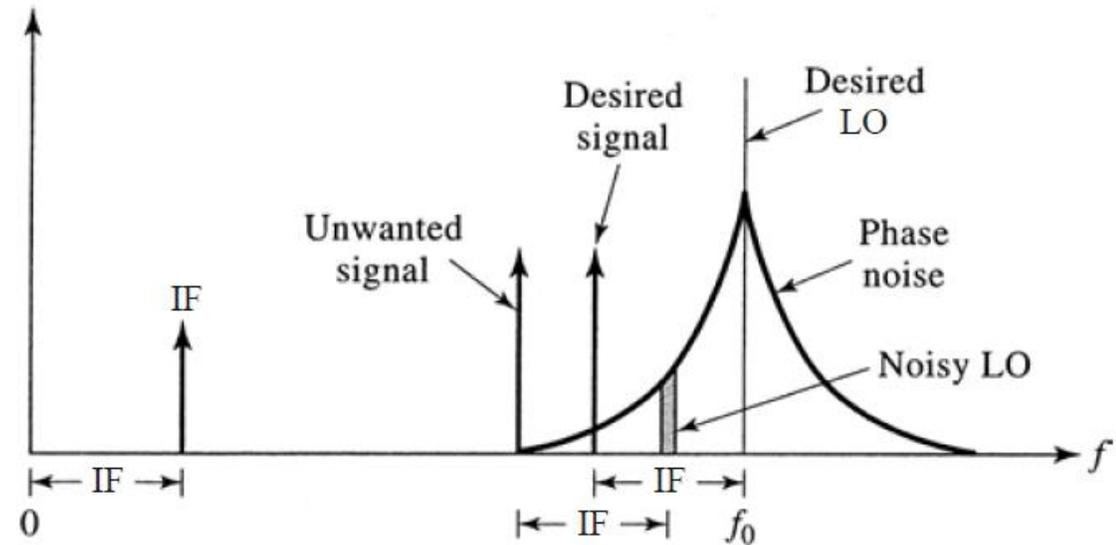
# Phase noise (2)

- Downconversion error
- Maximum interferer tolerable -> choice of L spec.



$$\mathcal{L}(f_m) = C \text{ (dBm)} - S \text{ (dB)} - I \text{ (dBm)} - 10 \log(B), \text{ (dBc/Hz)},$$

Distortion

# Nonlinear effects & distortion

- Harmonic generation
- Saturation (gain reduction, AM-AM distortion)
- Intermodulation (two tones mix)
- AM-PM conversion (amplitude  $\rightarrow$  phase shift)
- N order of terms
  - DC, linear, quadratic, etc.





$$v_o = a_0 + a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots,$$

$$\begin{aligned} v_o &= a_0 + a_1 V_0 \cos \omega_0 t + a_2 V_0^2 \cos^2 \omega_0 t + a_3 V_0^3 \cos^3 \omega_0 t + \dots \\ &= \left( a_0 + \frac{1}{2} a_2 V_0^2 \right) + \left( a_1 V_0 + \frac{3}{4} a_3 V_0^3 \right) \cos \omega_0 t + \frac{1}{2} a_2 V_0^2 \cos 2\omega_0 t \\ &\quad + \frac{1}{4} a_3 V_0^3 \cos 3\omega_0 t + \dots \end{aligned}$$

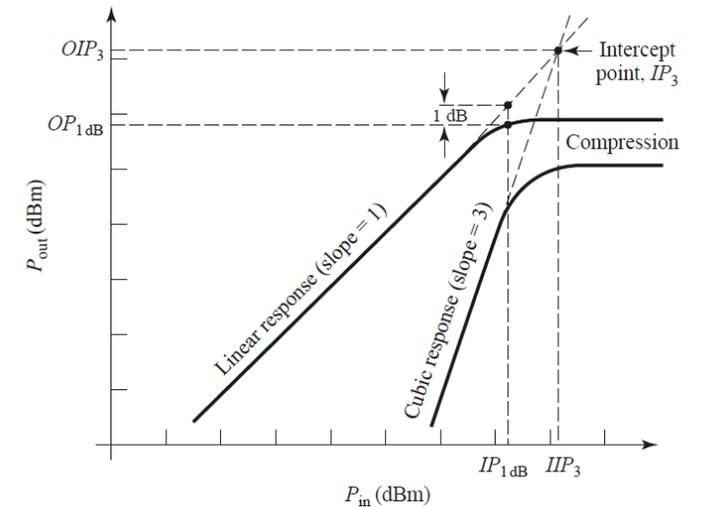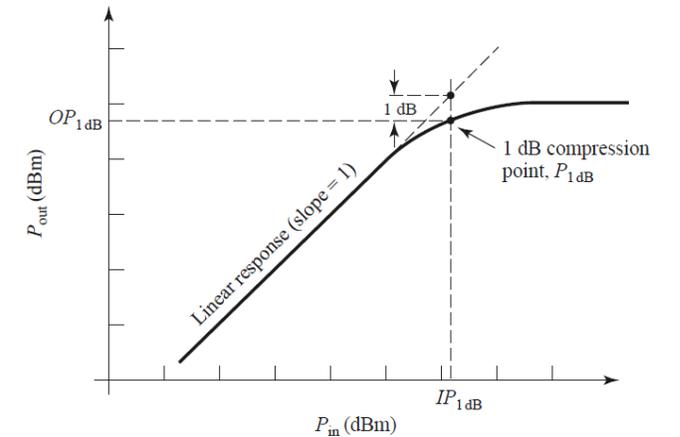
# Different kinds of distortion

- Gain compression (P1db)
  - Lower than expected output
- Third order intercept (IIP3/OIP3)
  - Mixing term of two-tone input
- Passive intermodulation (PIM)
  - Parasitic diodes from oxidation on metal
  - Only a consideration at high power


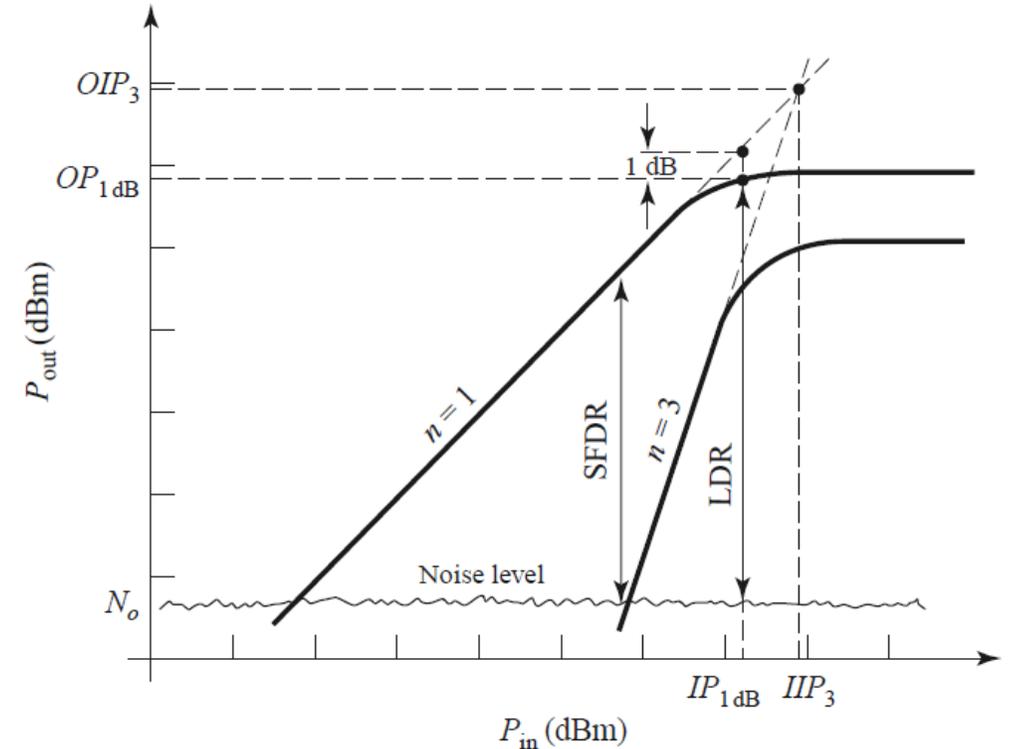
# Dynamic Ranges

- Power range over which performance is desirable
- Limited by which undesired effect we want to avoid!
- Linear dynamic range (LDR)
  - Range over which operation is “linear”
  - Noise floor  $\rightarrow$   $P_{1dB}$
- Spurious free dynamic range (SFDR)
  - Range over which spurs below noise floor
    - Typ. 3<sup>rd</sup> order ( $2f_2-f_1$ ,  $2f_1-f_2$ )
  - SFDR typ.  $\ll$  LDR








# Sensitivity

- Definition specific to receiver
- Smallest detectable signal
- Sensitivity (dBm) for comms =  $-174 + NF + 10\log B + SNR$
- For antenna temperature NOT 290K
  - More generally:  $S_i(\min) = kB(T_A + (F-1)T_0)SNR_{\min}$

# Components and Connections



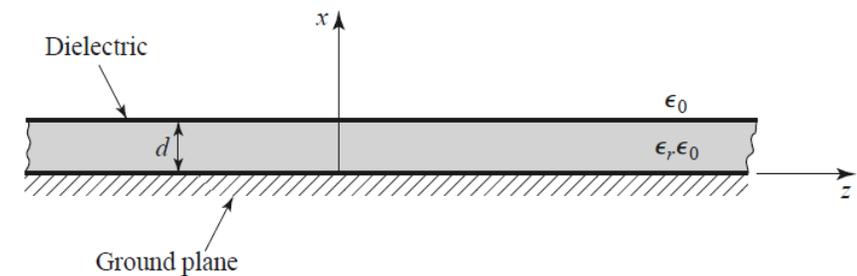
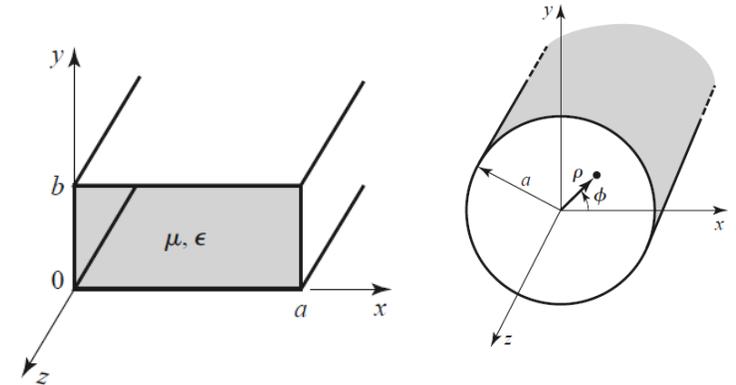
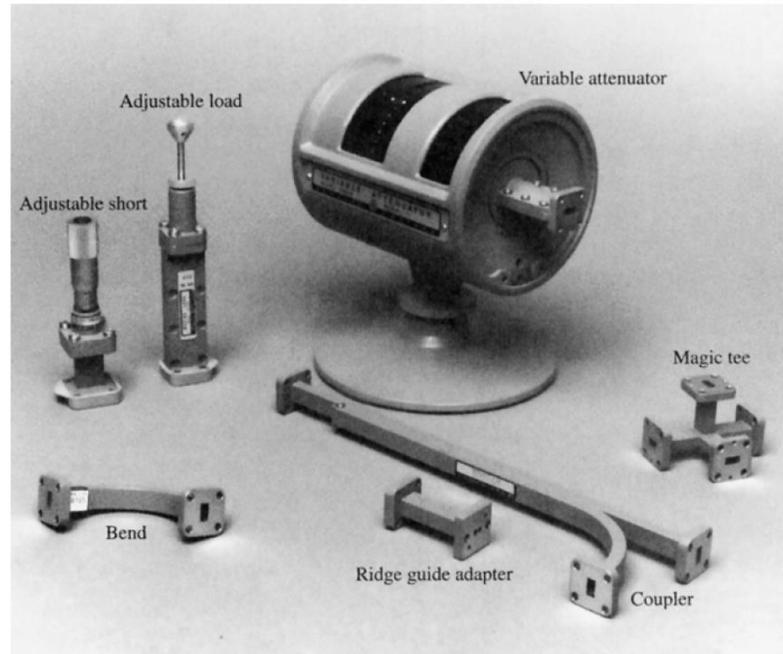
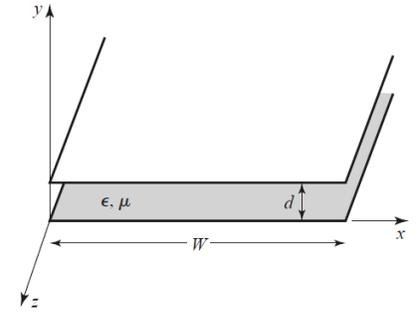
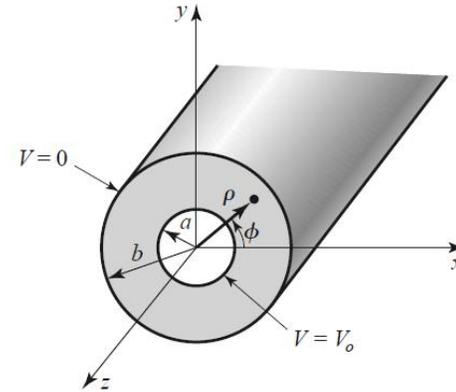
# Transmission media (1)

- Waveguide
  - Coax
    - Modes!
  - Parallel Plate
    - Parasitic!
  - Surface Waves
    - Parasitic!
  - Rectangular, Circular



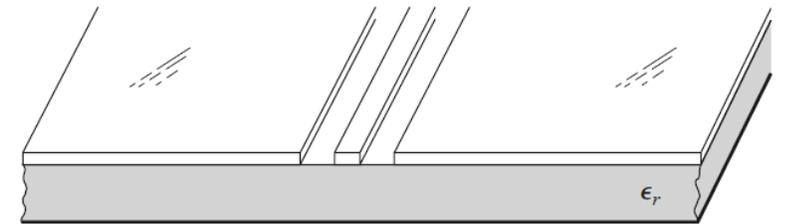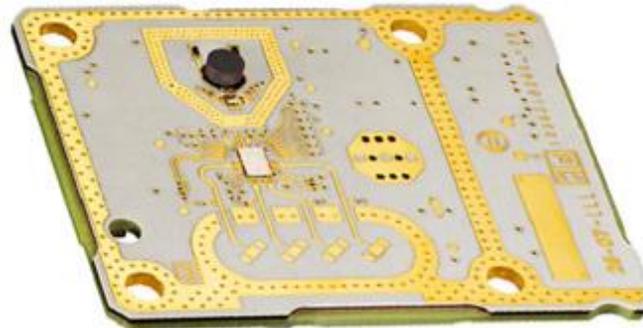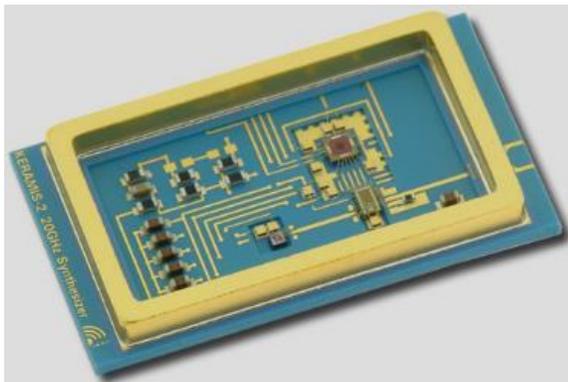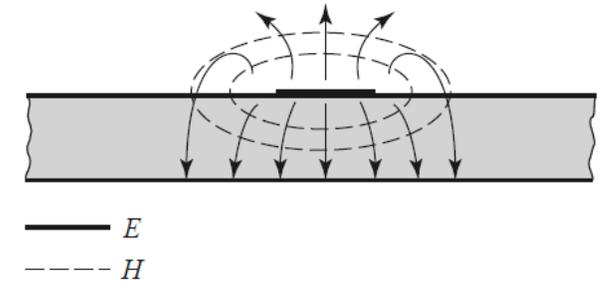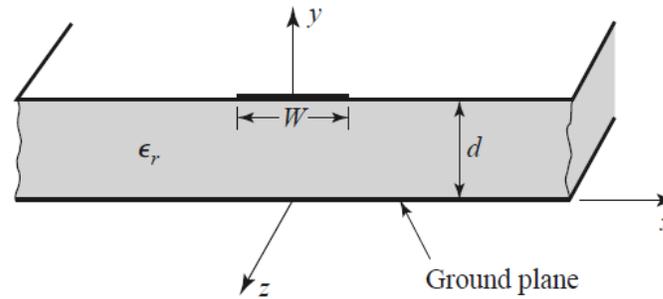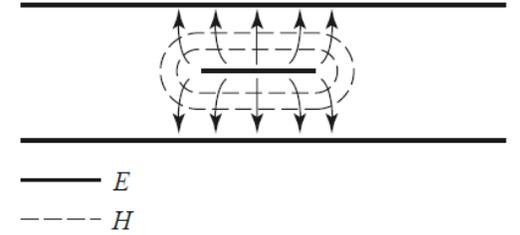
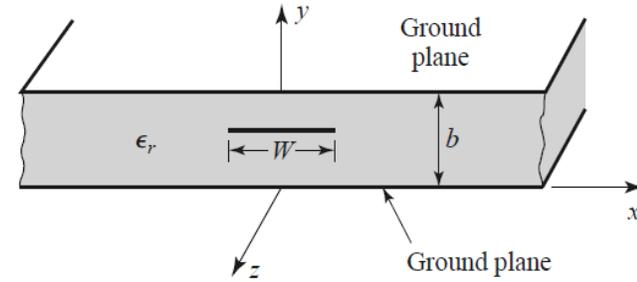
# Transmission media (2)

- Planar
  - Stripline
  - Microstrip
  - CPW, GCPW
  - And others...
- Integrate with SMD components






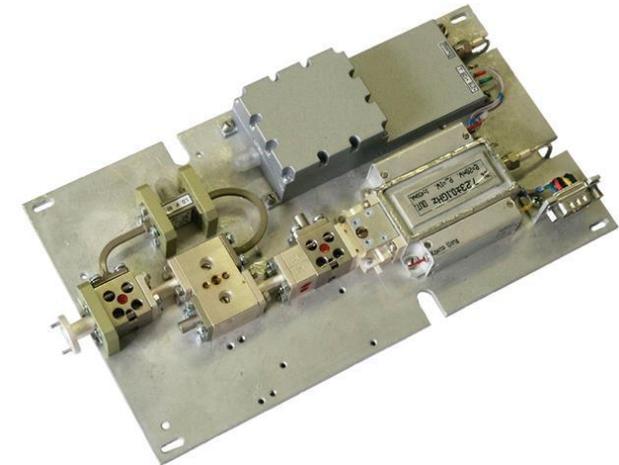
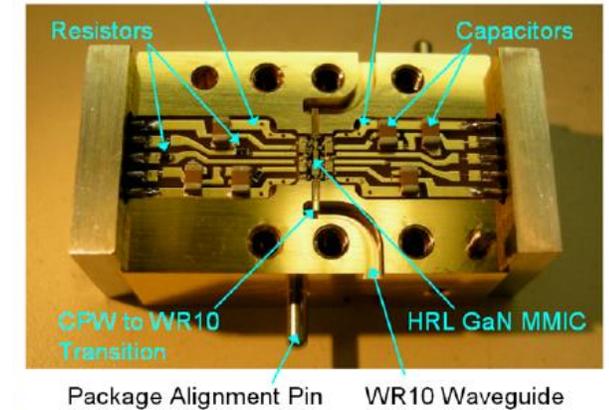
# Non-planar system integration

- Waveguide
  - Split block / finline
  - WR standards
- Microwave coax connectors
  - Different standards for different frequencies
    - SMA most common
- Mixed modules
  - WG RF, coax IF
- Cables
  - Limited by overmoding, connectors







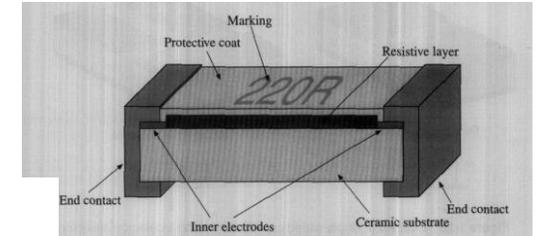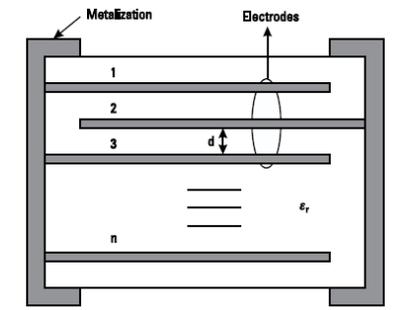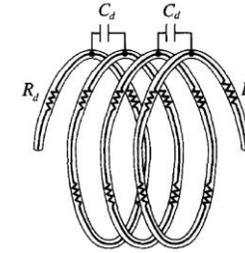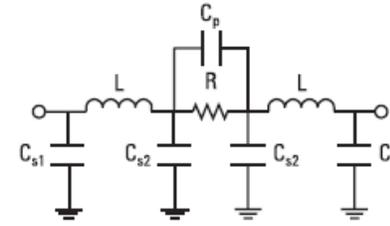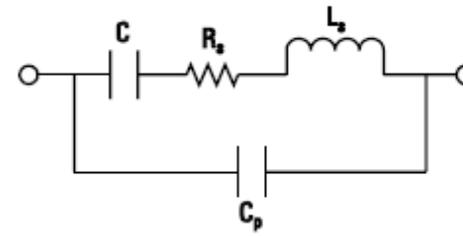
# Passive components

- Resistors, capacitors, inductors
  - Complex responses



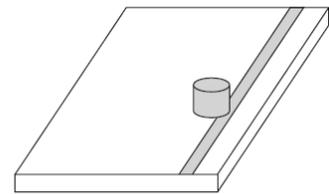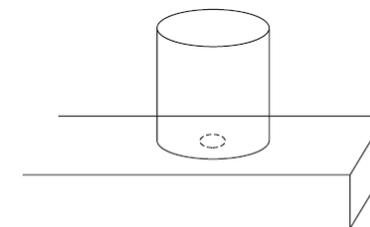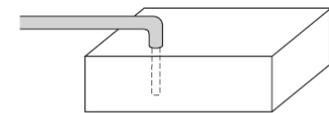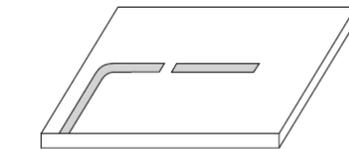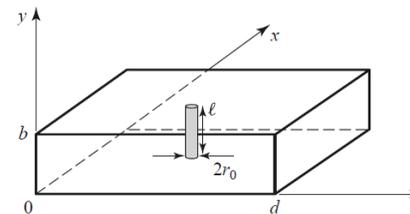- Resonators
  - Used for e.g. filters, oscillators
  - Temporary storage of energy at a specific frequency



(a)






(b)

(c)

(d)

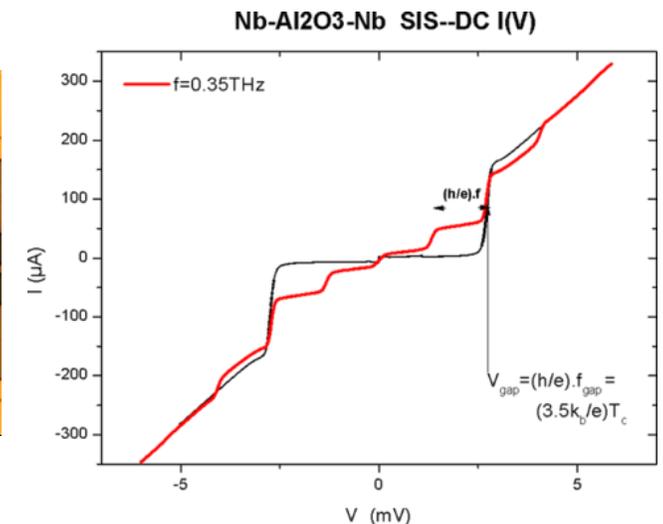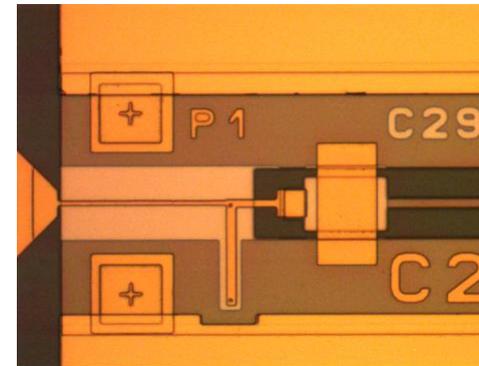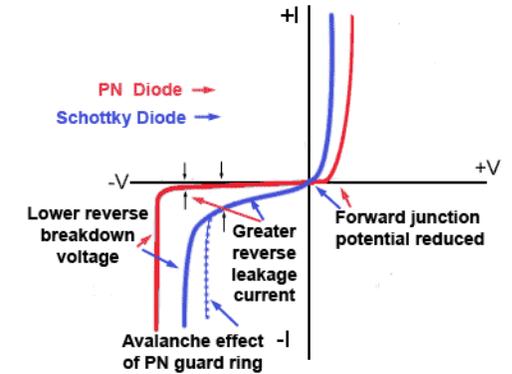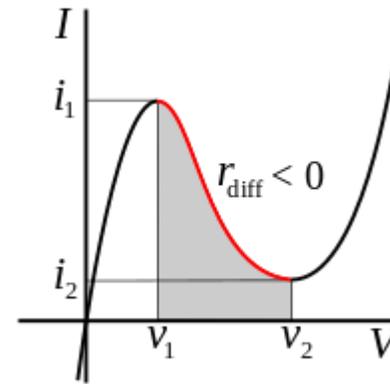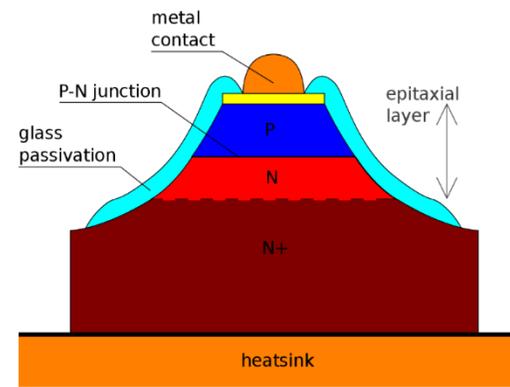
# Diodes

- PN: low frequency
  - Varactor: Vary C with DC (depletion layer)
- PIN
  - DC biasing -> very linear R at RF
  - Switches, variable attenuators
- Schottky
  - Metal-semi contact
  - Fast switching; no recovery time
  - Detectors
- Tunnel Diode
  - Negative I-V region
    - Quantum well
  - Detectors, switches
- SIS mixers
  - Photon-assisted tunnelling, superconducting T's
  - Used for detecting sub-THz and THz frequencies




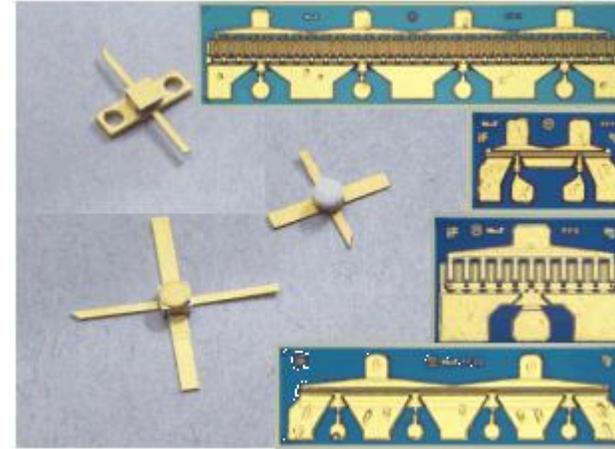
# Transistors

- Different semiconductors
  - Si: Cheap, moderate performance
  - SiGe: More expensive, faster III-V
    - GaAs: Common in Radio Astronomy
    - InP: The best, most expensive choice
- Types
  - Bipolar: BJT / HBT
  - MOSFET, MESFET
  - HEMT





|              | IIIA                  | IVA                   | VA                     | VIA                   | VIIA            |                |
|--------------|-----------------------|-----------------------|------------------------|-----------------------|-----------------|----------------|
| III-V        | <b>B</b><br>Boron     | C<br>Carbon           | <b>N</b><br>Nitrogen   | O<br>Oxygen           | F<br>Fluorine   |                |
|              | <b>Al</b><br>Aluminum | Si<br>Silicon         | <b>P</b><br>Phosphorus | S<br>Sulphur          | Cl<br>Chlorine  |                |
| IB           | IIB                   | <b>Ga</b><br>Gallium  | Ge<br>Germanium        | <b>As</b><br>Arsenic  | Se<br>Selenium  | Br<br>Bromine  |
| Cu<br>Copper | Zn<br>Zinc            | <b>In</b><br>Indium   | Sn<br>Tin              | <b>Sb</b><br>Antimony | Te<br>Tellurium | I<br>Iodine    |
| Ag<br>Silver | Cd<br>Cadmium         | <b>Tl</b><br>Thallium | Pb<br>Lead             | <b>Bi</b><br>Bismuth  | Po<br>Polonium  | At<br>Astatine |
| Au<br>Gold   | Hg<br>Mercury         |                       |                        |                       |                 |                |

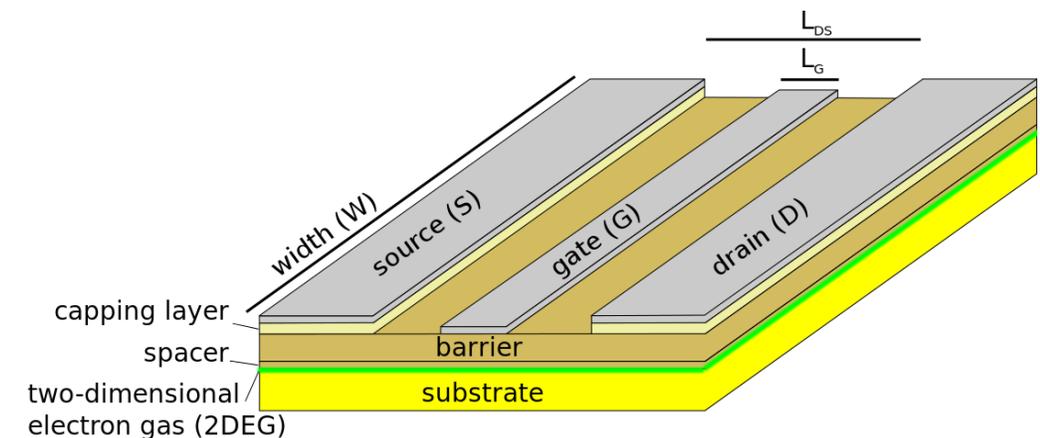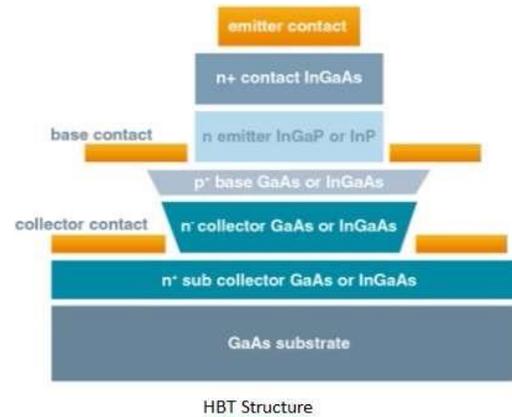

Important RF circuits
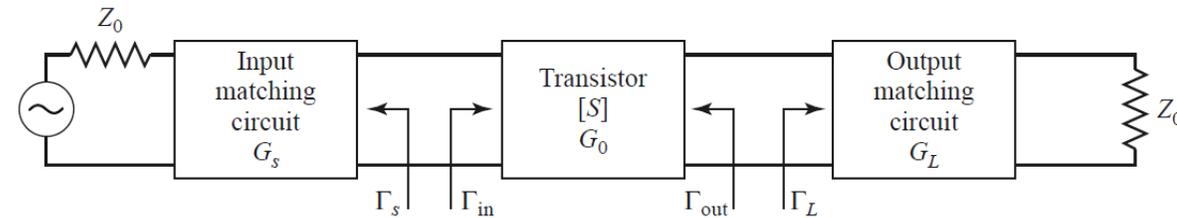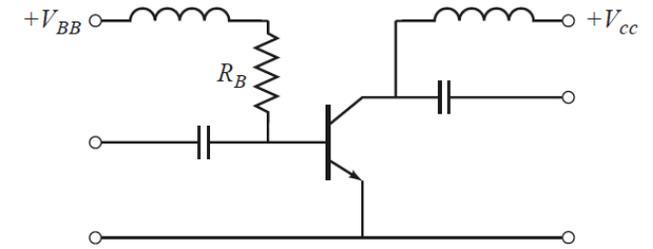
# Low noise amplifiers

- Transistor, biasing, matching
- Match for
  - Gain
    - Complex conjugate power match
  - Noise
    - $NF_{\min}$ ,  $R_N$ ,  $\Gamma_{\text{opt}}$  in datasheet
  - Stability
  - ... It's a trade-off.
- Usually multiple stages




$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2},$$

$$G_0 = |S_{21}|^2,$$


$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}.$$

$$N = \frac{|\Gamma_S - \Gamma_{\text{opt}}|^2}{1 - |\Gamma_S|^2} = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{\text{opt}}|^2$$

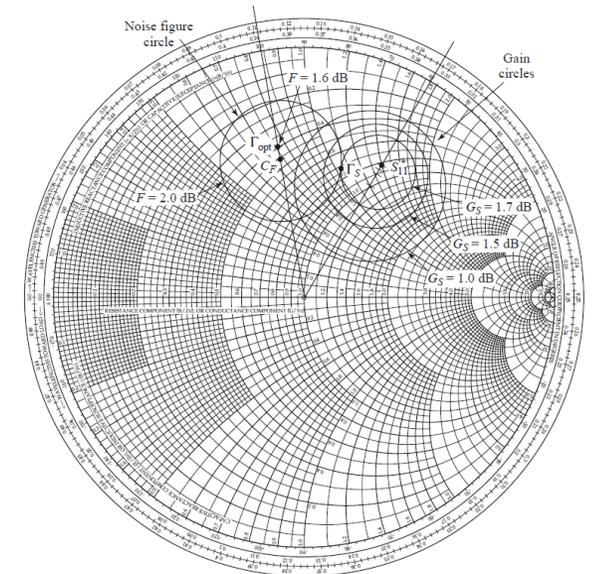

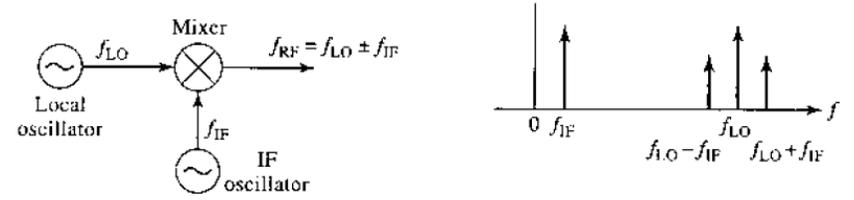
# Mixers




- 3-port device for frequency translation
- Image frequencies!
- Diode circuits
- Transistor circuits
  - Gilbert cell
- Harmonic versions



(a)



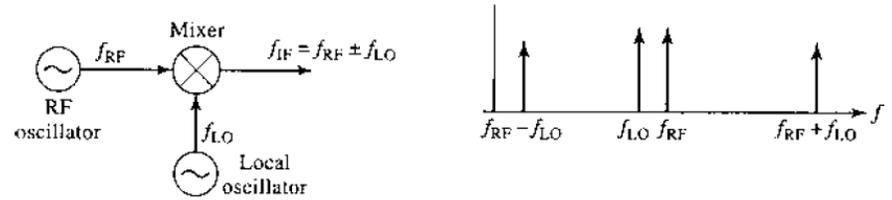


(b)

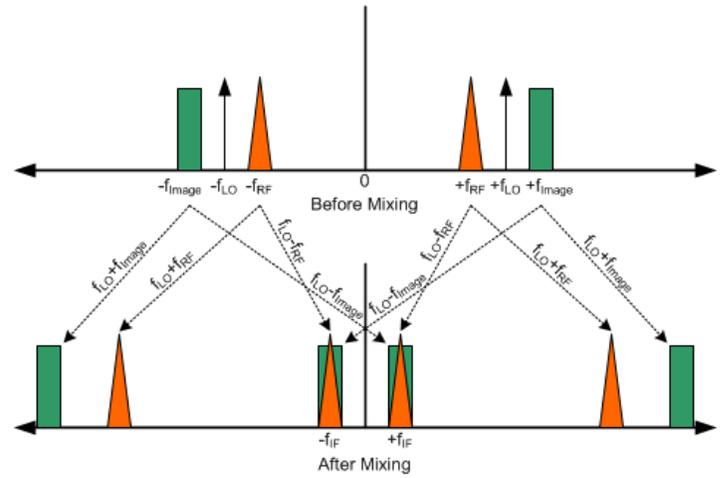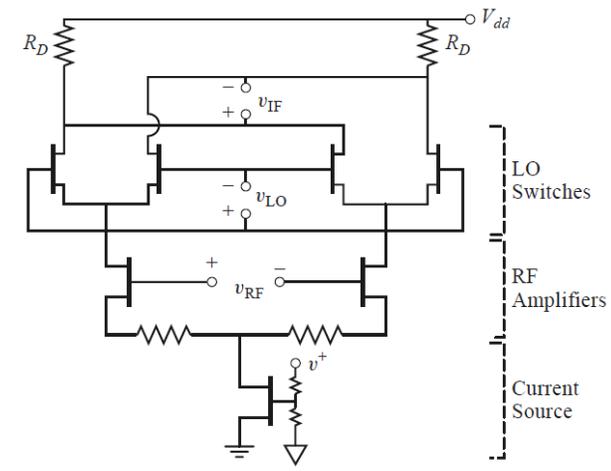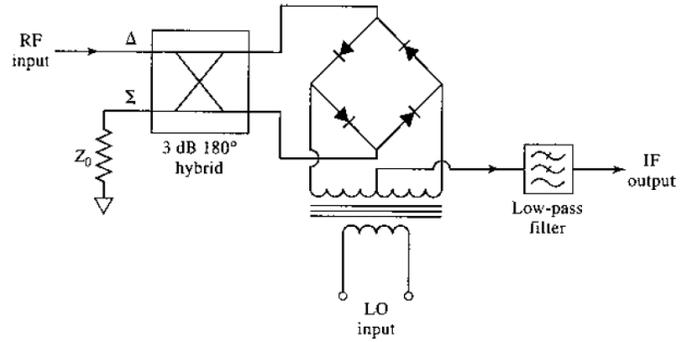


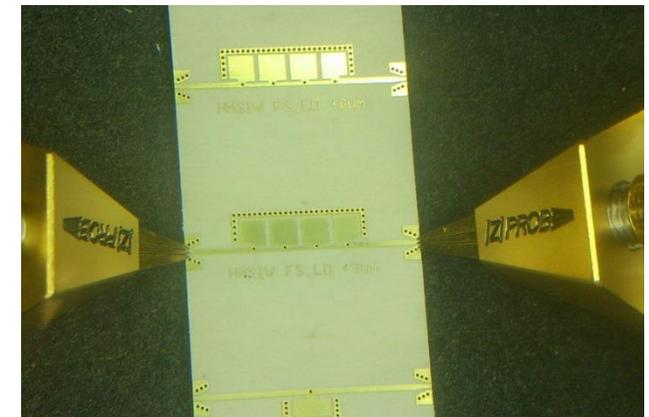
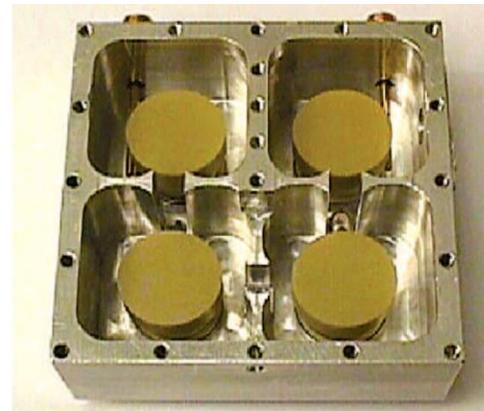
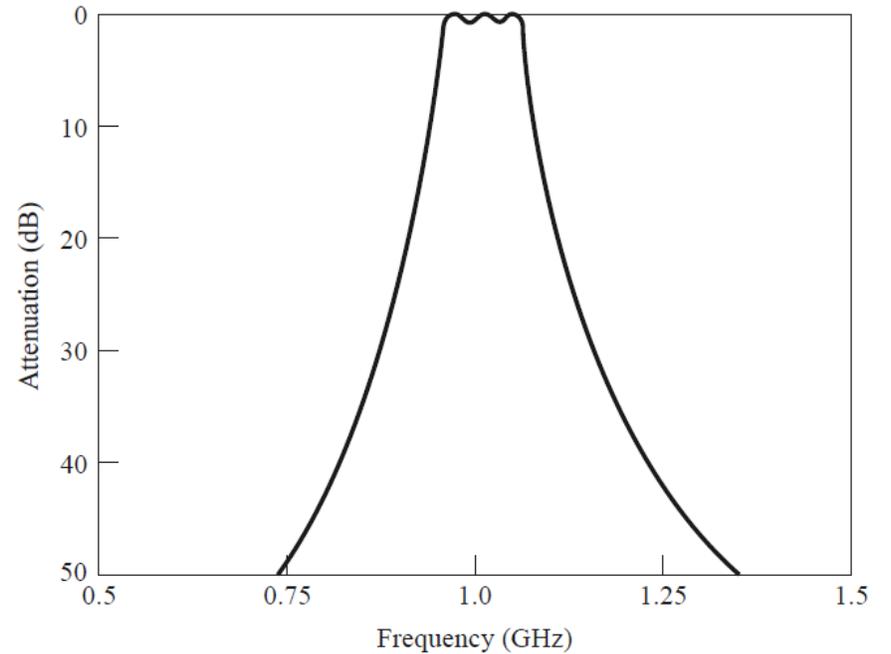
# Filters

- Low-pass, high-pass, band-pass, band-stop
- Frequency selective transmission
- Limits received noise band
- Suppresses mixing products
- Reject interferers
- More elements:
  - More selective
  - More loss



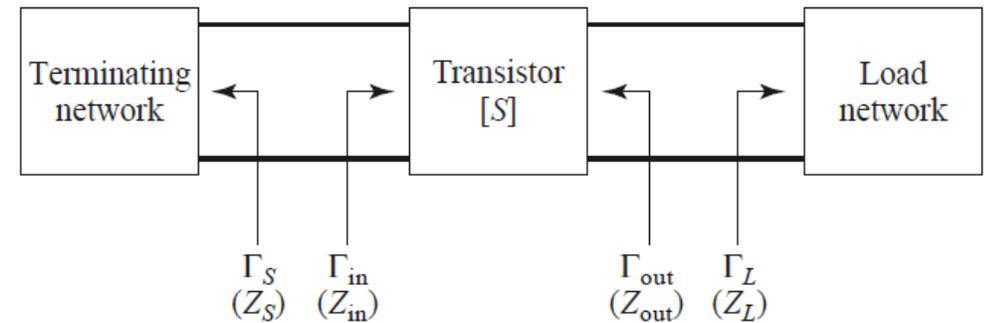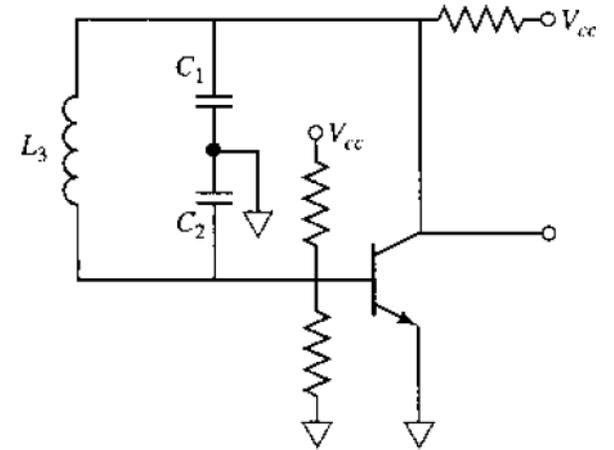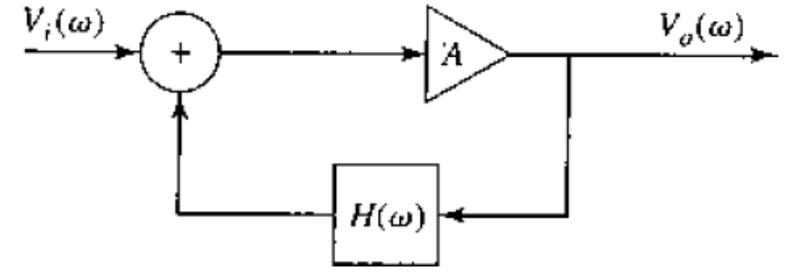
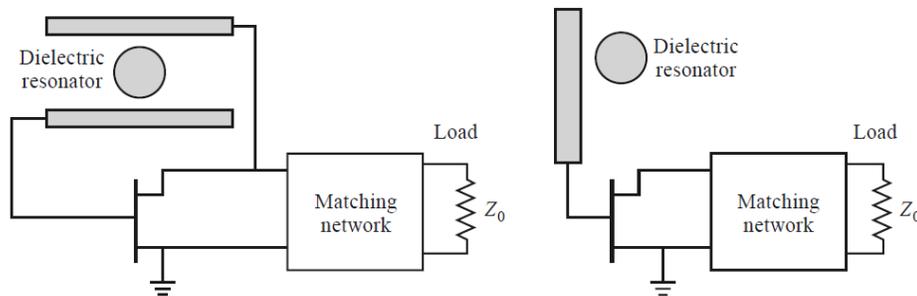
# Oscillators

- Generate a steady sinusoid
- Characterized by
  - Power
  - Phase noise
  - Tunability
- Gain + a stable feedback
  - Can use a stable reflection as well









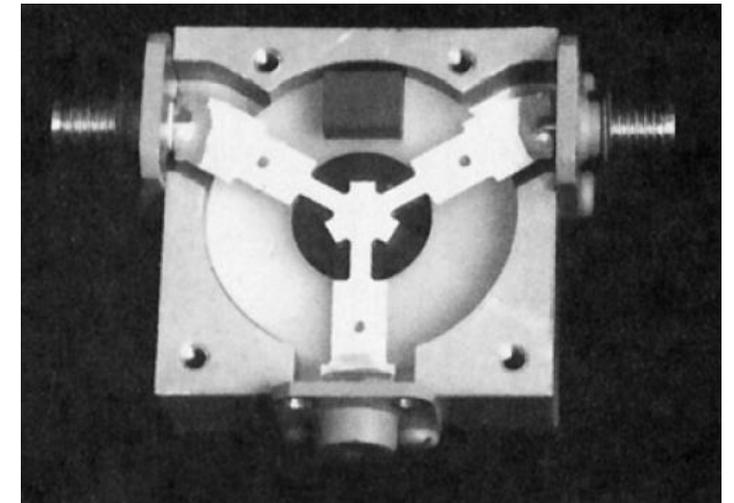
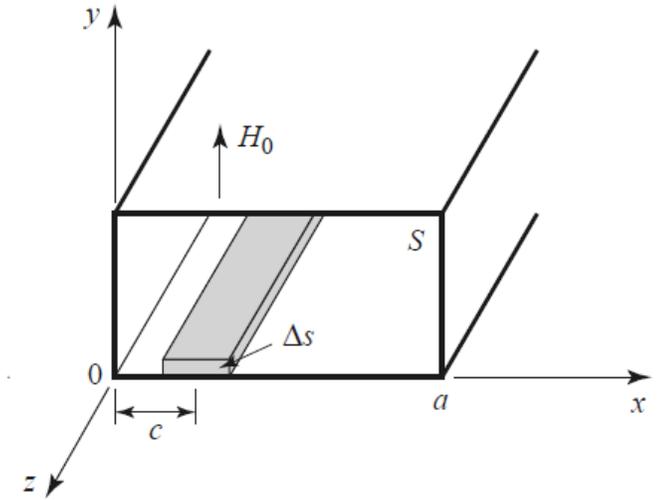
# Isolators

- RF transmission in one direction, but not the other
  - $S_{21} \approx 0$  dB,  $S_{12} < -40$  dB
  - Usually ferromagnetic
- Used to
  - Control noise and leakage propagation
    - Eg. LO reflection from antenna
  - Improve impedance matching
- Three-port: Circulator
  - Signal Merry-go-round



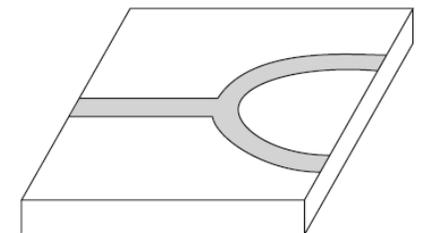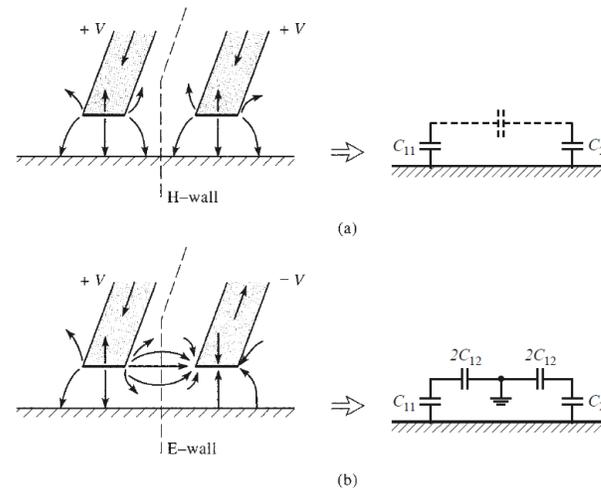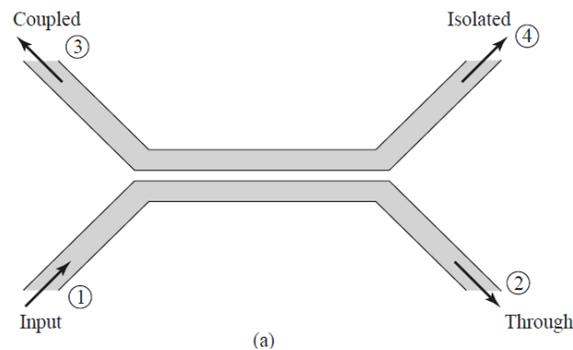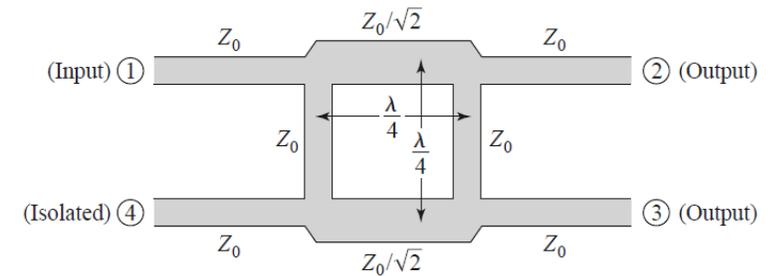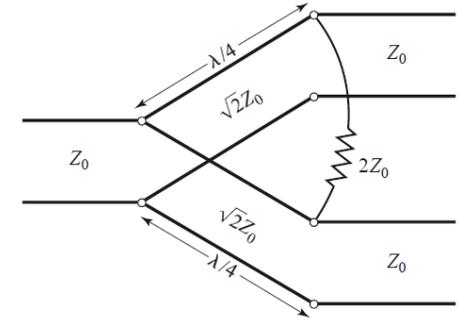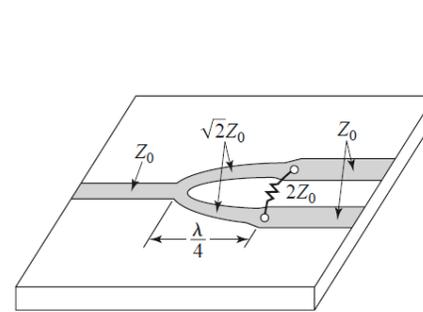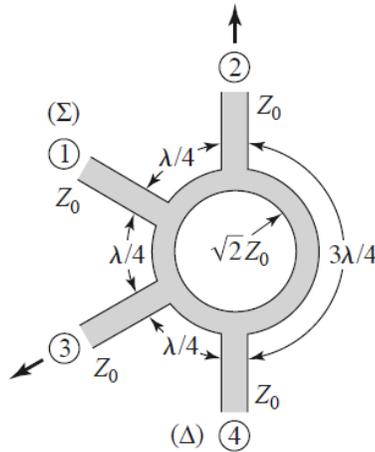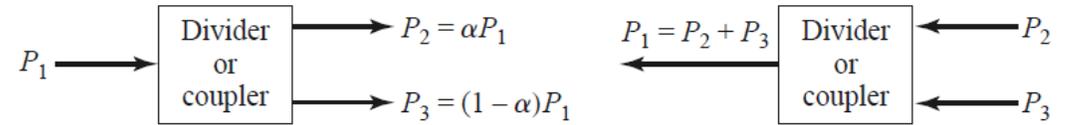
# Couplers

- Split energy from source to outputs
- T-junction
  - 3-port
  - Wilkinson
- Quadrature Hybrid
- Directional
  - 4-port
- Rat Race



# Receiver Architectures



# Common components

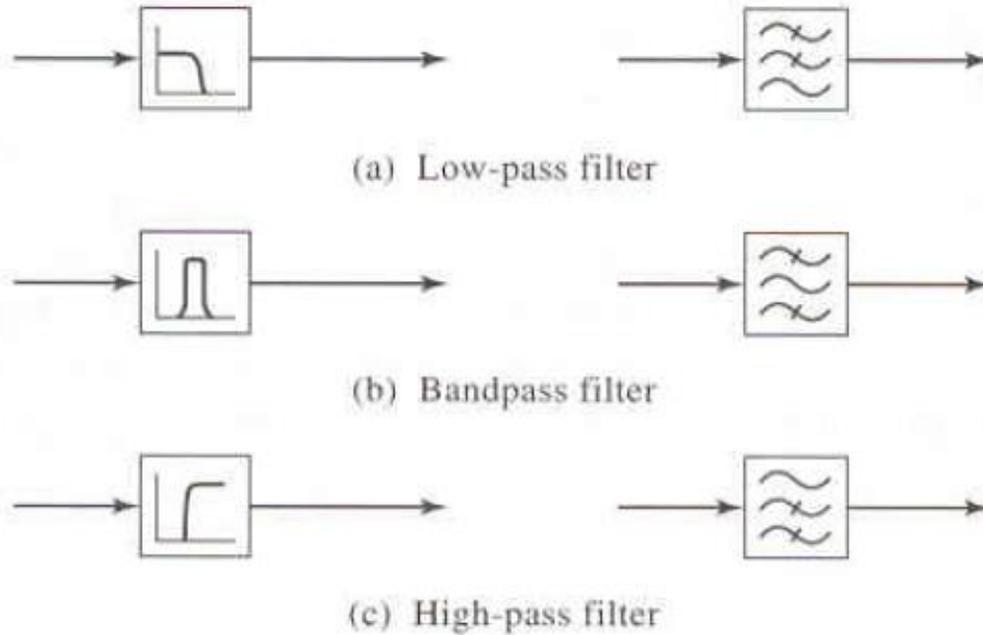

| Component Symbol | Component Name       |
|------------------|----------------------|
|                  | Antenna              |
|                  | Amplifier            |
|                  | Mixer                |
|                  | Oscillator           |
|                  | 90° power divider    |
|                  | Frequency multiplier |
|                  | Frequency divider    |
|                  | Switch               |

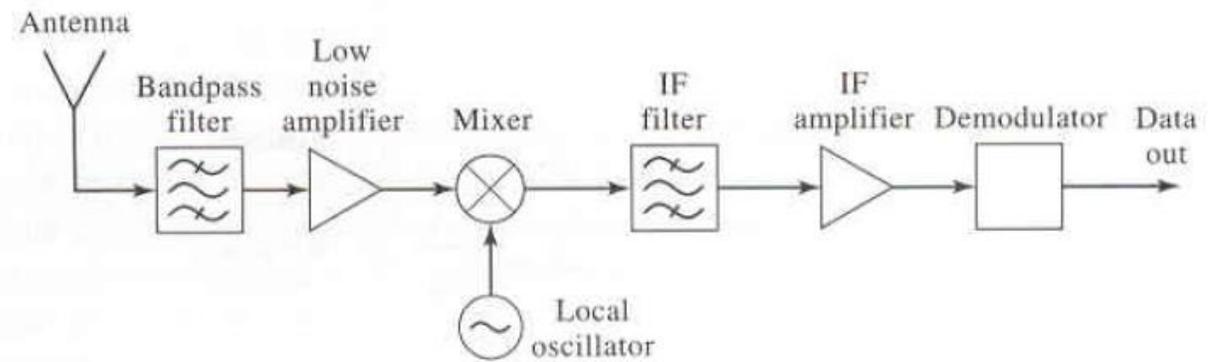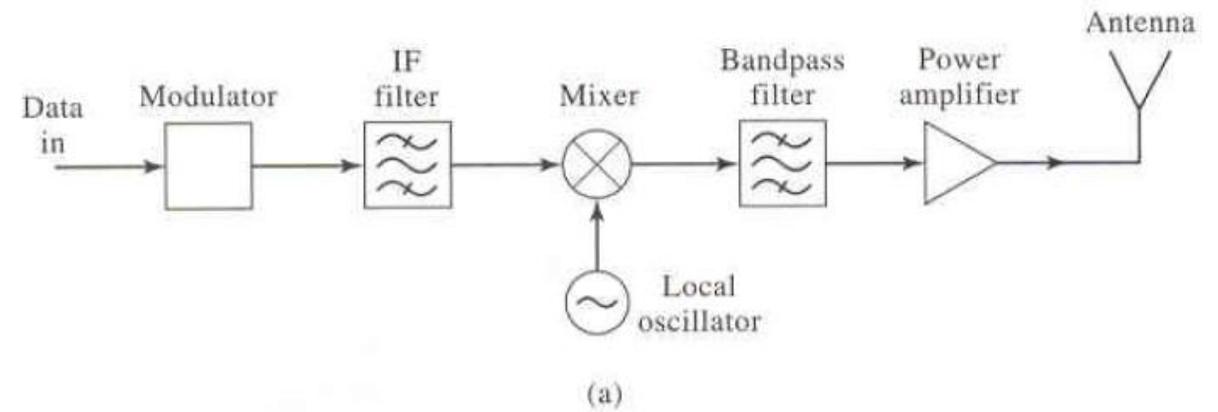
# Basic TX and RX blocks

- Digitization
- Filtering
- Mixing
- Generation
- Amplification



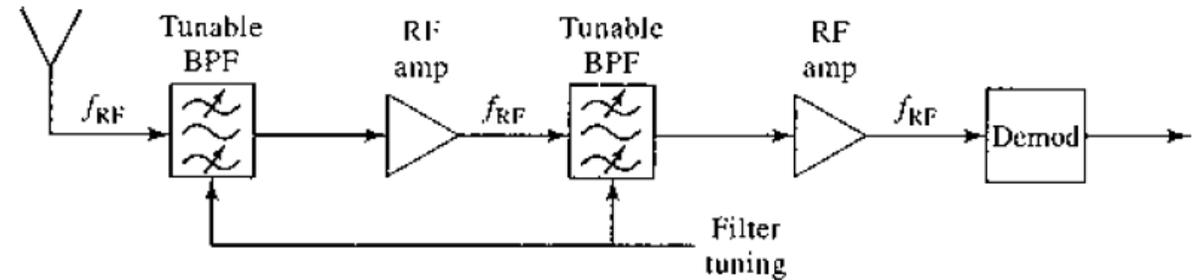
# Downconversion Architectures (1)

- Tuned receivers
  - Modern: direct digitization receivers





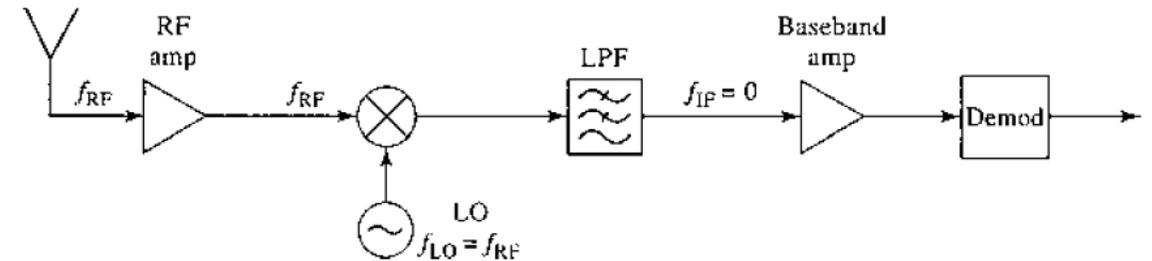- Direct conversion receivers
  - Zero IF, homodyne
  - No image frequency
  - Stability, precision!
    - Doppler RADAR
  - Sensitive to DC offsets



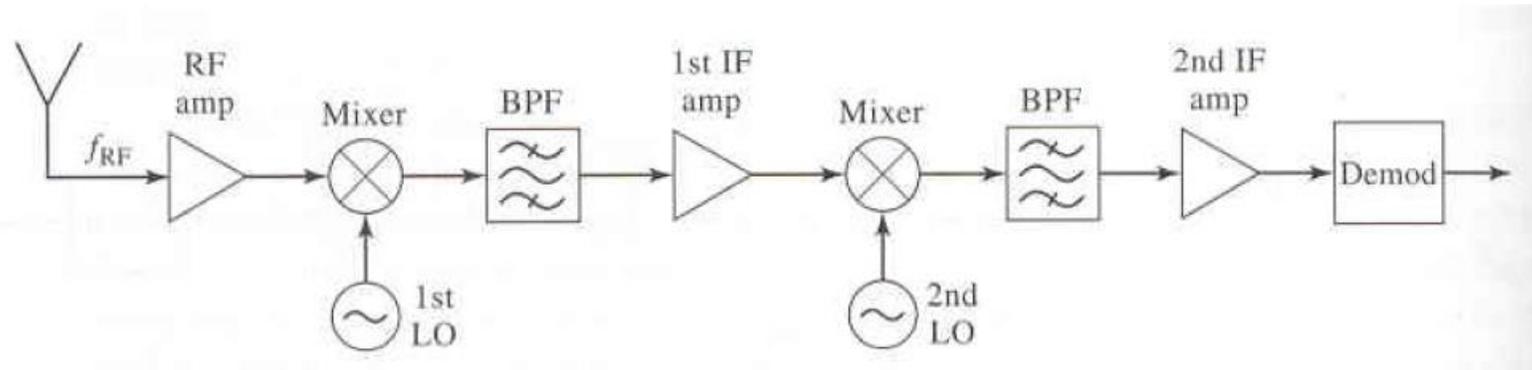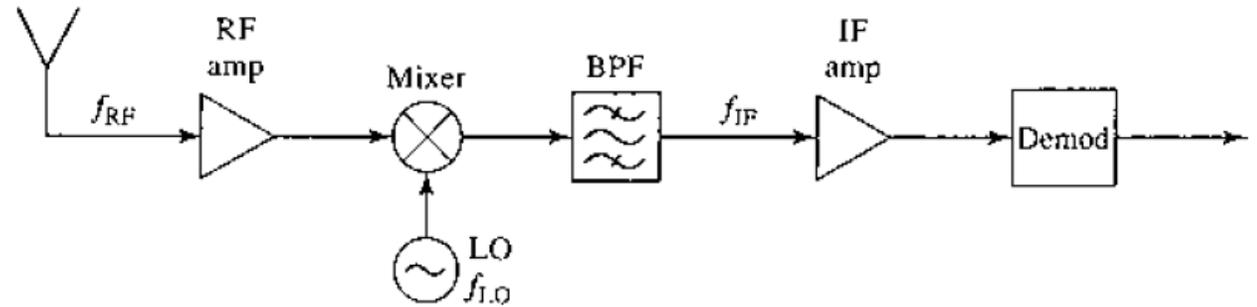
# Downconversion Architectures (2)

- Superheterodyne
  - Non-zero IF (filters)
  - More stages sometimes used
    - More LOs, IFs



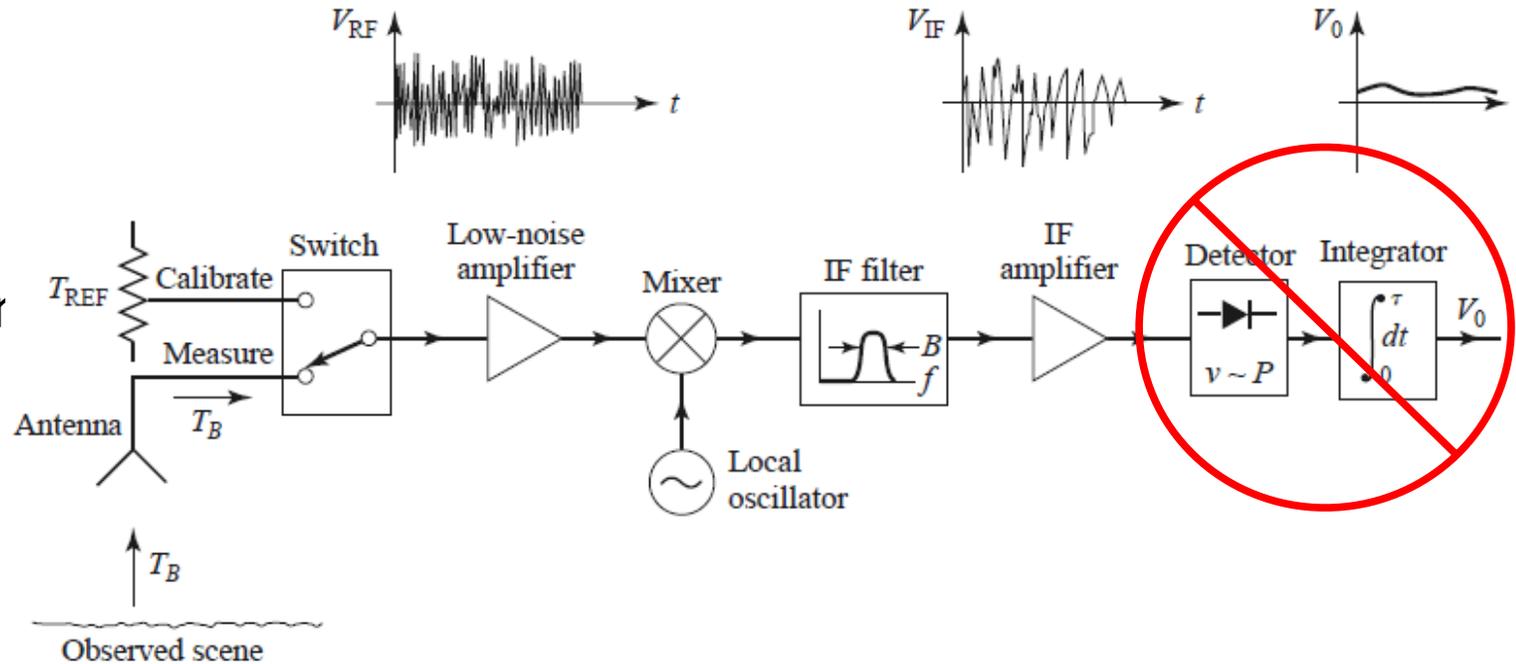
# Radiometer receivers

- Total power radiometer
  - Simple
  - Gain variation
  - Can't distinguish between system and observed T
  - Regular calibration!
- Analog diode detection less common today
  - Analog-to-digital conversion + digital signal processing


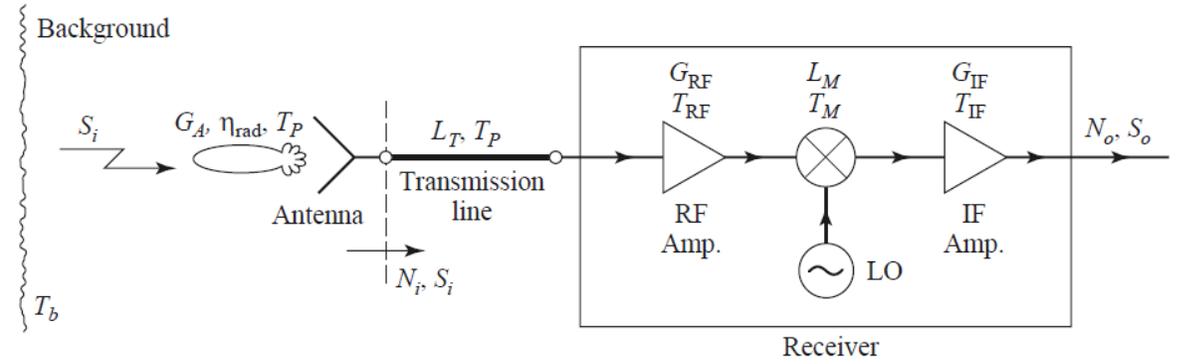
# Noise in receivers

- Everything generates noise
  - Loss == noise
- Noise floor increases down the chain
- Need  $\text{SNR}_{\min}$  for demod




$$\frac{S_o}{N_o} = \frac{S_i}{kBT_{\text{SYS}}} = \frac{S_i}{kB[\eta_{\text{rad}}T_b + (1 - \eta_{\text{rad}})T_p + (L_T - 1)T_p + L_T T_{\text{REC}}]}$$

| System                   | SNR (dB) |
|--------------------------|----------|
| Analog voice             | 5–10     |
| Analog telephone         | 25–30    |
| Analog television        | 45–55    |
| AMPS cellular            | 18       |
| AM-PCM                   | 30–40    |
| QPSK ( $P_e = 10^{-5}$ ) | 10       |

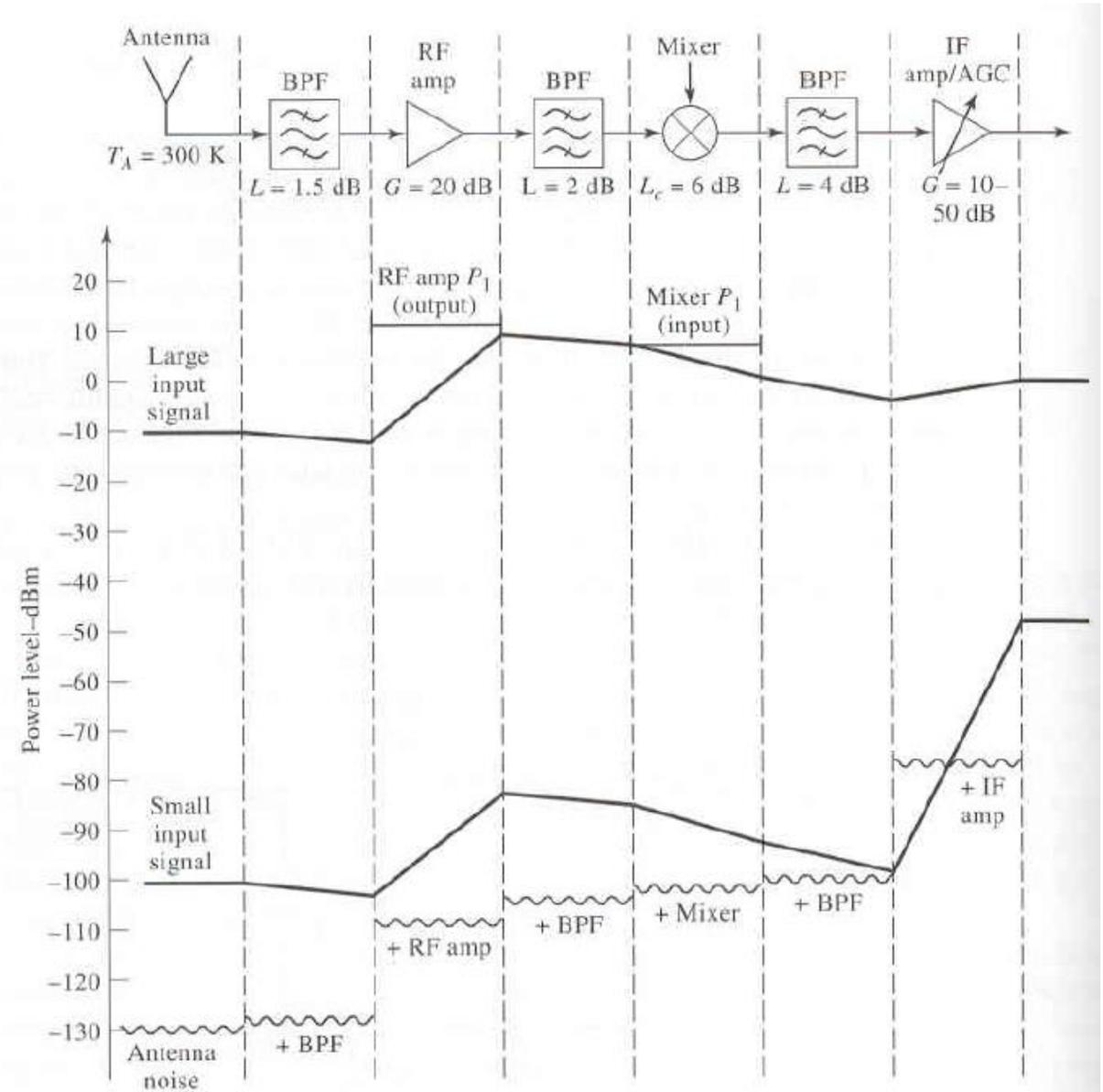
# Dynamic Range

- “Ceiling” limited by compression
- “Floor” limited by noise



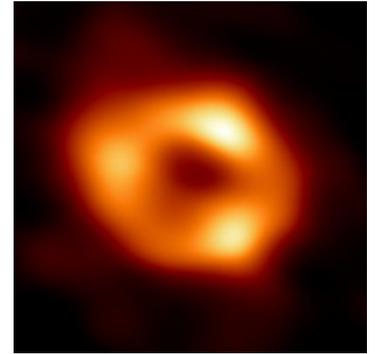
# New receiver trends

- Wideband, multi-band
  - Frequency Phase Transfer (FPT)
  - Establish coherence with longer wavelength observation, transfer to higher band
  - Need concurrent observations over wide separated bands.






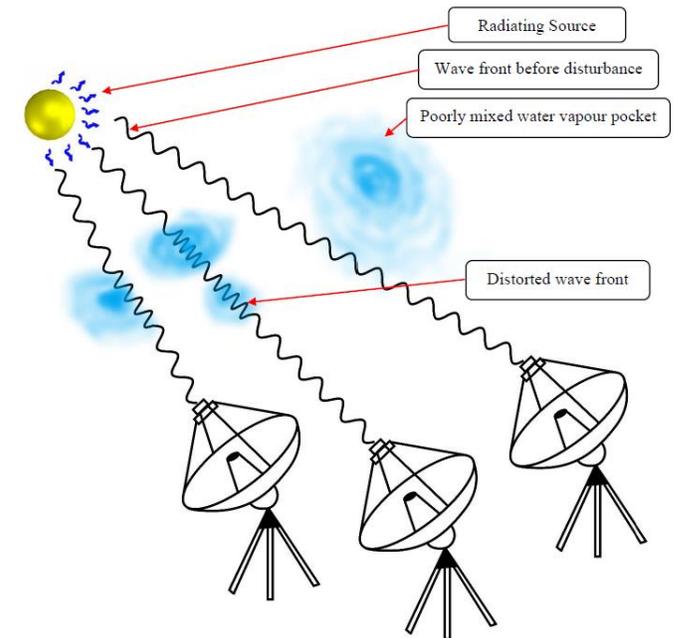Sgr A\*. Image courtesy of EHT Collaboration, [www.eventhorizontelescope.org](http://www.eventhorizontelescope.org)


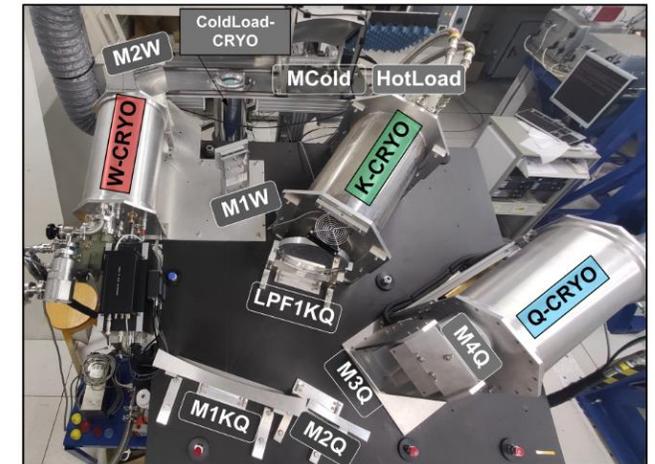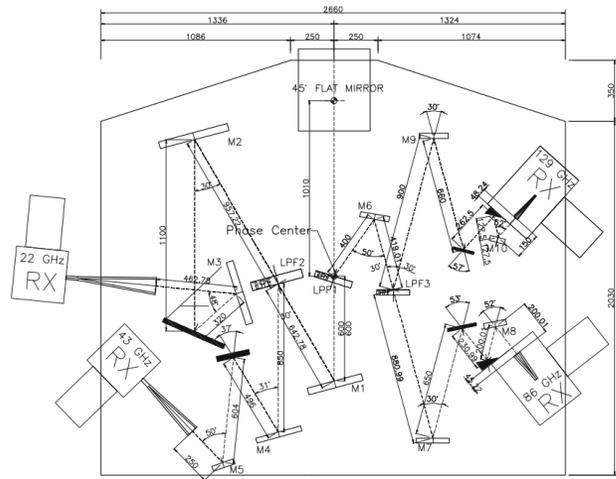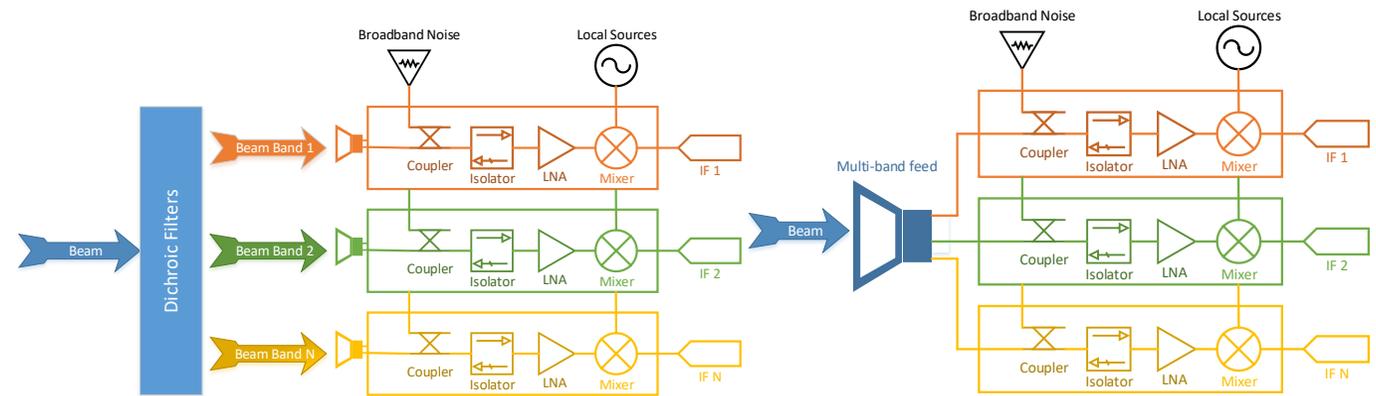
# Multi-band observation with multiple receivers



- Typically: multiple independent receivers, optical beam splitting.
- Some multi-band feeds
- Examples:
  - KVN, Yebes 40m, TNRT 22, 43, 86, 129 GHz
  - Sardinia (L-P), RAEGE (2.4, 8, 30 GHz).



S.-T. Han et al., "Millimeter-wave Receiver Optics for Korean VLBI Network," *Int. J. Infrared Millimeter Waves*, vol. 29, no. 1, pp. 69–78, Jan. 2008; F. Tercero et al., "Yebes 40 m radio telescope and the broad band Nanocosmos receivers at 7 mm and 3 mm for line surveys," *Astron. Astrophys.*, vol. 645, p. A37, Jan. 2021; Stander et al, ICEAA 2024

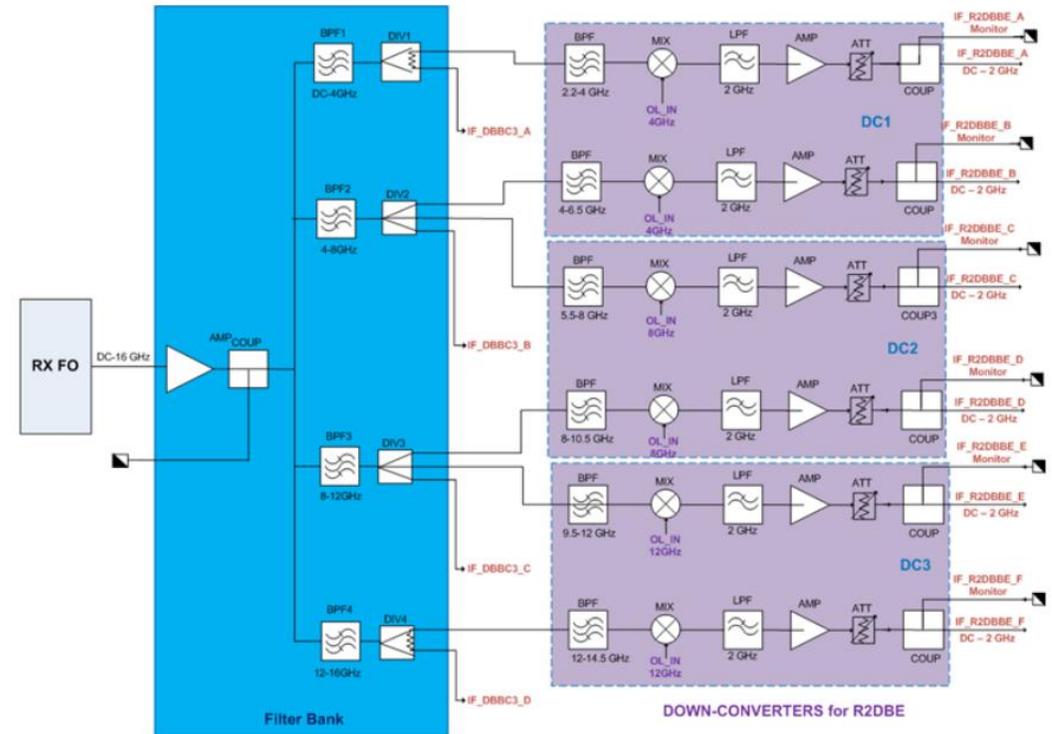
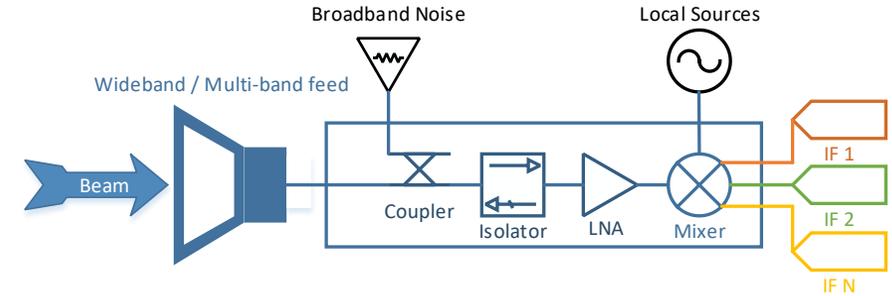
# Wideband receivers

- All-in-one-go
  - Observation bands selected by downconversion / IF
- Examples:
  - VGOS


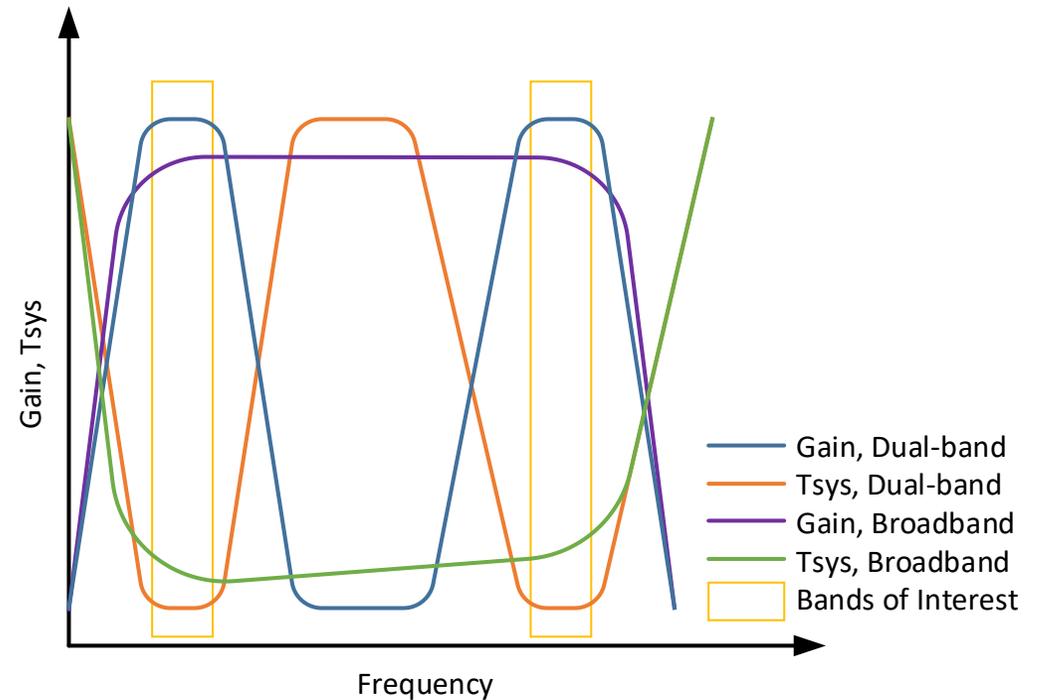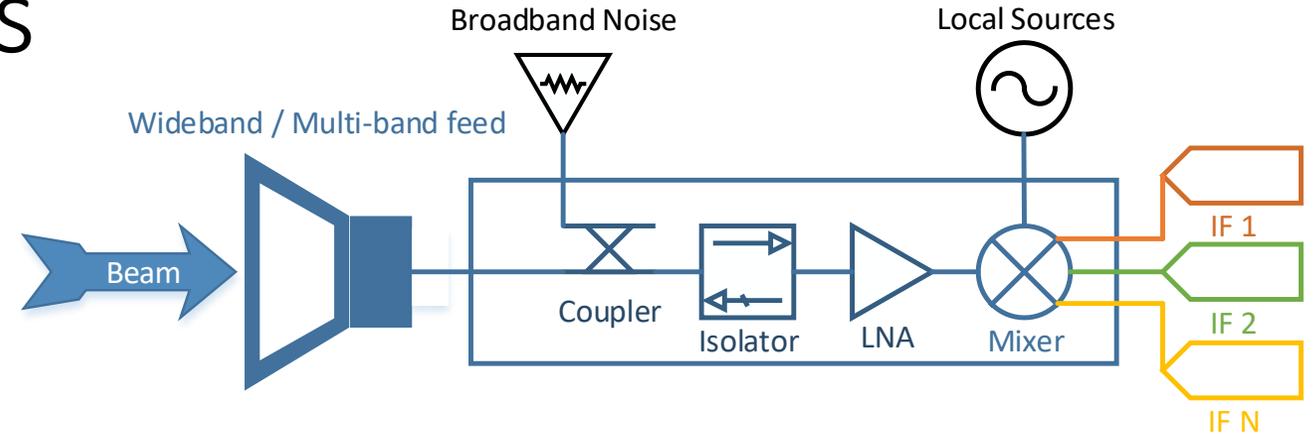
# Multi-band receivers

- Multiple concurrent bands
- 4:1  $\rightarrow$  6:1 separation
- Individual FBWs of 3%  $\rightarrow$  9%
- Wideband = optimized for unused spectrum
- *What is the appropriate wideband / multi-band mix?*
- *Look at components first!*



# And the winners are...


For receiver 4:1  $\rightarrow$  6:1 band spacing, FBWs of 3%  $\rightarrow$  9%...

| Component      | Wideband                                       | Multi-band  |
|----------------|--|---|
| Feed           | Designs available                              | Needs work: Single feed point, $N > 2$ bands                    |
| LNA            | Exists, but with severe performance trade-offs | No $N > 2$ , but worth exploring!                               |
| Isolator       | Custom designs, but proven feasible.           | Would need $N > 2$ improvement, no apparent multi-band benefit? |
| Couplers       | Exist as ICs; fairly high loss                 | Exist, with independent band control, but $N > 2$ ?             |
| Downconversion | Wideband poses little difficulty               | Cascaded SSB / multi-LO   |
| OMT            | Needs investigation!                           | Needs investigation!  |

RF measurement equipment
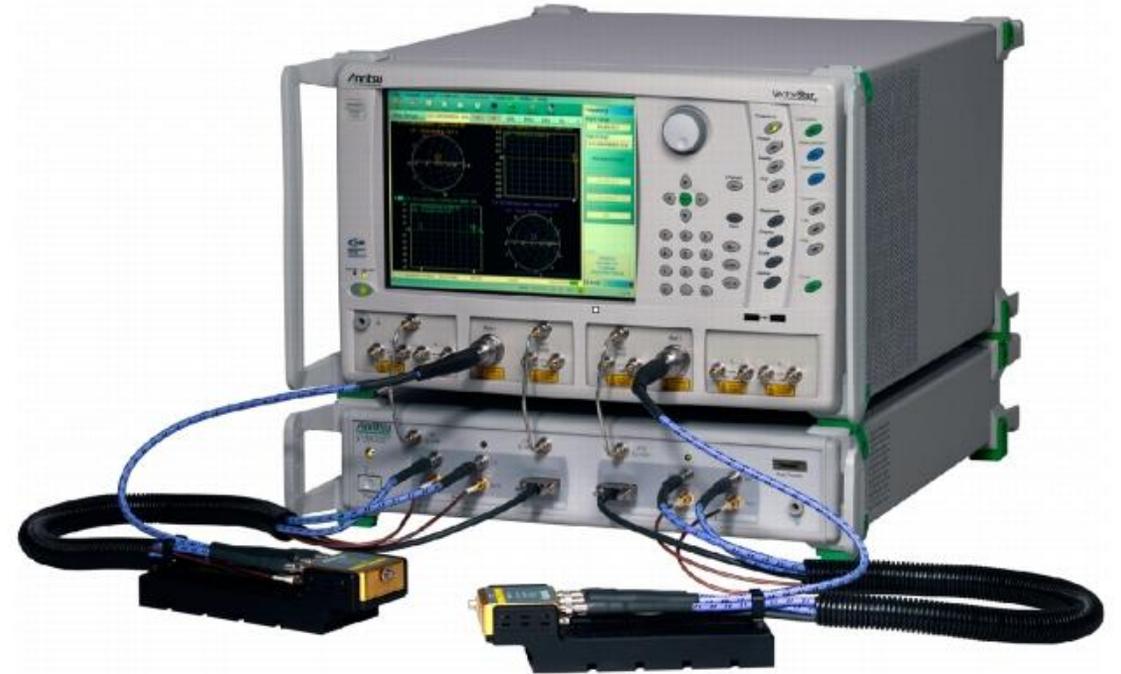
# Vector Network Analyser (VNA)

- Two or more ports
- Single frequency tone in
  - Monitors outputs at all other ports
- Linear S-parameters
  - Complex values
  - Can do power sweep
- Calibrated every time before use!



# Spectrum Analyser

- Single input port
- Provides a view of the RF spectrum
  - Multiple tones / harmonics
  - Only P over frequency




# Signal generator

- Generates an output signal for testing
- Sinusoid of controlled
  - Frequency
  - Power
- Can produce modulated output
  - Digital modulation
  - Pulsed RF


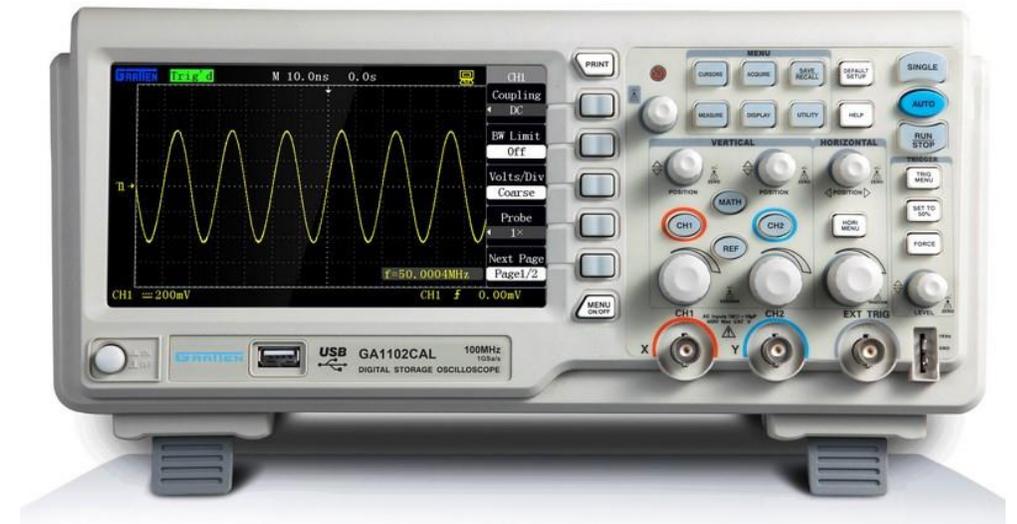
# Oscilloscope

- Voltage over time
- Modern versions go to RF frequencies
- Built-in processing available
- Need special probes
- Usually for frequencies  $< 1 - 2$  GHz



# Power meter

- Total power over the sensitivity spectrum
- Usually thermal sensor
- Used to verify power levels



# Torque wrench

- Used to connect RF connectors and cables
  - SMA, 3.5mm and up
  - Not for BNC
- Prohibits over-torque
- Always use this!
- NEVER USE AN ORDINARY WRENCH!



# References

- D. M. Pozar, Microwave engineering, 4th ed. Hoboken, NJ: Wiley, 2012.
- D. M. Pozar, Microwave and RF Design of Wireless Systems. John Wiley & Sons, Inc., 2001.
- R. Ludwig and G. Bogdanov, RF Circuit Design. Pearson Education, 2009.
- I. J. Bahl, Lumped Elements for RF and Microwave Circuits. Artech House, 2013.
- N. Honingh, SIS Mixers, <https://astro.uni-koeln.de/honingh/sis-mixers>