

An introduction to RF receivers for radio astronomy

2026 DARA February Training School

Tinus Stander
Carl and Emily Fuchs Institute for Microelectronics
Dept. EEC Engineering, University of Pretoria
tinus.stander@up.ac.za


Agenda

- RF Basics
- Noise & Distortion
- Components and Connections
- Important RF circuits
- Receiver architectures
- RF measurement equipment

RF Basics

The Decibel (dB)

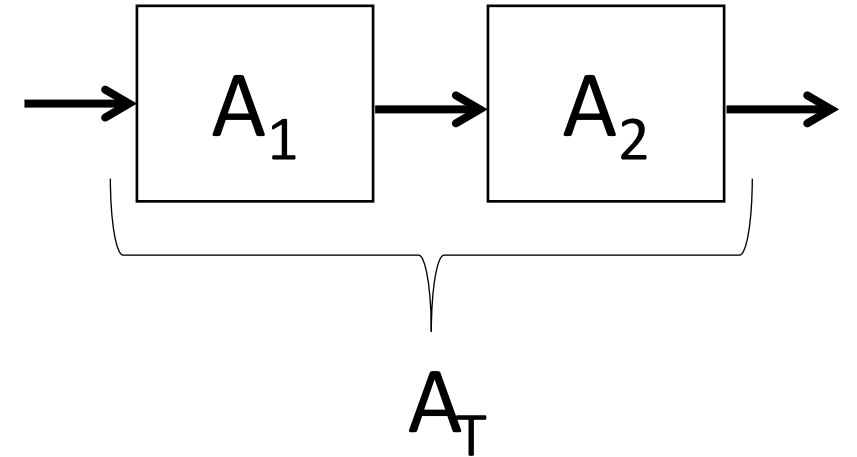- Used wherever we have a ratio
 - Usually loss or gain
- $A_T = A_1 \times A_2$
- Power: $A_x \text{ (dB)} = 10\log(A_x)$
- Voltage / Current / S-parameters:
 $A_x \text{ (dB)} = 20\log(A_x)$
- $A_T \text{ (dB)} = A_1 \text{ (dB)} + A_2 \text{ (dB)}$
- $A > 0 \text{ dB}$: gain
- $A < 0 \text{ dB}$: loss



The S-parameter (Scattering Matrix)

- Incident and reflected voltage wave relationships
 - Frequency variant
 - Complex
- All ports terminated Z_0
 - Characteristic impedance of system
- Important ones for $N = 2$:
 - S_{21} : Forward transmission
 - S_{11} : Input reflection
 - S_{22} : Output reflection
 - S_{12} : Reverse transmission
- Reciprocal: $S_{21} = S_{12}$


$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & & & \vdots \\ S_{N1} & \cdots & & S_{NN} \\ \vdots & & & \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}$$

$$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0 \text{ for } k \neq j}$$

$$[S] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$


Wires and Interconnects

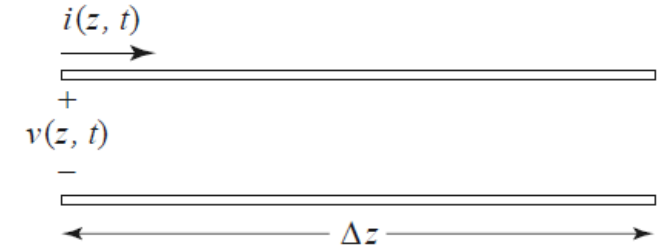- DC approximation: $i(z=0) = i(z = z_x)$, $v(z=0)=v(z=z_x)$
- Non-negligible other effects:
 - Inductance
 - Resistance
 - Stray capacitance (get to that with TX lines)
- Lumped Element approximation: $z_x \ll \lambda/10 \rightarrow \lambda/20$






Transmission Lines

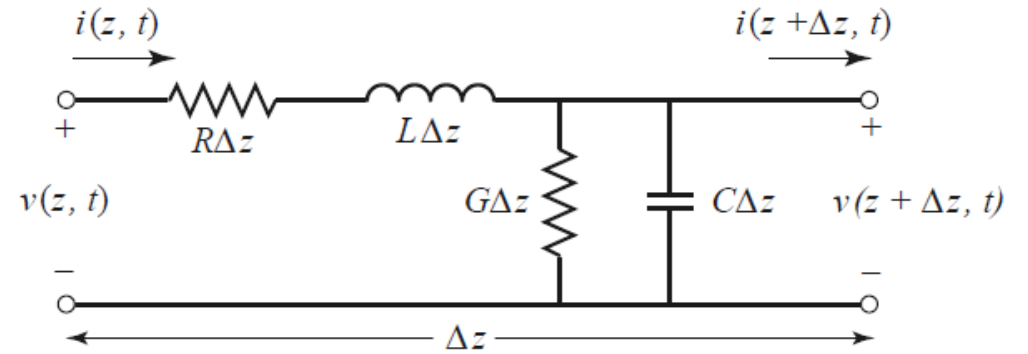- Wave propagating along medium
 - $v(z,t)$, $i(z,t)$
 - Finite phase shift
- Medium characteristics
 - Z , β , α
 - Reflection
- TEM modes
 - Nondispersive, 2+ conductors
- TE, TM modes
 - Dispersive, 1+ conductor




$$v_p = \frac{\omega}{\beta} = \lambda f, \quad Z_0 = \sqrt{\frac{L}{C}}, \quad \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}}$$
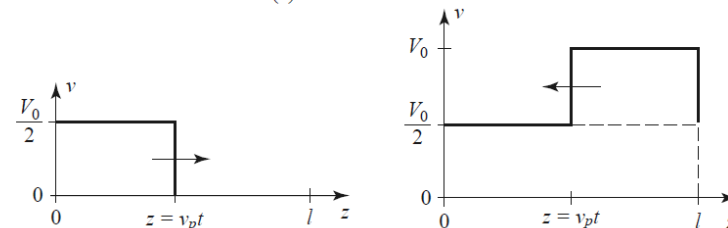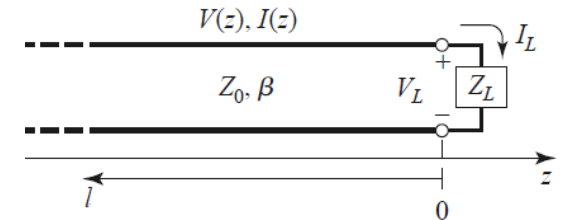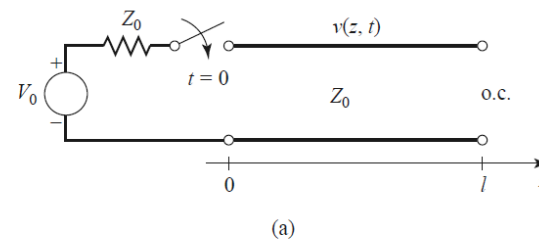
$$\alpha \simeq \frac{1}{2} \left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) = \frac{1}{2} \left(\frac{R}{Z_0} + GZ_0 \right)$$



Impedance matching

- Maximum power delivery between matched source and load
- Sometimes a specific source impedance is sought
 - We'll get to that later
- In cases of mismatch: impedance matching network
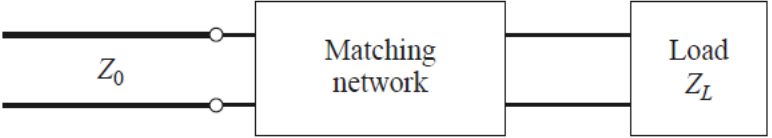
$$Z_{\text{in}} = Z_0 \frac{1 + \Gamma_{\ell} e^{-2j\beta\ell}}{1 - \Gamma_{\ell} e^{-2j\beta\ell}} = Z_0 \frac{Z_{\ell} + jZ_0 \tan \beta\ell}{Z_0 + jZ_{\ell} \tan \beta\ell},$$


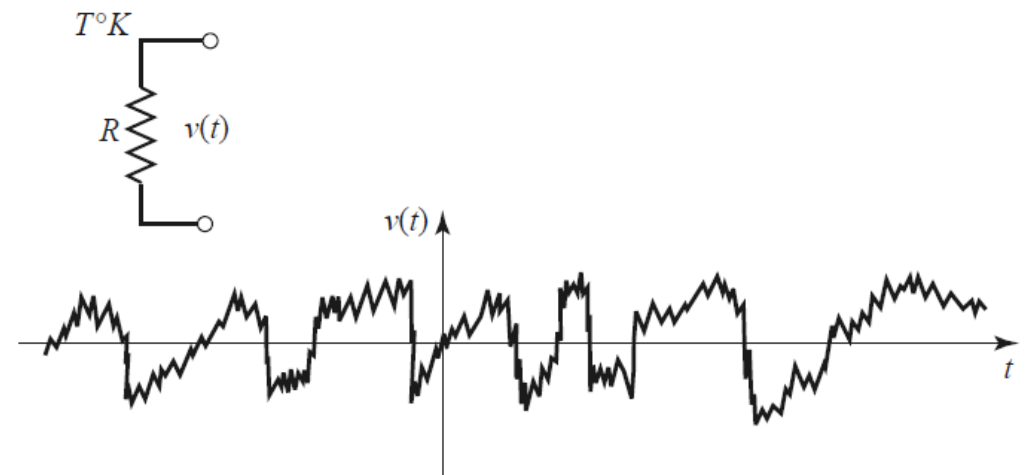
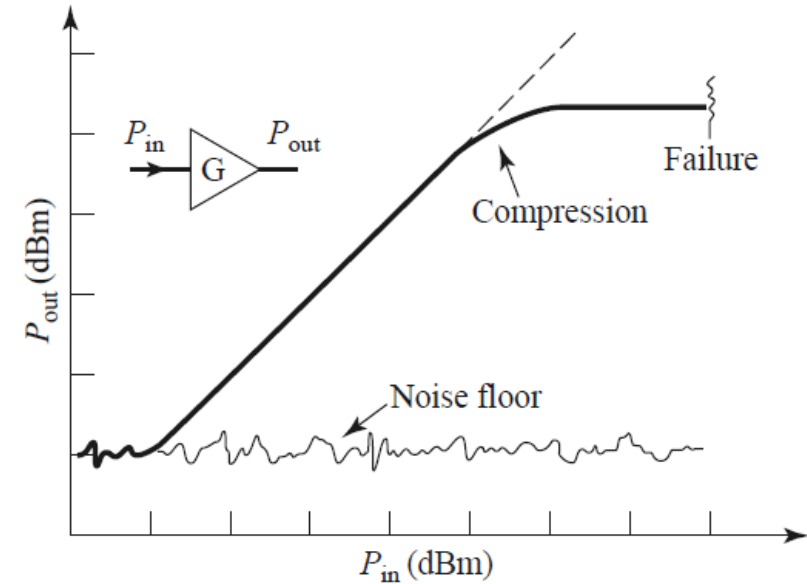
The diagram illustrates an impedance matching setup. On the left, two horizontal lines represent a transmission line with characteristic impedance Z_0 . These lines enter a rectangular box labeled "Matching network". From the right side of the "Matching network" box, two horizontal lines exit and enter another rectangular box labeled "Load Z_L ".

$$\Gamma_{\ell} = \frac{Z_{\ell} - Z_0}{Z_{\ell} + Z_0}.$$

Noise


General principles (1)

- Random variation
 - Internal: charge carriers
 - Thermal noise (Johnson / Nyquist)
 - Shot noise
 - Flicker (1/f) noise
 - External: physical phenomenon
 - Thermal emissions, cosmic background
 - Sources = interferers, not noise
 - Flat spectrum = “white noise”
 - Zero average, nonzero RMS
- Limits dynamic range
 - Other end: compression / distortion




General principles (2)

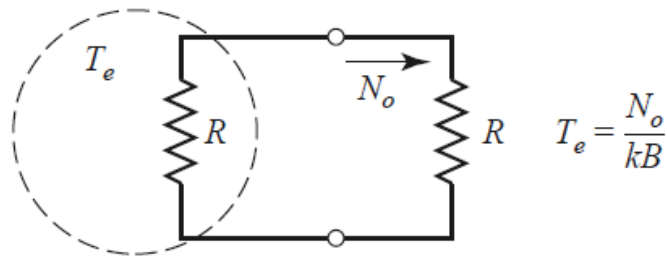
- Link between noise and temperature
- Planck blackbody
 - Rayleigh-Jeans approx. okay, except
 - $f > 1 \text{ THz}$, $K \ll 300\text{K}$
- Equivalent noise temperature
- Used for noise-generating components
- Used for antennas




$$T_e = \frac{N_o}{kB}$$

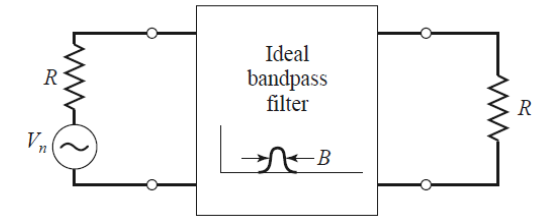

$$V_n = \sqrt{4kTBR}.$$

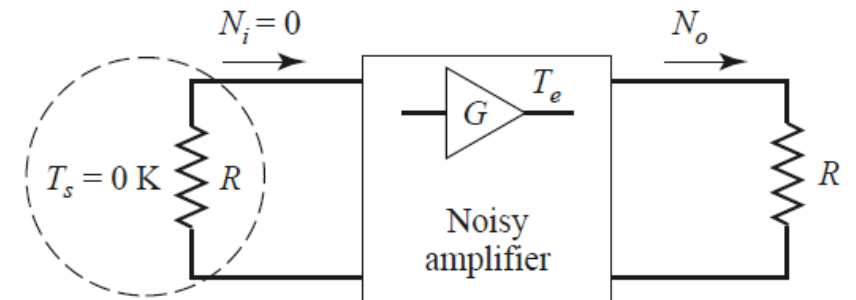


(a)

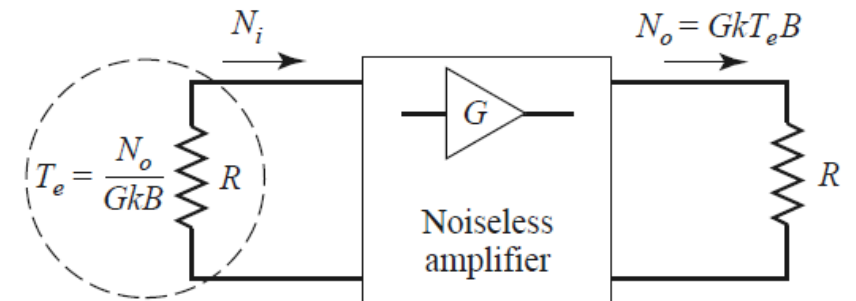

(b)

Noise Measurement

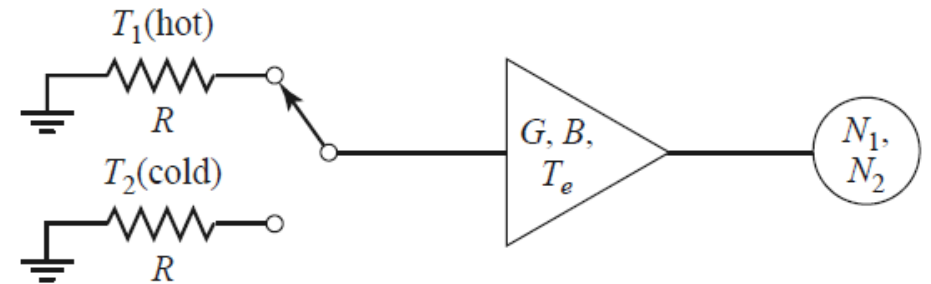- Y-factor method
- Switch between “hot” and “cold” loads
- Need $Y \gg 1$
 - $T_1 \gg T_2$
 - $T_1, T_2 \gg T_e$
- Re-write i.t.o. ENR: T_1/T_2
 - ENR tables provided in noise sources




$$N_1 = GkT_1B + GkT_eB, \quad Y = \frac{N_1}{N_2} = \frac{T_1 + T_e}{T_2 + T_e} > 1, \\ N_2 = GkT_2B + GkT_eB,$$

$$T_e = \frac{T_1 - YT_2}{Y - 1},$$

Noise Figure

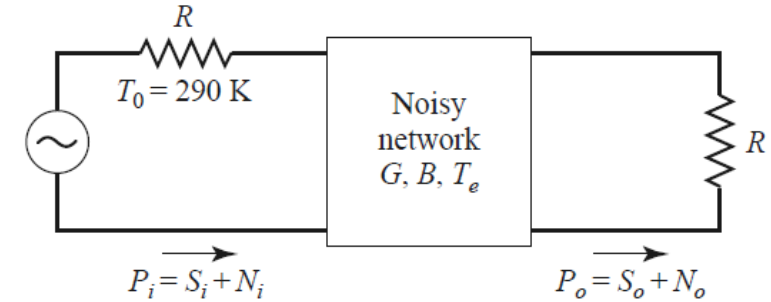
- Measure of $\text{SNR}_i/\text{SNR}_o, > 1$
- Nomenclature:
 - F = Noise Factor, linear
 - NF = Noise Figure, dB
- Defined for:
 - Matched load input
 - Reference T_0
 - Else: stick to T_e
 - Or: T_A , for antenna front-end.
- Passive, lossy components:
 - $\text{IL} = F$
 - Can apply to mismatch too: gain lower



$$F = \frac{S_i/N_i}{S_o/N_o} \geq 1,$$


$$F = \frac{S_i}{kT_0B} \frac{kGB(T_0 + T_e)}{GS_i} = 1 + \frac{T_e}{T_0} \geq 1.$$

$$T_e = (F - 1)T_0.$$

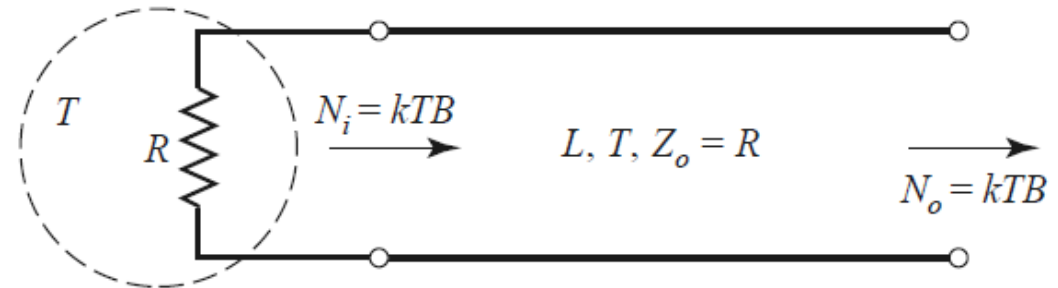

NF in Cascaded Systems

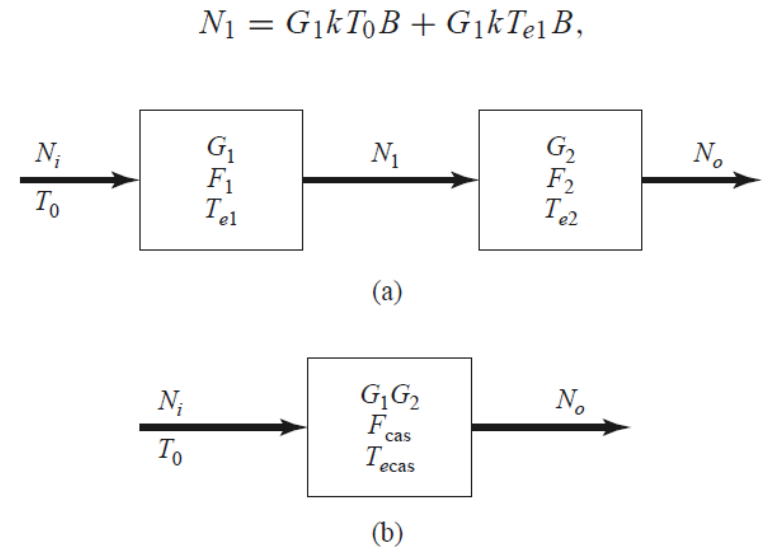- Amplifiers amplify gain AND noise!
 - $\text{SNR}_i/\text{SNR}_o$ increases down the chain
 - F increases
- Subsequent noise contribution mitigated by prior gain stages...
- First stage NF dominant in system!
 - Want T_A low as well.
- Use T, not NF, to avoid $T \neq T_0$



$$N_o = G_2 N_1 + G_2 k T_{e2} B$$


$$= G_1 G_2 k B \left(T_0 + T_{e1} + \frac{1}{G_1} T_{e2} \right).$$

$$T_{\text{cas}} = T_{e1} + \frac{T_{e2}}{G_1} + \frac{T_{e3}}{G_1 G_2} + \dots,$$

$$F_{\text{cas}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots.$$

NF of mismatched amplifiers

- F increases with mismatch

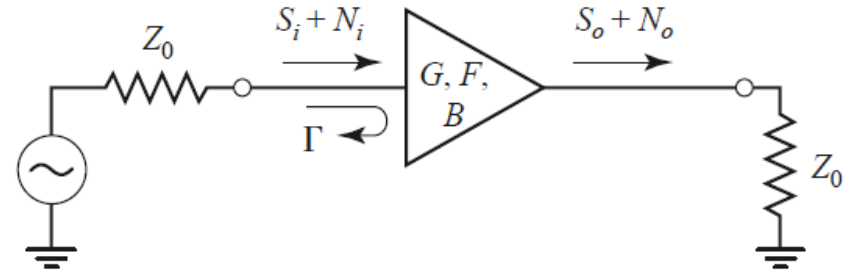


$$N_o = kT_0 GB(1 - |\Gamma|^2) + kT_0 (F - 1) GB$$



$$F_m = \frac{S_i N_o}{S_o N_i} = 1 + \frac{F - 1}{1 - |\Gamma|^2}.$$

Phase noise

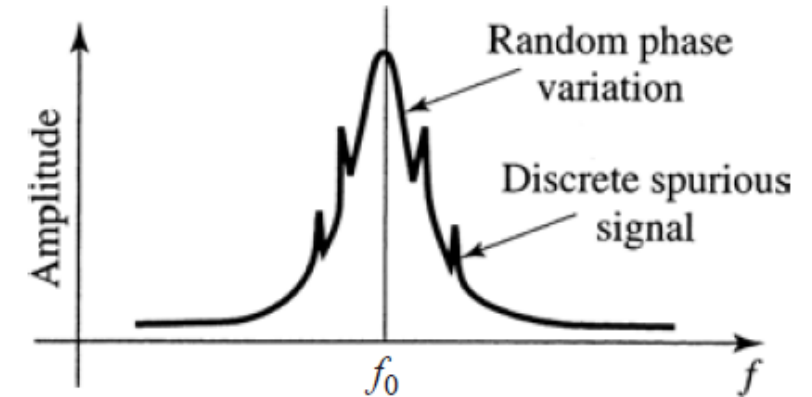- Random variation of tone f_0
 - Frequency or phase variation
 - Increase noise power
 - Error in downconversion
- Expressed in dBc/Hz @ offset f_m
- Spectrum described by Leeson's model
 - For oscillators with resonators of Q.
 - High Q reduces L
- f_α corner frequency of $1/f$
 - Transistor dependent
- Far out: amplifier NF



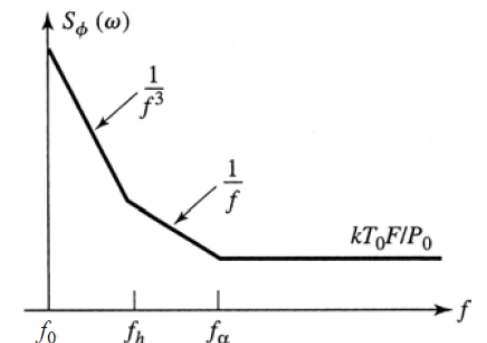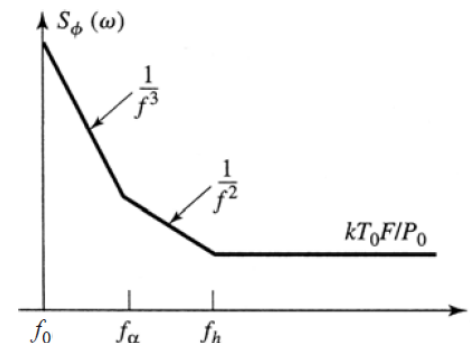
$$S_\phi(\omega) = \frac{kT_0 F}{P_0} \left(\frac{K \omega_0^2 \omega_\alpha}{4 Q_0^2 \Delta \omega^3} + \frac{\omega_0^2}{4 Q_0^2 \Delta \omega^2} + \frac{K \omega_\alpha}{\Delta \omega} + 1 \right)$$



Phase noise (2)

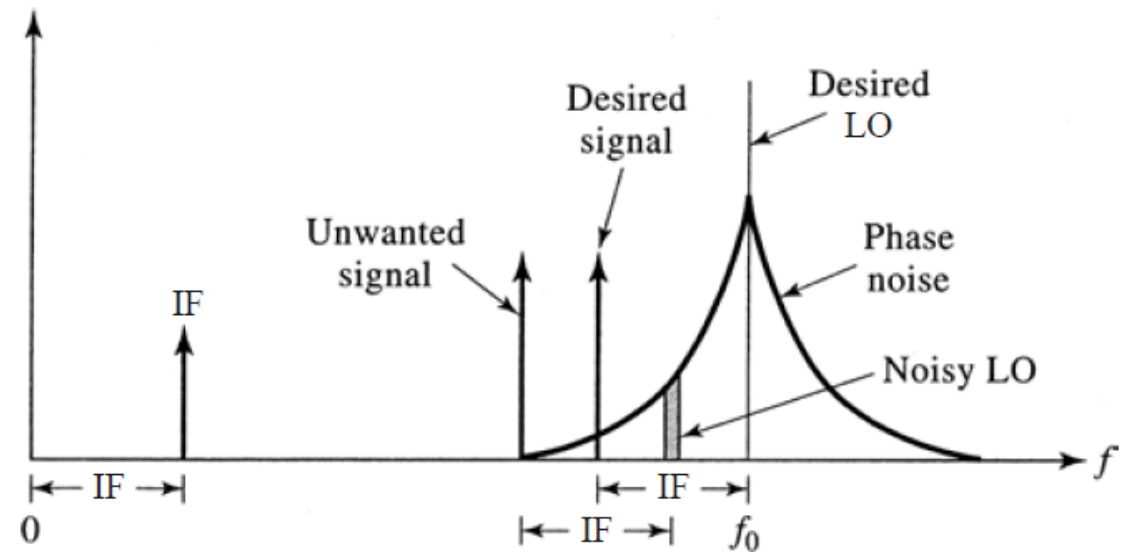- Downconversion error
- Maximum interferer tolerable -> choice of L spec.



$$\mathcal{L}(f_m) = C \text{ (dBm)} - S \text{ (dB)} - I \text{ (dBm)} - 10 \log(B), \text{ (dBc/Hz)},$$

Distortion

Nonlinear effects & distortion

- Harmonic generation
- Saturation (gain reduction, AM-AM distortion)
- Intermodulation (two tones mix)
- AM-PM conversion (amplitude → phase shift)
- N order of terms
 - DC, linear, quadratic, etc.





$$v_o = a_0 + a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots,$$

$$\begin{aligned} v_o &= a_0 + a_1 V_0 \cos \omega_0 t + a_2 V_0^2 \cos^2 \omega_0 t + a_3 V_0^3 \cos^3 \omega_0 t + \dots \\ &= \left(a_0 + \frac{1}{2} a_2 V_0^2 \right) + \left(a_1 V_0 + \frac{3}{4} a_3 V_0^3 \right) \cos \omega_0 t + \frac{1}{2} a_2 V_0^2 \cos 2\omega_0 t \\ &\quad + \frac{1}{4} a_3 V_0^3 \cos 3\omega_0 t + \dots \end{aligned}$$


Different kinds of distortion

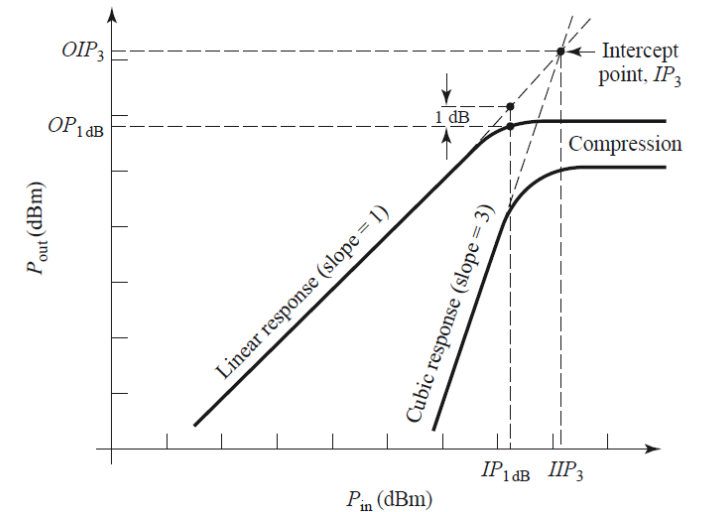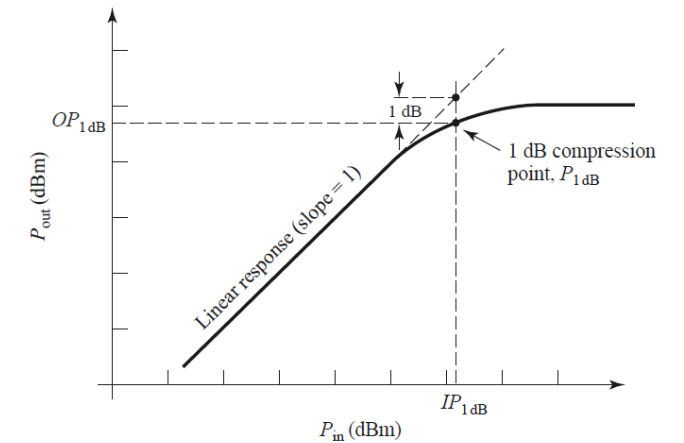- Gain compression (P1db)
 - Lower than expected output
- Third order intercept (IIP3/OIP3)
 - Mixing term of two-tone input
- Passive intermodulation (PIM)
 - Parasitic diodes from oxidation on metal
 - Only a consideration at high power



Dynamic Ranges

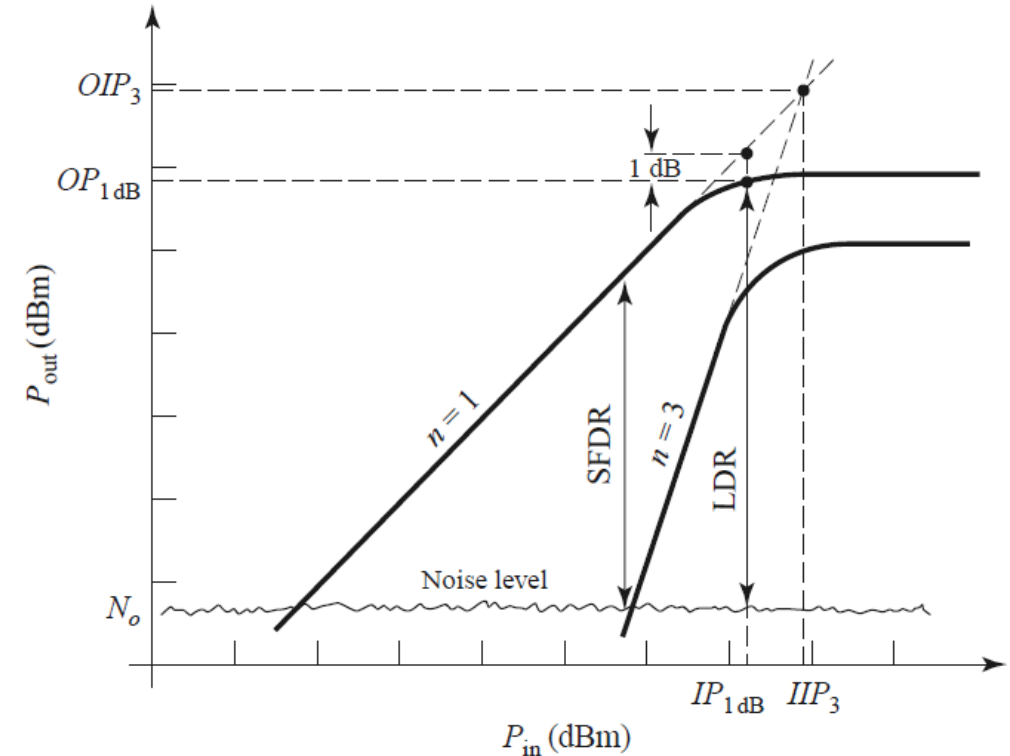- Power range over which performance is desirable
- Limited by which undesired effect we want to avoid!
- Linear dynamic range (LDR)
 - Range over which operation is “linear”
 - Noise floor $\rightarrow$ $P_{1\text{dB}}$
- Spurious free dynamic range (SFDR)
 - Range over which spurs below noise floor
 - Typ. 3rd order ($2f_2 - f_1$, $2f_1 - f_2$)
 - SFDR typ. $\ll$ LDR








Sensitivity

- Definition specific to receiver
- Smallest detectable signal
- Sensitivity (dBm) for comms = $-174 + NF + 10\log B + SNR$
- For antenna temperature NOT 290K
 - More generally: $S_i(\min) = kB(T_A + (F-1)T_0)SNR_{\min}$

Components and Connections





Transmission media (1)

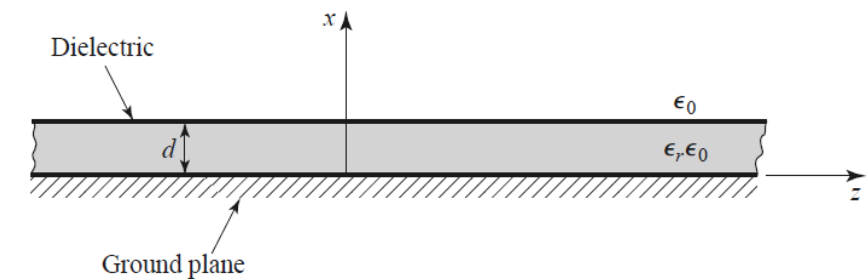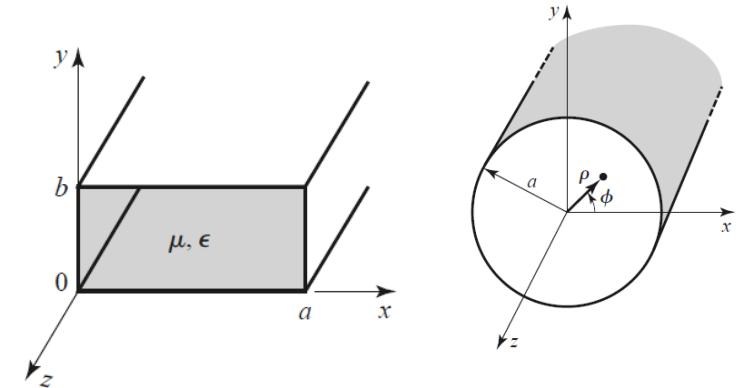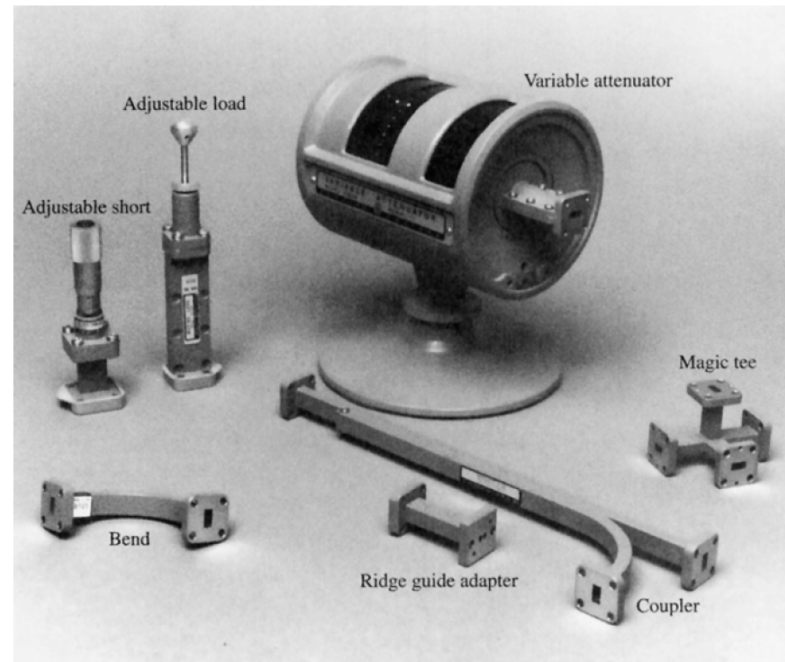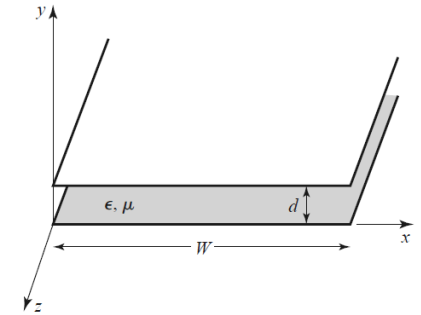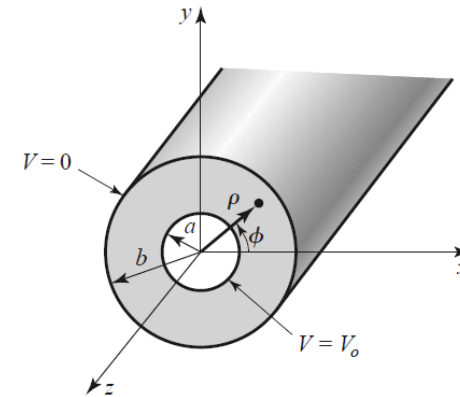- Waveguide
 - Coax
 - Modes!
 - Parallel Plate
 - Parasitic!
 - Surface Waves
 - Parasitic!
 - Rectangular, Circular





Transmission media (2)

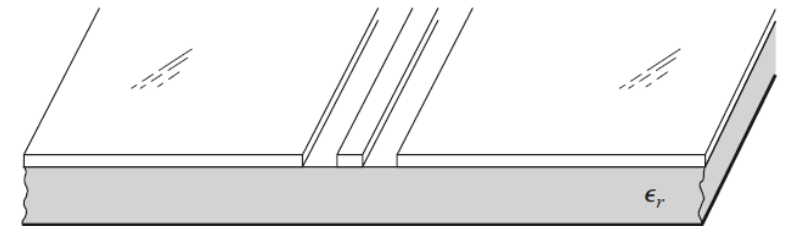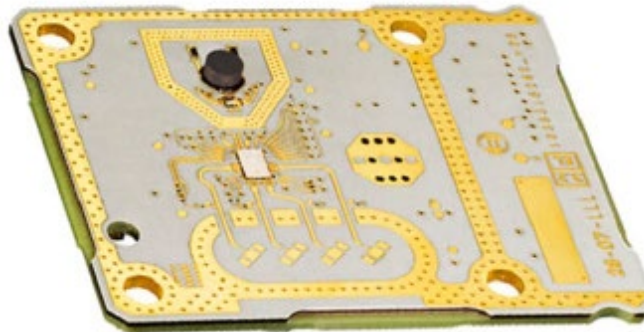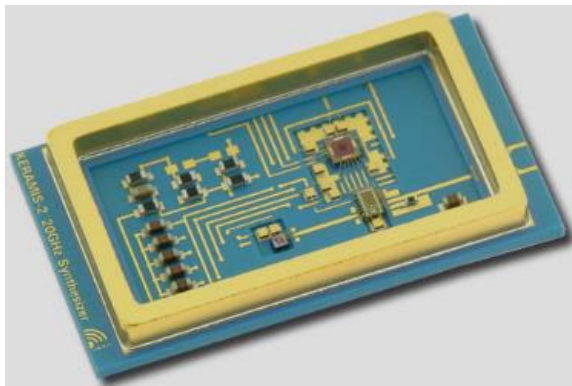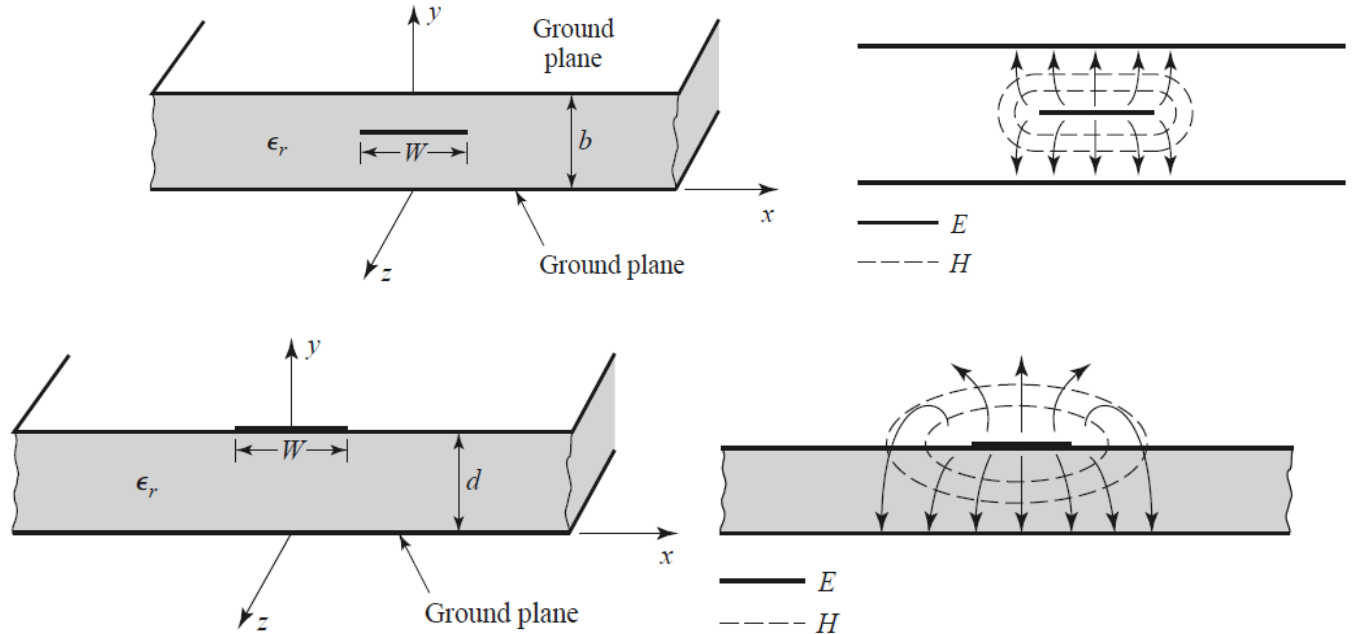- Planar
 - Stripline
 - Microstrip
 - CPW, GCPW
 - And others...
- Integrate with SMD components








Non-planar system integration

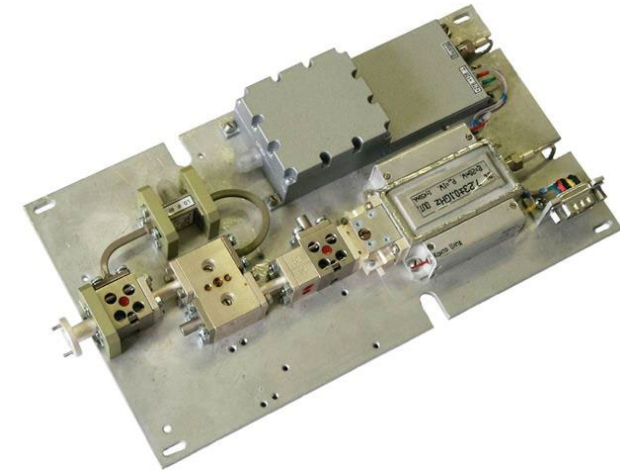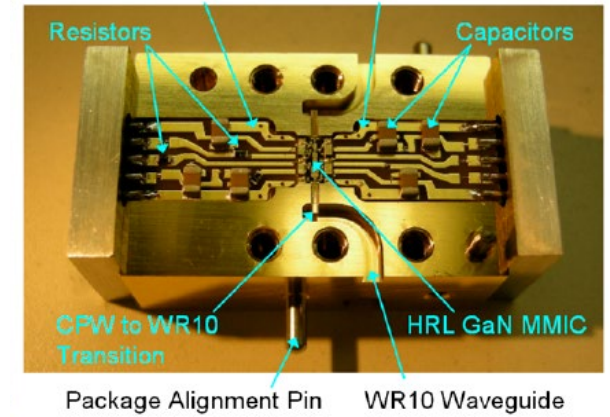- Waveguide
 - Split block / finline
 - WR standards
- Microwave coax connectors
 - Different standards for different frequencies
 - SMA most common
- Mixed modules
 - WG RF, coax IF
- Cables
 - Limited by overmoding, connectors





Passive components

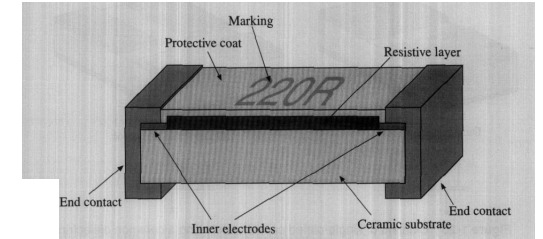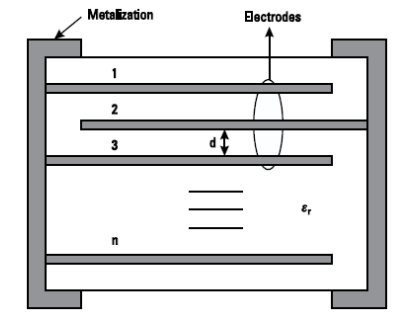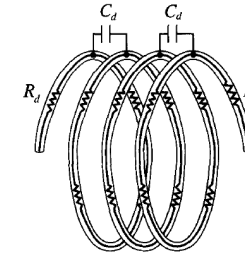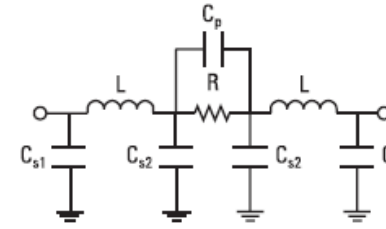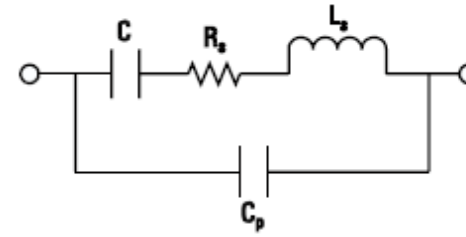
- Resistors, capacitors, inductors
 - Complex responses



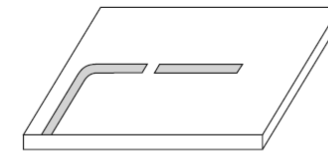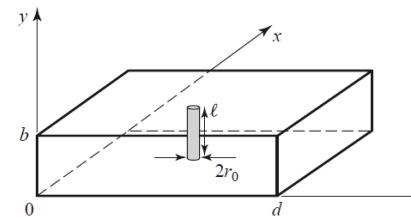
- Resonators
 - Used for e.g. filters, oscillators
 - Temporary storage of energy at a specific frequency




(a)

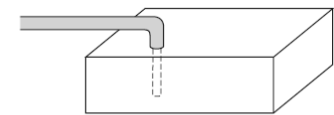

(b)

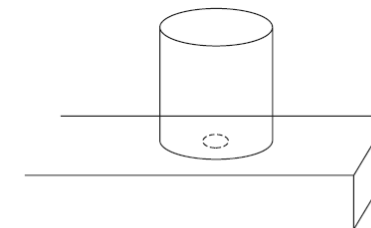






(c)

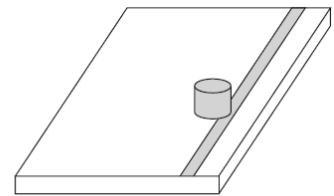

(d)


Diodes

- PN: low frequency
 - Varactor: Vary C with DC (depletion layer)
- PIN
 - DC biasing -> very linear R at RF
 - Switches, variable attenuators
- Schottky
 - Metal-semi contact
 - Fast switching; no recovery time
 - Detectors
- Tunnel Diode
 - Negative I-V region
 - Quantum well
 - Detectors, switches
- SIS mixers
 - Photon-assisted tunnelling, superconducting T's
 - Used for detecting sub-THz and THz frequencies

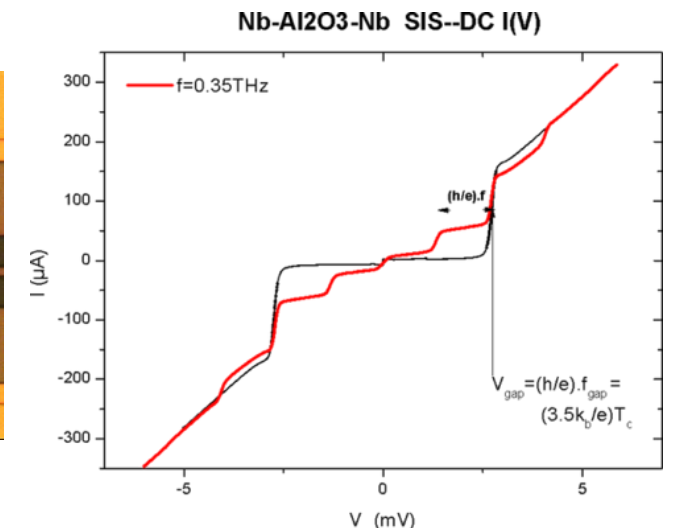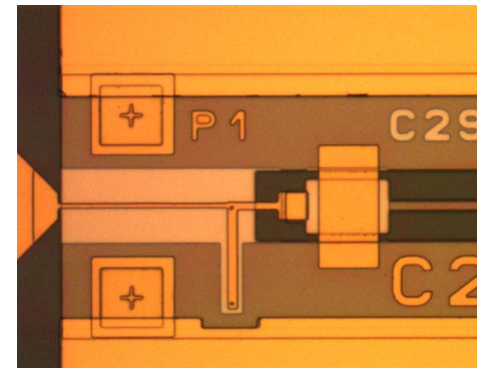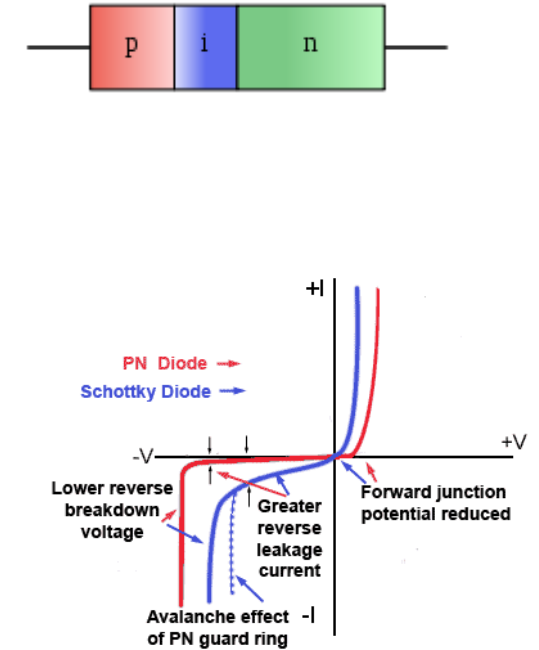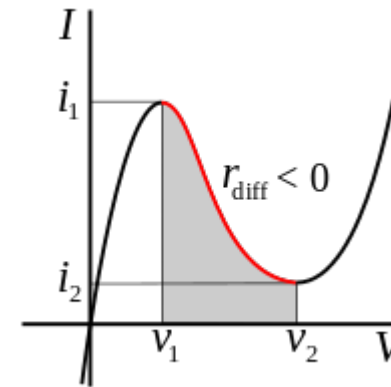
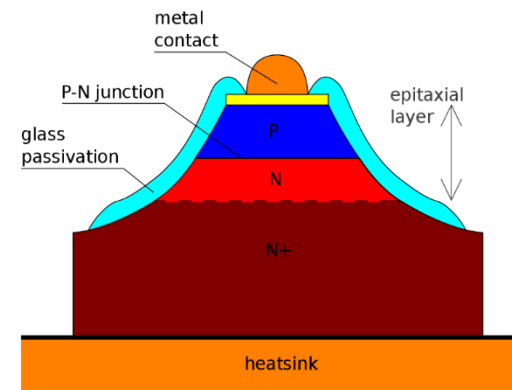


Transistors

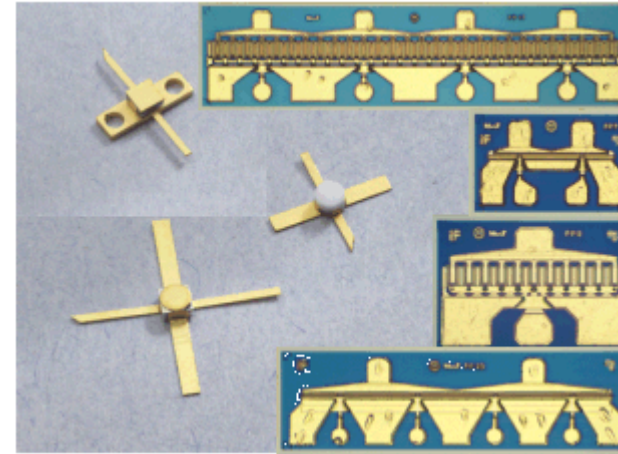- Different semiconductors
 - Si: Cheap, moderate performance
 - SiGe: More expensive, faster III-V
 - GaAs: Common in Radio Astronomy
 - InP: The best, most expensive choice
- Types
 - Bipolar: BJT / HBT
 - MOSFET, MESFET
 - HEMT





		IIIA	IVA	VA	VIA	VIIA
III-V		B Boron	C Carbon	N Nitrogen	O Oxygen	F Fluorine
		Al Aluminum	Si Silicon	P Phosphorus	S Sulphur	Cl Chlorine
IB	IIB	Ga Gallium	Ge Germanium	As Arsenic	Se Selenium	Br Bromine
Cu Copper	Zn Zinc					
Ag Silver	Cd Cadmium	In Indium	Sn Tin	Sb Antimony	Te Tellurium	I Iodine
Au Gold	Hg Mercury	Tl Thallium	Pb Lead	Bi Bismuth	Po Polonium	At Astatine

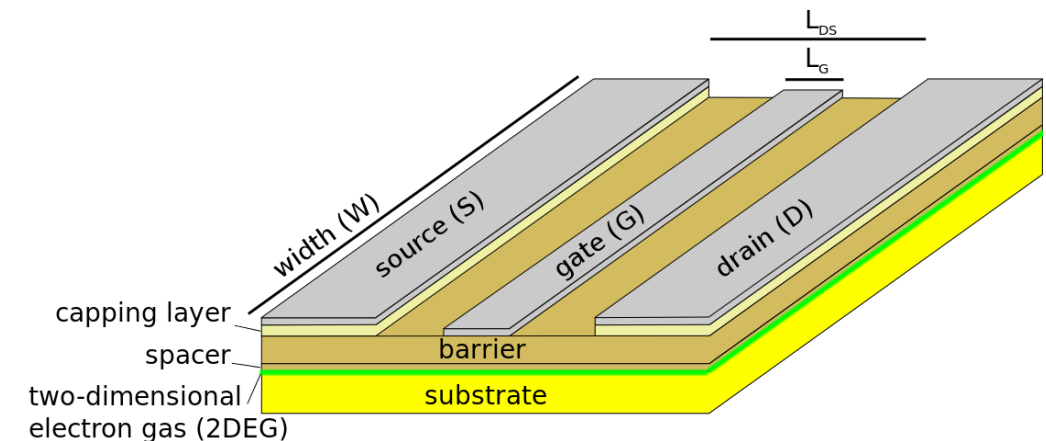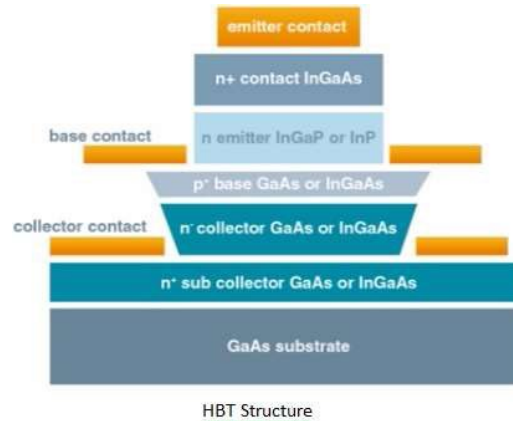

Important RF circuits

Low noise amplifiers

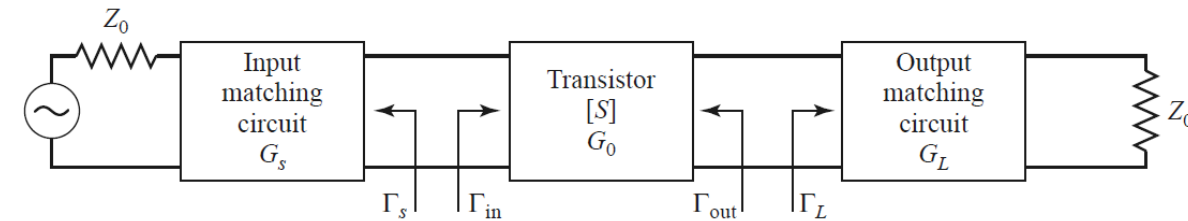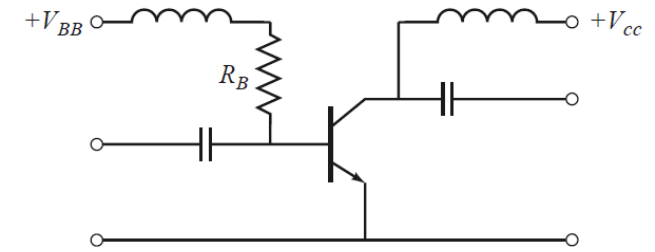- Transistor, biasing, matching
- Match for
 - Gain
 - Complex conjugate power match
 - Noise
 - $NF_{\min}$, R_N , Γ_{opt} in datasheet
 - Stability
 - ... It's a trade-off.
- Usually multiple stages




$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2},$$

$$G_0 = |S_{21}|^2,$$






$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}.$$

$$N = \frac{|\Gamma_S - \Gamma_{\text{opt}}|^2}{1 - |\Gamma_S|^2} = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{\text{opt}}|^2$$

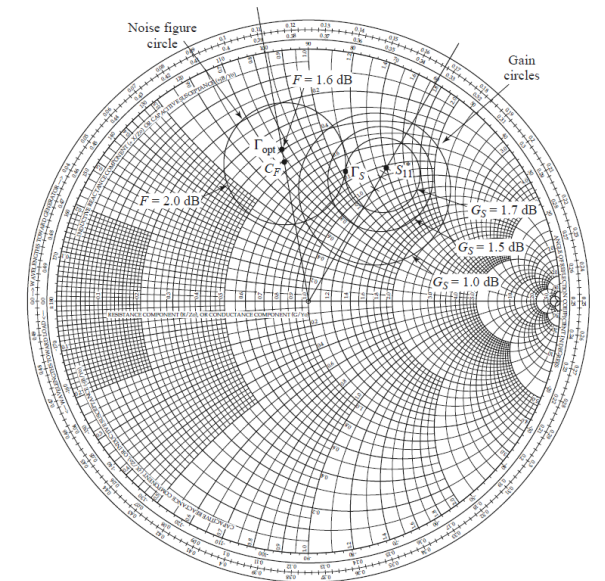




Mixers

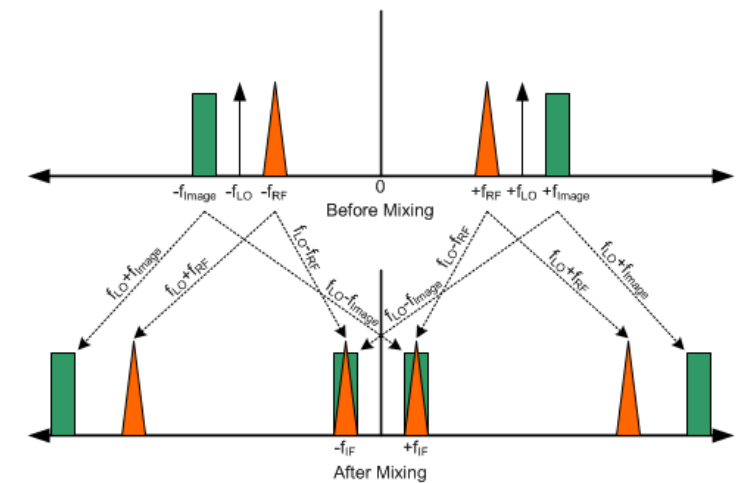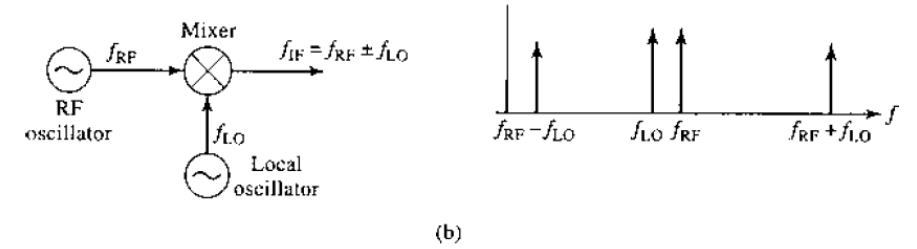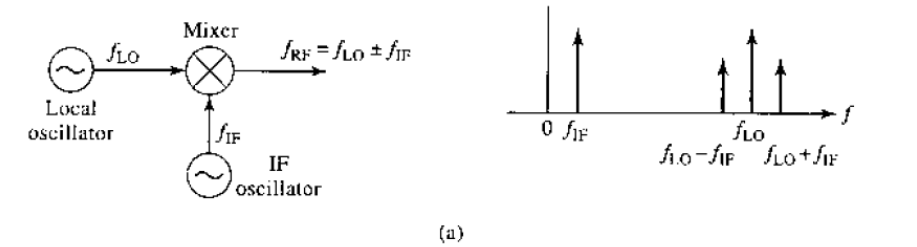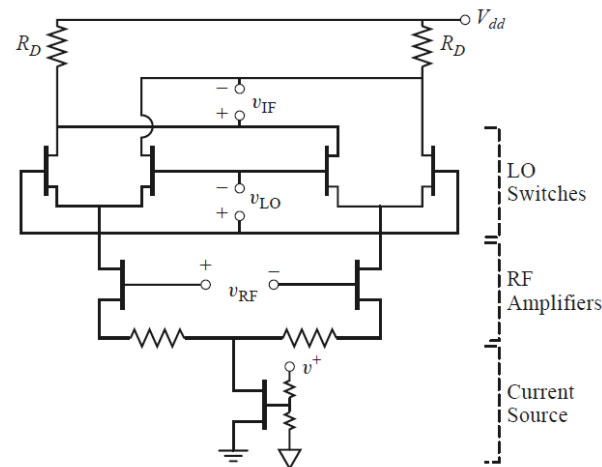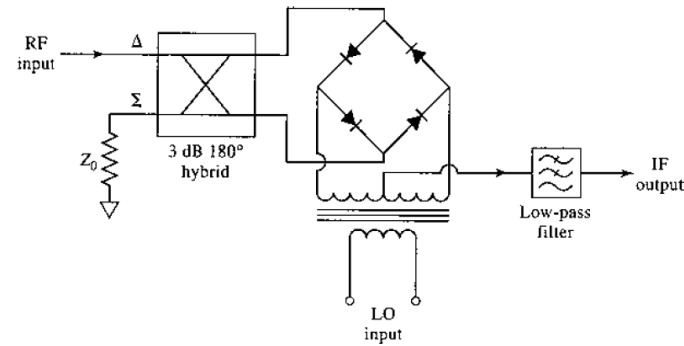- 3-port device for frequency translation
- Image frequencies!
- Diode circuits
- Transistor circuits
 - Gilbert cell
- Harmonic versions







Filters

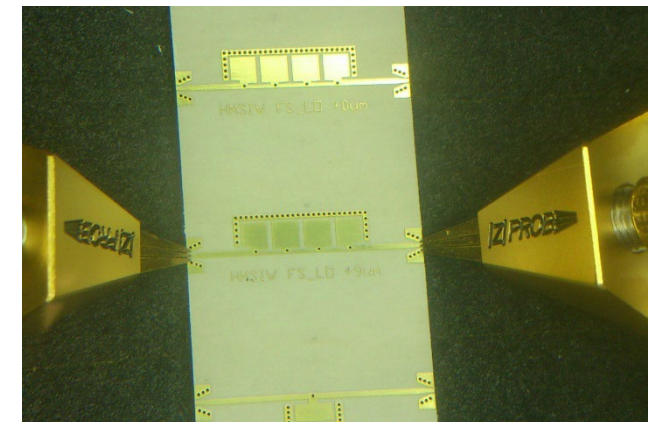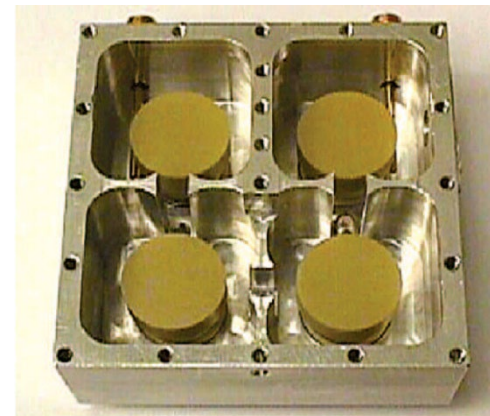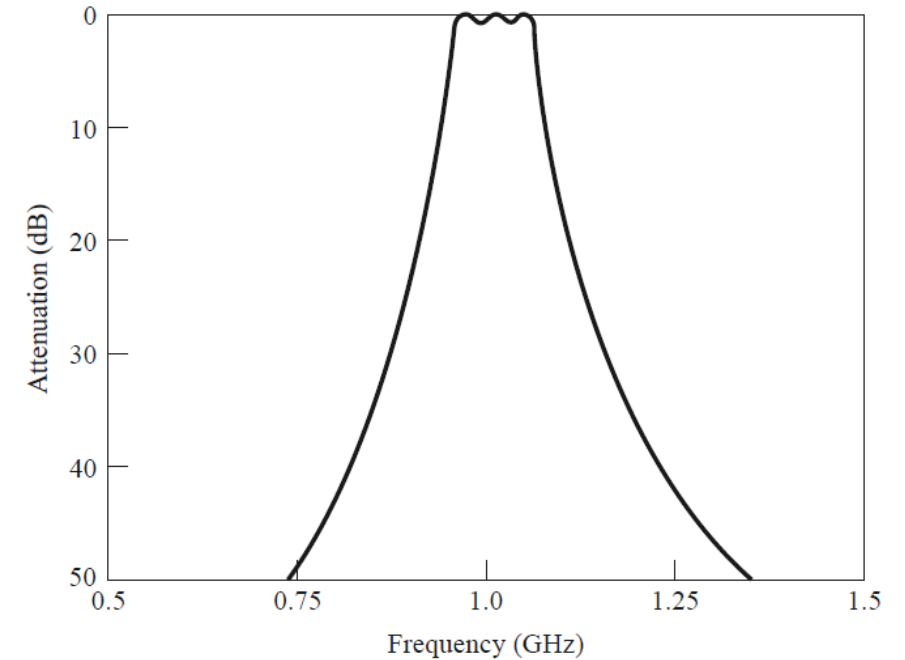- Low-pass, high-pass, band-pass, band-stop
- Frequency selective transmission
- Limits received noise band
- Suppresses mixing products
- Reject interferers
- More elements:
 - More selective
 - More loss





Oscillators

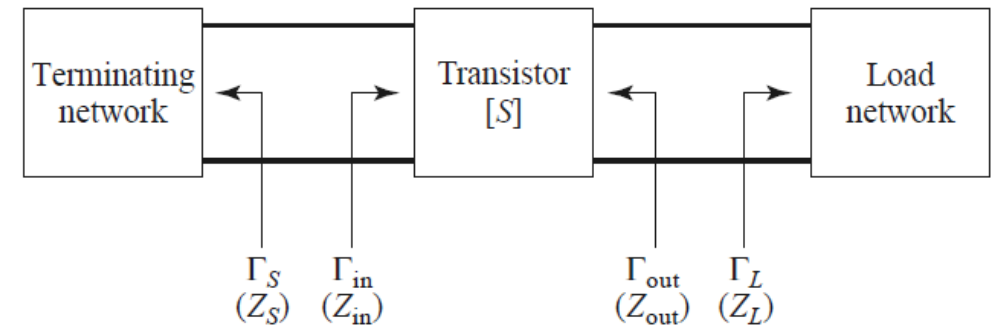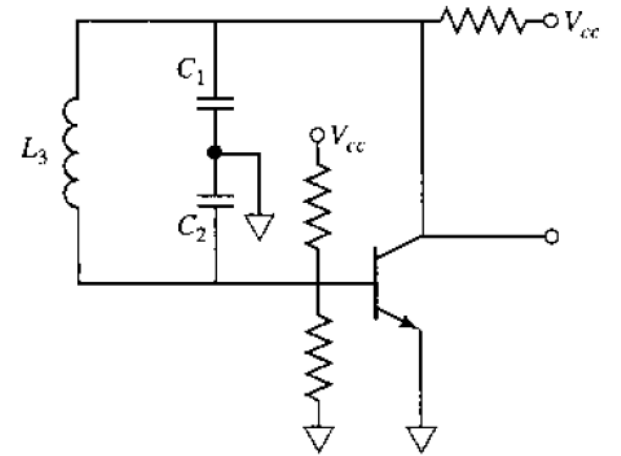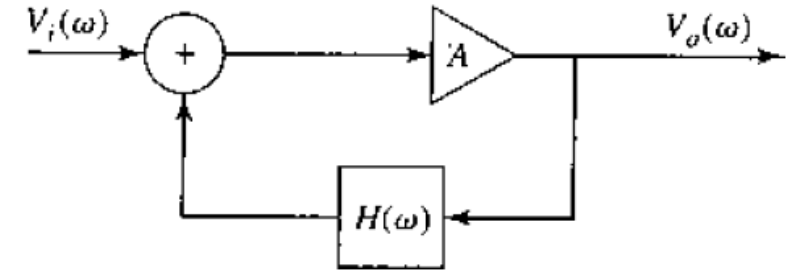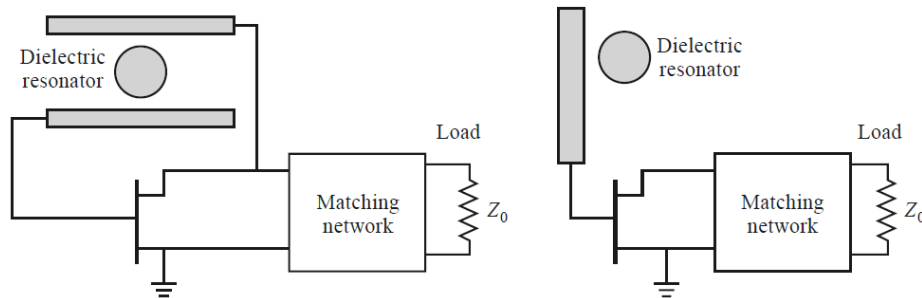- Generate a steady sinusoid
- Characterized by
 - Power
 - Phase noise
 - Tunability
- Gain + a stable feedback
 - Can use a stable reflection as well









Isolators

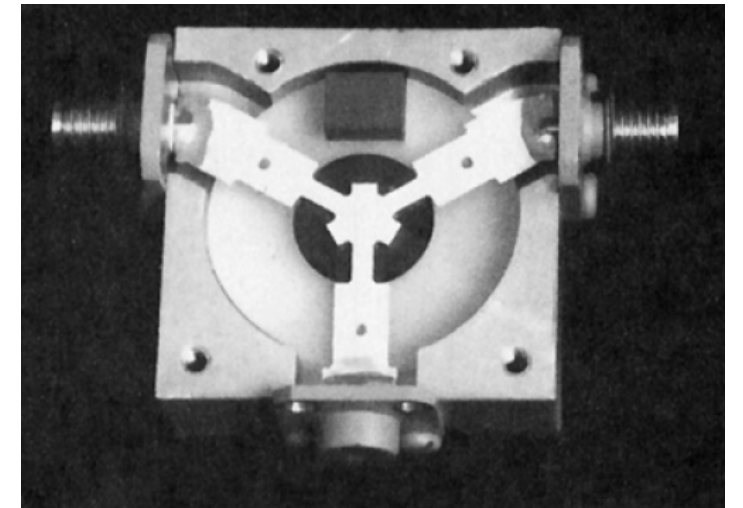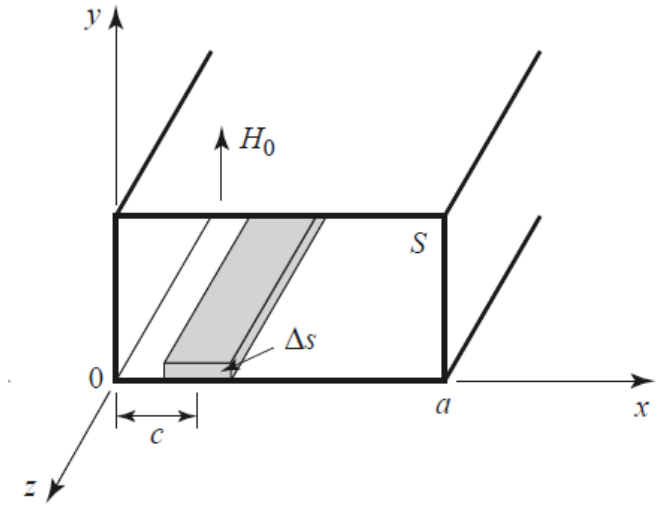- RF transmission in one direction, but not the other
 - $S_{21} \approx 0 \text{ dB}$, $S_{12} < -40 \text{ dB}$
 - Usually ferromagnetic
- Used to
 - Control noise and leakage propagation
 - Eg. LO reflection from antenna
 - Improve impedance matching
- Three-port: Circulator
 - Signal Merry-go-round




Couplers

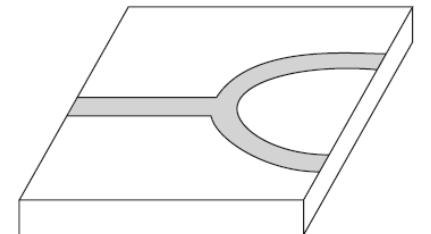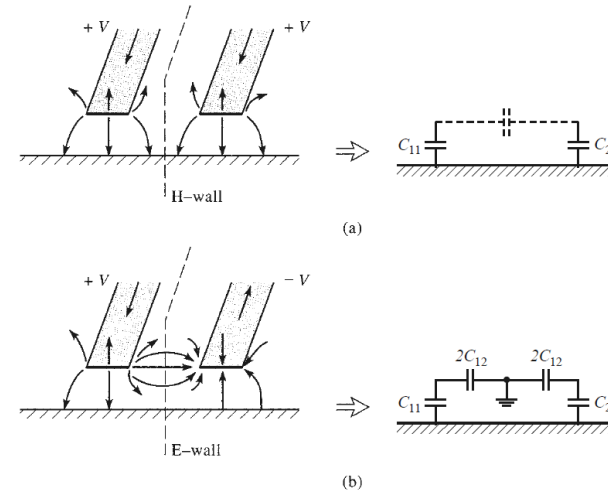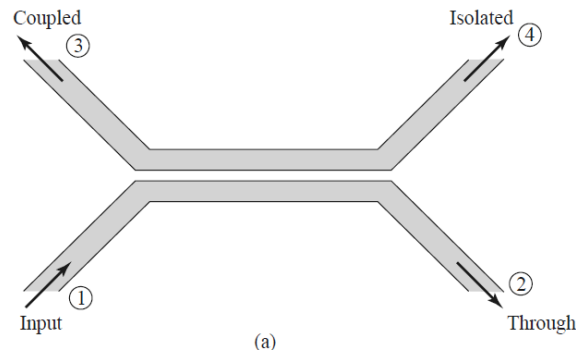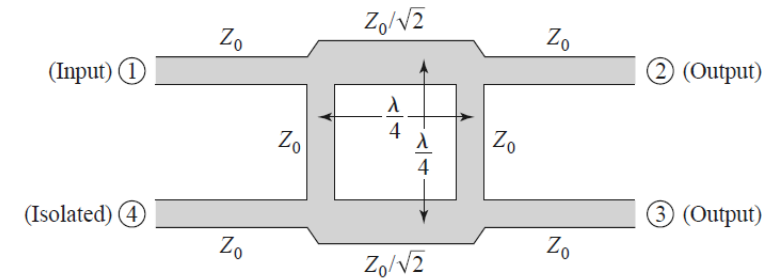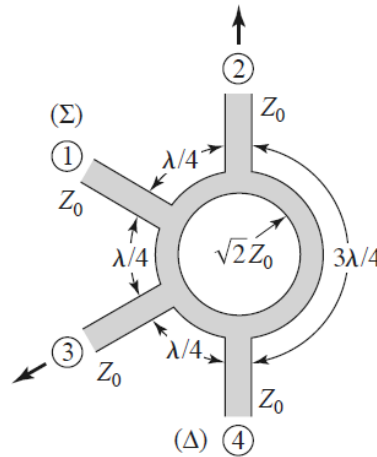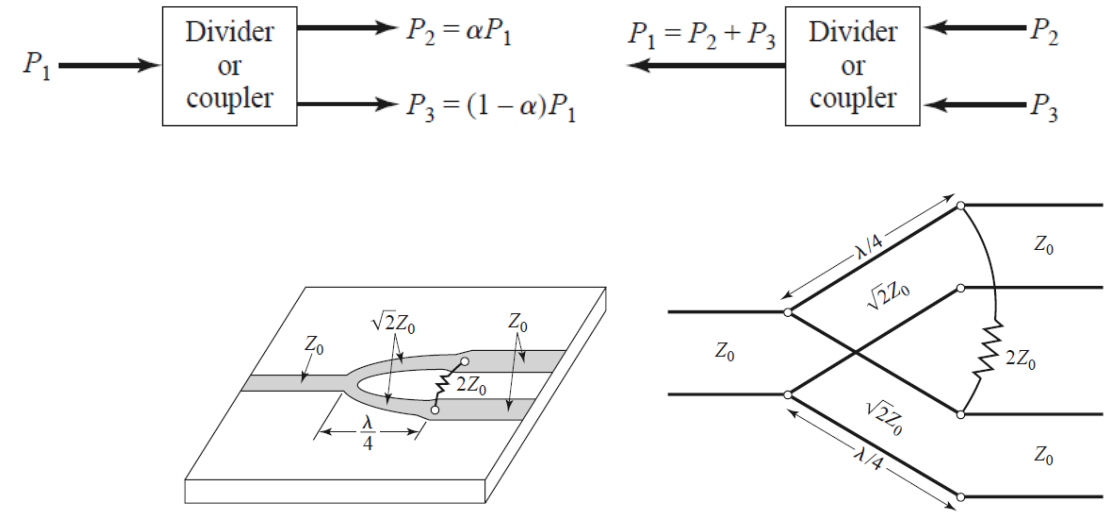- Split energy from source to outputs
- T-junction
 - 3-port
 - Wilkinson
- Quadrature Hybrid
- Directional
 - 4-port
- Rat Race



Receiver Architectures



Common components

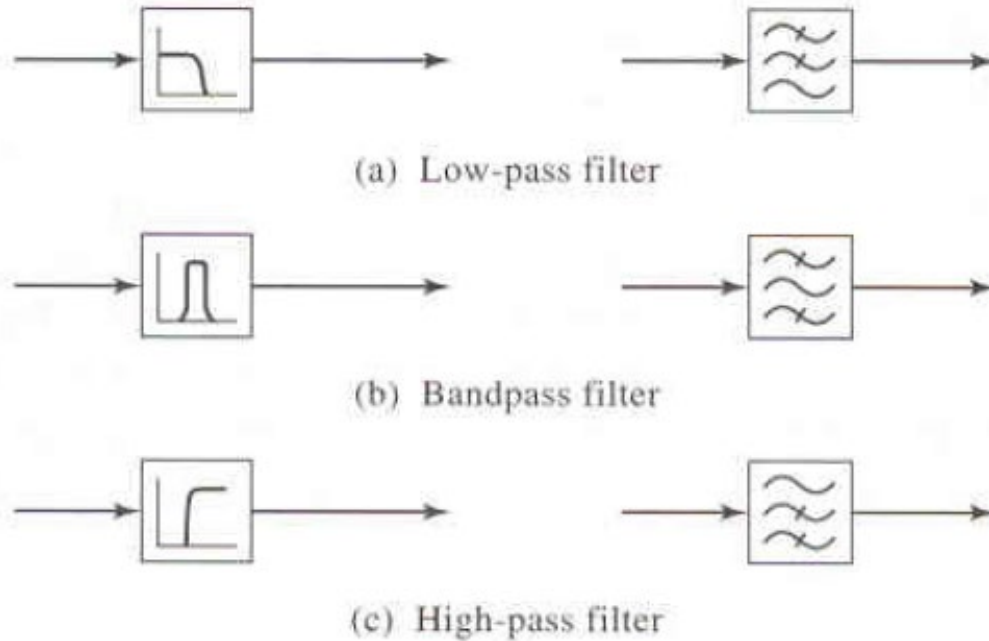

Component Symbol	Component Name
	Antenna
	Amplifier
	Mixer
	Oscillator
	90° power divider
	Frequency multiplier
	Frequency divider
	Switch



Basic TX and RX blocks

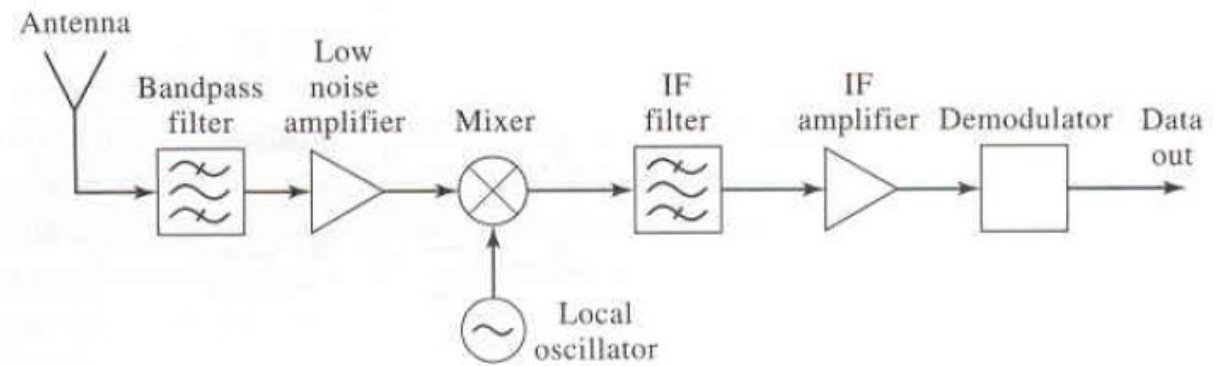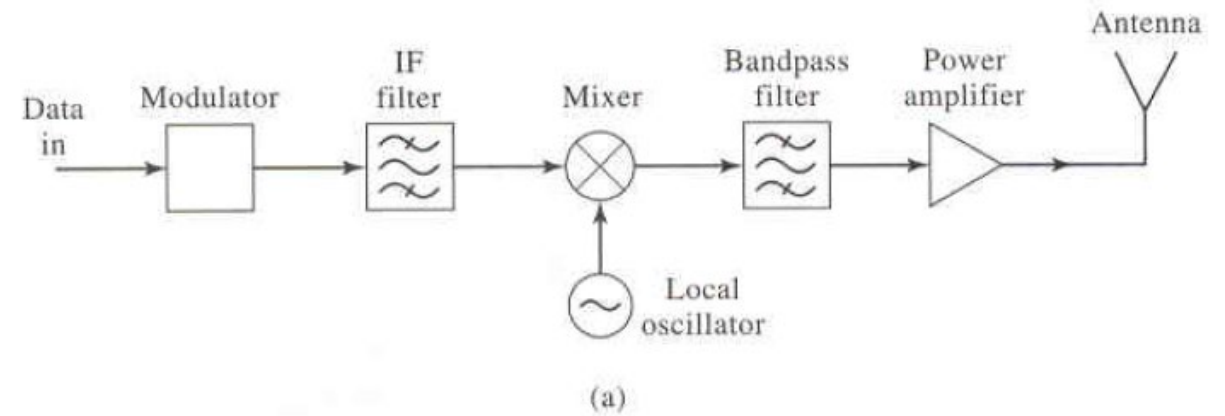- Digitization
- Filtering
- Mixing
- Generation
- Amplification





Downconversion Architectures (1)

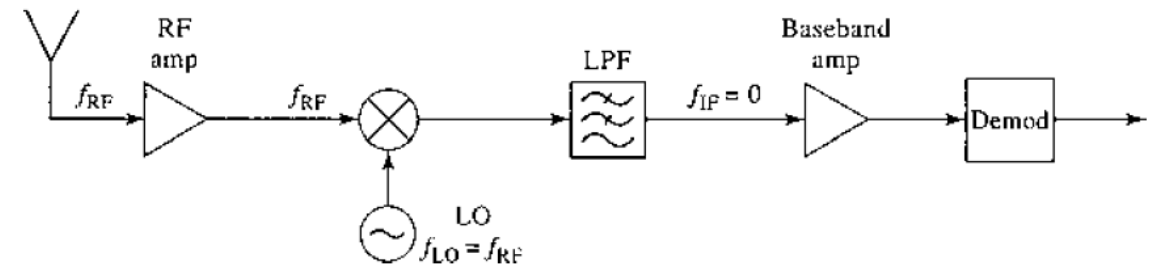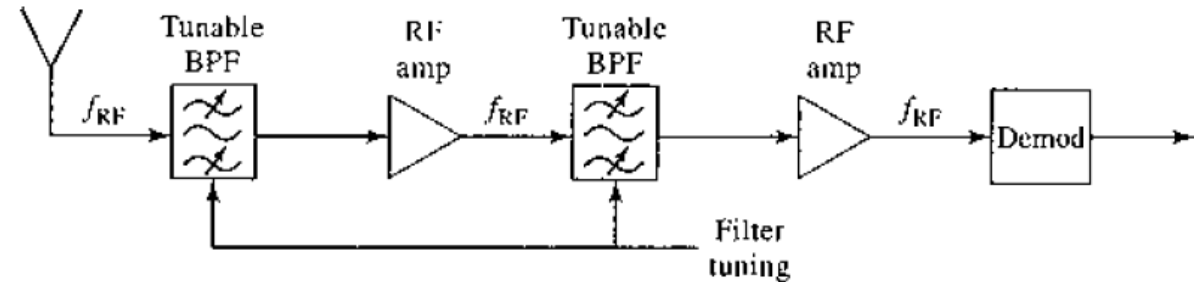- Tuned receivers
 - Modern: direct digitization receivers
- Direct conversion receivers
 - Zero IF, homodyne
 - No image frequency
 - Stability, precision!
 - Doppler RADAR
 - Sensitive to DC offsets




Downconversion Architectures (2)

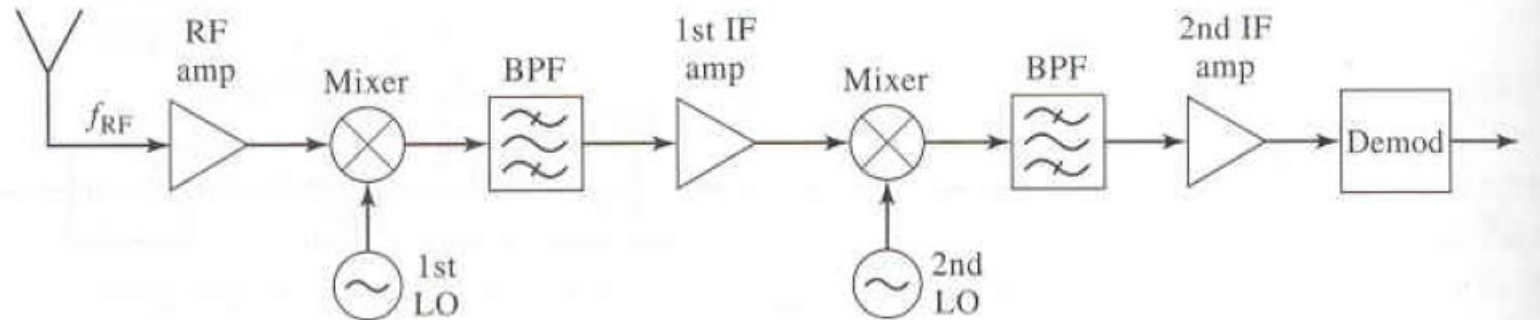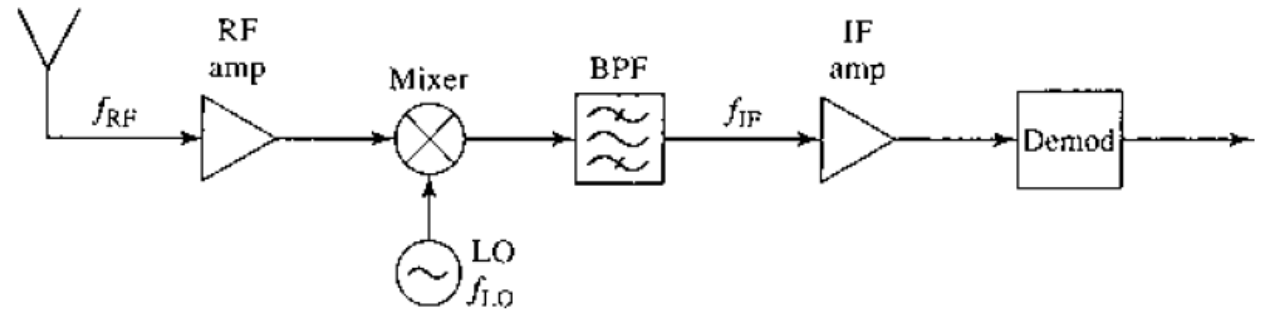- Superheterodyne
 - Non-zero IF (filters)
 - More stages sometimes used
 - More LOs, IFs




Radiometer receivers

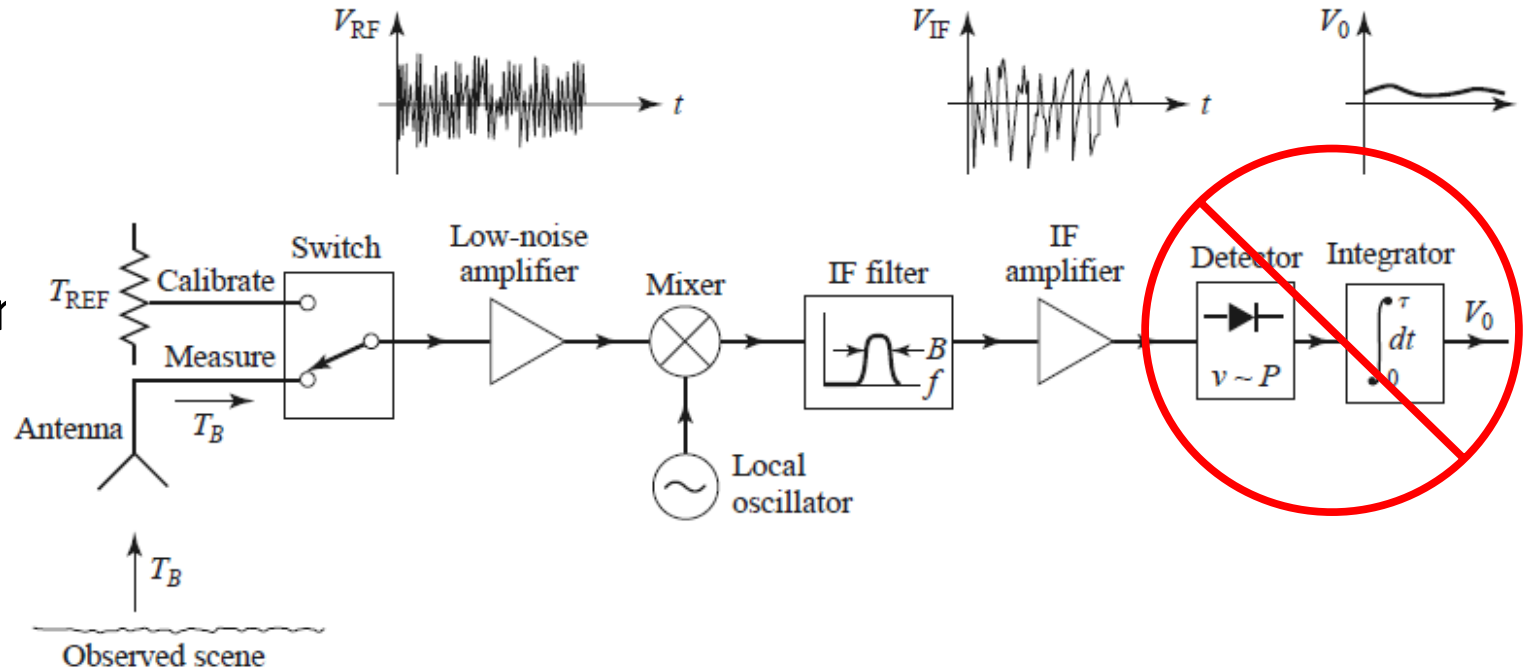- Total power radiometer
 - Simple
 - Gain variation
 - Can't distinguish between system and observed T
 - Regular calibration!
- Analog diode detection less common today
 - Analog-to-digital conversion + digital signal processing



Noise in receivers

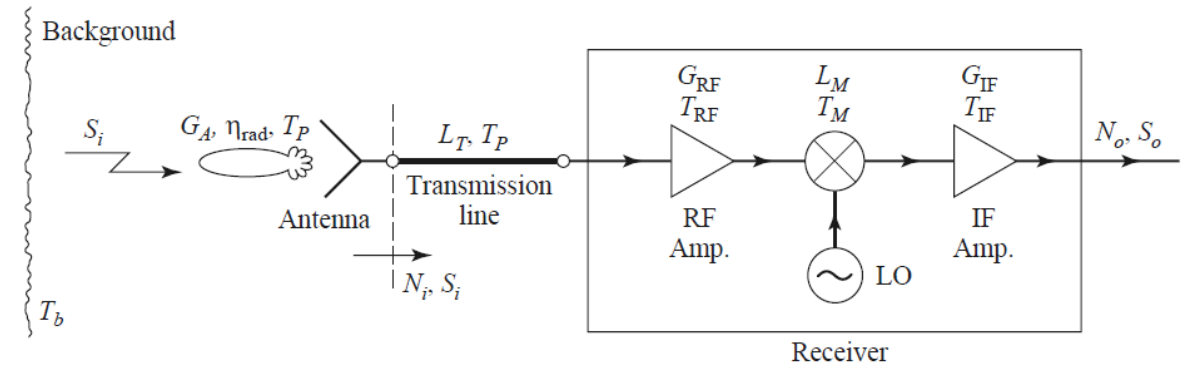- Everything generates noise
 - Loss == noise
- Noise floor increases down the chain
- Need $\text{SNR}_{\min}$ for demod




$$\frac{S_o}{N_o} = \frac{S_i}{kBT_{\text{SYS}}} = \frac{S_i}{kB[\eta_{\text{rad}}T_b + (1 - \eta_{\text{rad}})T_P + (L_T - 1)T_P + L_T T_{\text{REC}}]}.$$

System	SNR (dB)
Analog voice	5–10
Analog telephone	25–30
Analog television	45–55
AMPS cellular	18
AM-PCM	30–40
QPSK ($P_e = 10^{-5}$)	10


Dynamic Range

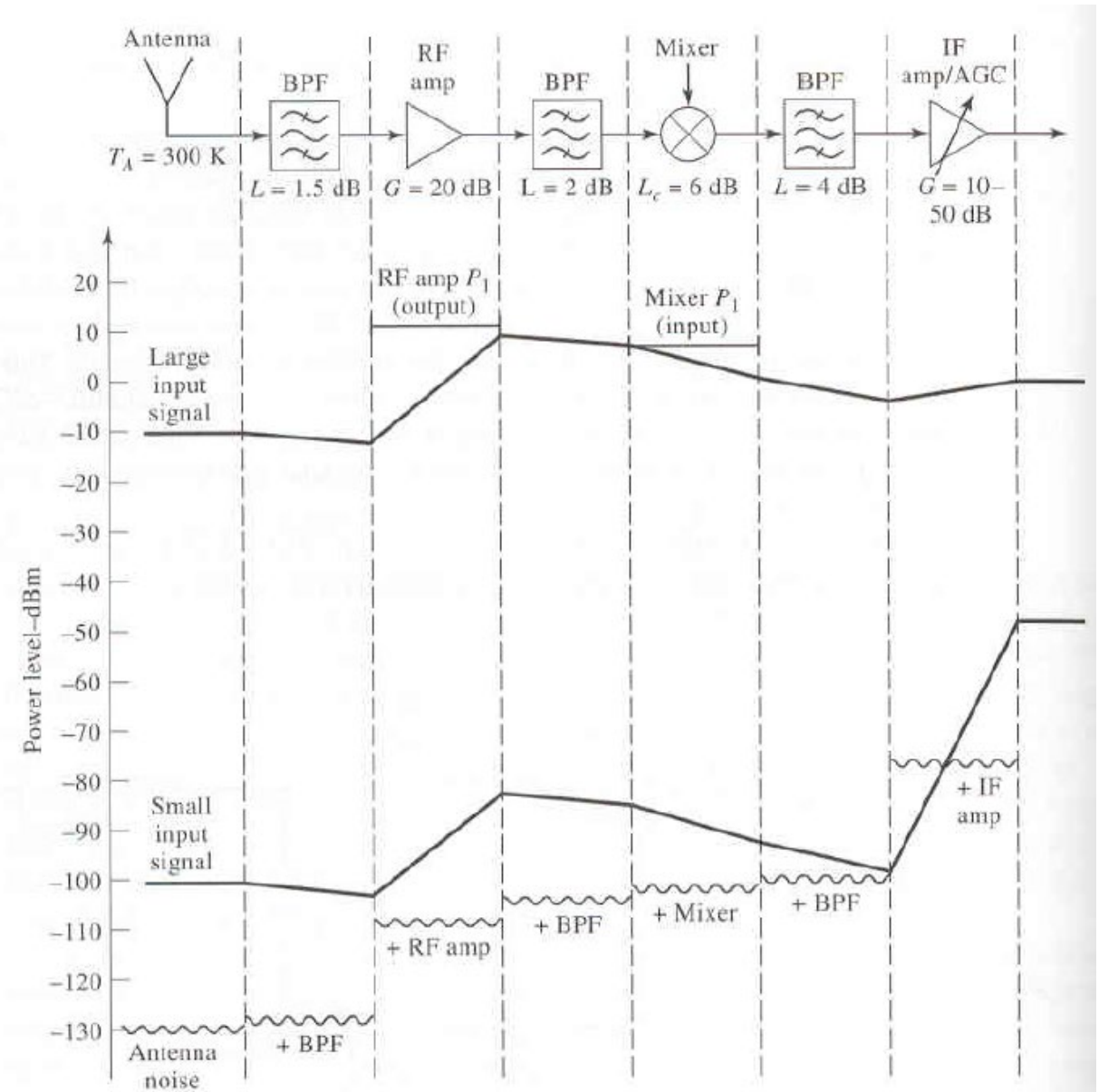- “Ceiling” limited by compression
- “Floor” limited by noise




New receiver trends

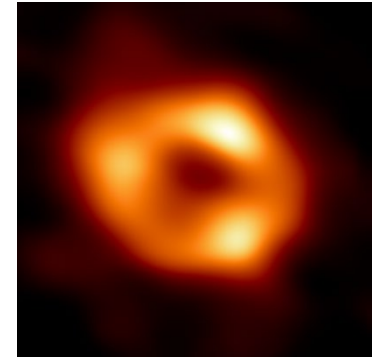- Wideband, multi-band
 - Frequency Phase Transfer (FPT)
 - Establish coherence with longer wavelength observation, transfer to higher band
- Need concurrent observations over wide separated bands.






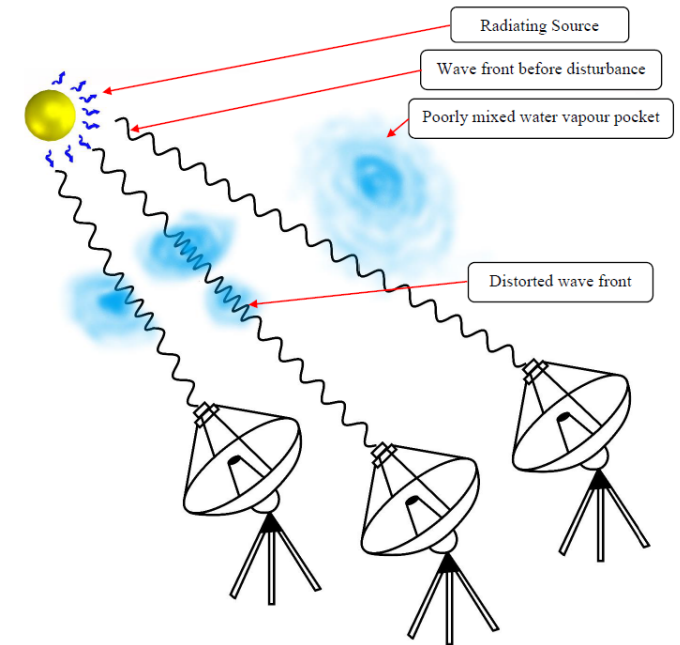Sgr A*. Image courtesy of EHT Collaboration,
www.eventhorizontelescope.org



Multi-band observation with multiple receivers

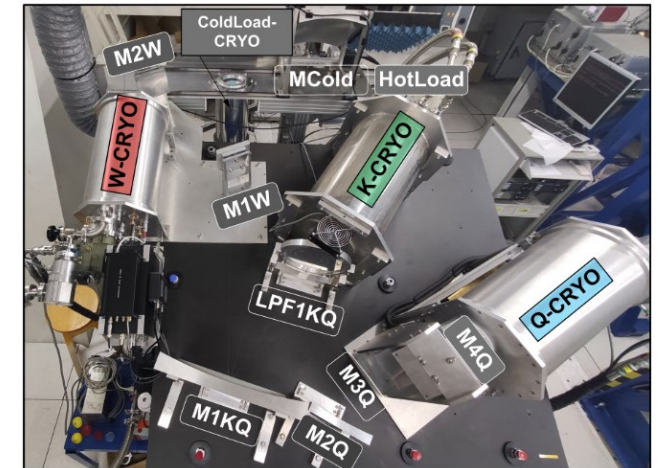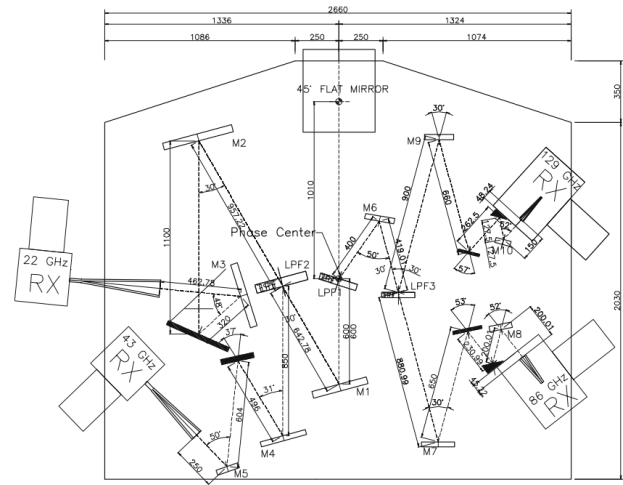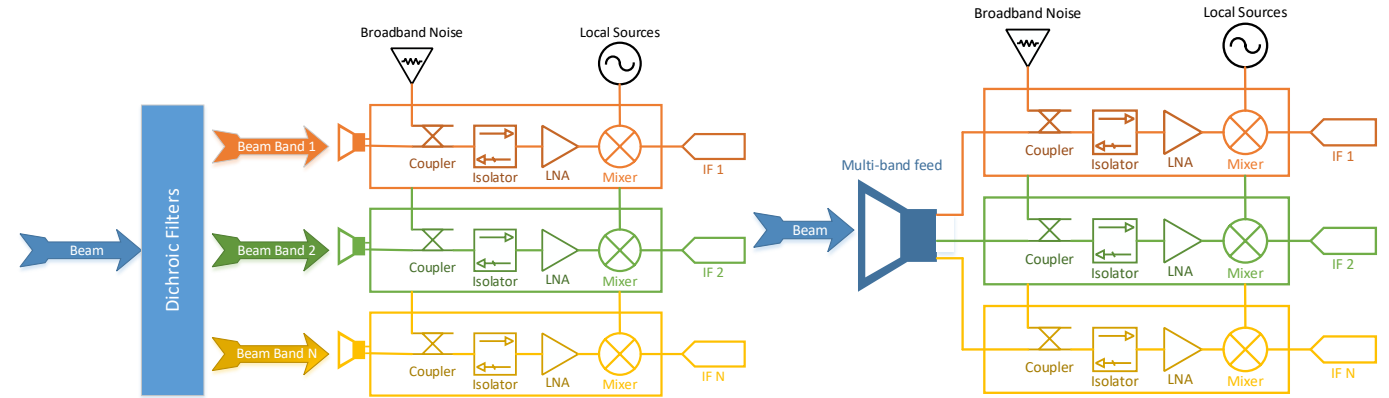
- Typically: multiple independent receivers, optical beam splitting.
- Some multi-band feeds
- Examples:
 - KVN, Yebes 40m, TNRT 22, 43, 86, 129 GHz
 - Sardinia (L-P), RAEGE (2.4, 8, 30 GHz).



S.-T. Han et al., "Millimeter-wave Receiver Optics for Korean VLBI Network," *Int. J. Infrared Millimeter Waves*, vol. 29, no. 1, pp. 69–78, Jan. 2008; F. Tercero et al., "Yebes 40 m radio telescope and the broad band Nanocosmos receivers at 7 mm and 3 mm for line surveys," *Astron. Astrophys.*, vol. 645, p. A37, Jan. 2021; Stander et al, ICEAA 2024

Wideband receivers

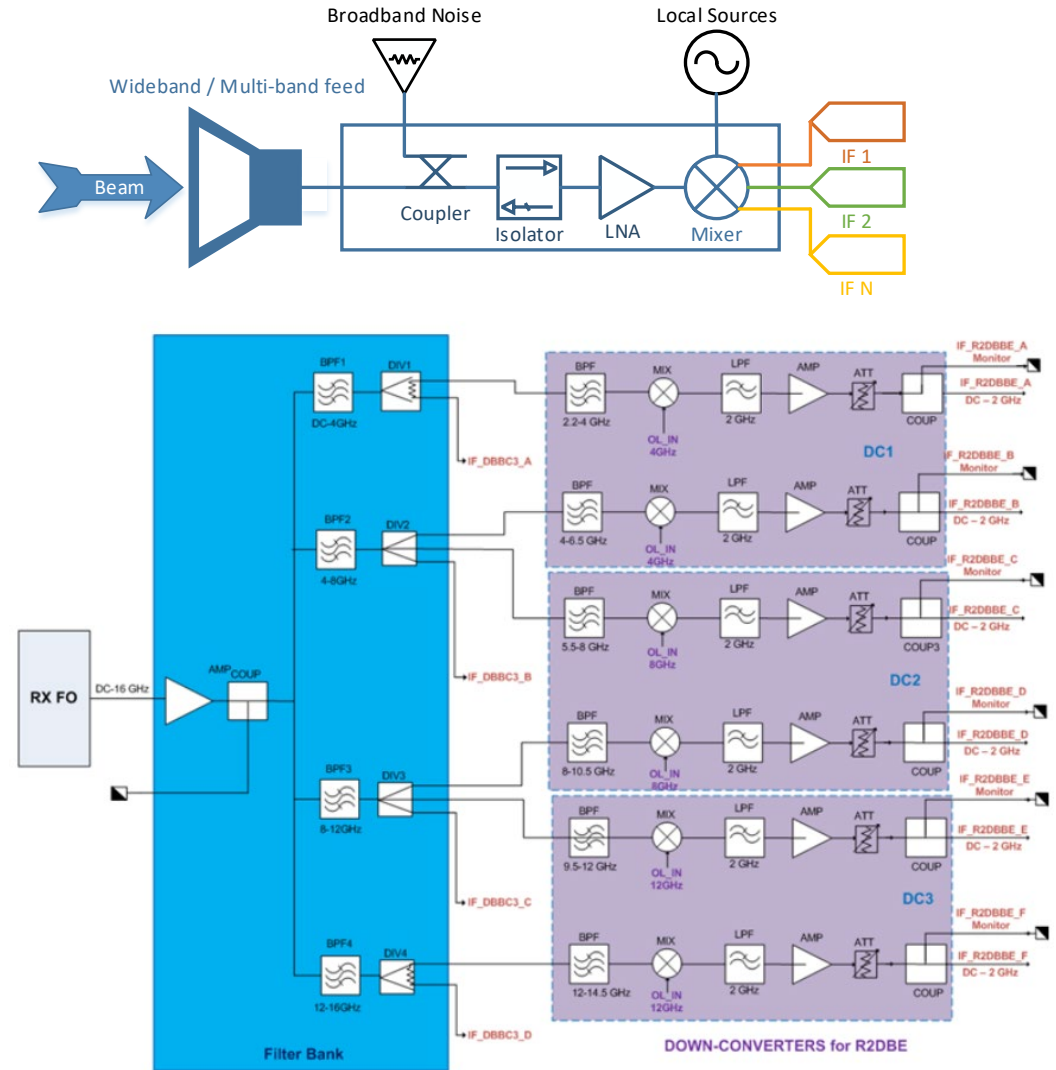
- All-in-one-go
 - Observation bands selected by downconversion / IF
- Examples:
 - VGOS



J. A. Lopez-Perez et al., "Description of RAEGE Yebes VGOS Receiver Upgrades," in *IVS 2022 General Meeting Proceedings, 2022*, pp. 47–51; Stander et al, ICEAA 2024.

Multi-band receivers

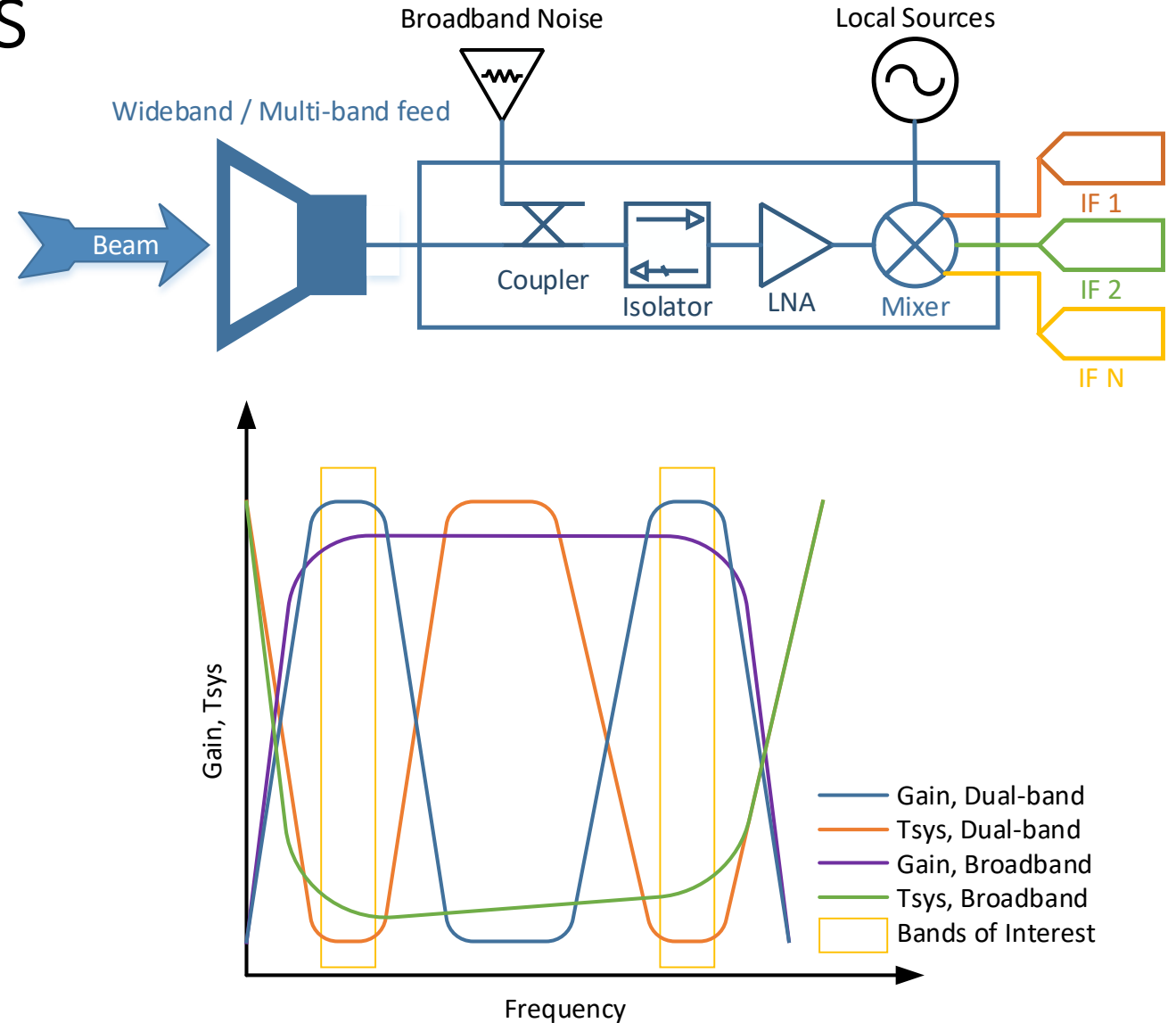- Multiple concurrent bands
- 4:1 $\rightarrow$ 6:1 separation
- Individual FBWs of 3% $\rightarrow$ 9%
- Wideband = optimized for unused spectrum
- *What is the appropriate wideband / multi-band mix?*
- *Look at components first!*



And the winners are...

For receiver 4:1 $\rightarrow$ 6:1 band spacing, FBWs of 3% $\rightarrow$ 9%...

Component	Wideband	Multi-band
Feed	Designs available	Needs work: Single feed point, $N > 2$ bands
LNA	Exists, but with severe performance trade-offs	No $N > 2$, but worth exploring!
Isolator	Custom designs, but proven feasible.	Would need $N > 2$ improvement, no apparent multi-band benefit?
Couplers	Exist as ICs; fairly high loss	Exist, with independent band control, but $N > 2$?
Downconversion	Wideband poses little difficulty	Cascaded SSB / multi-LO
OMT	Needs investigation!	Needs investigation!

RF measurement equipment


Vector Network Analyser (VNA)

- Two or more ports
- Single frequency tone in
 - Monitors outputs at all other ports
- Linear S-parameters
 - Complex values
 - Can do power sweep
- Calibrated every time before use!



Spectrum Analyser

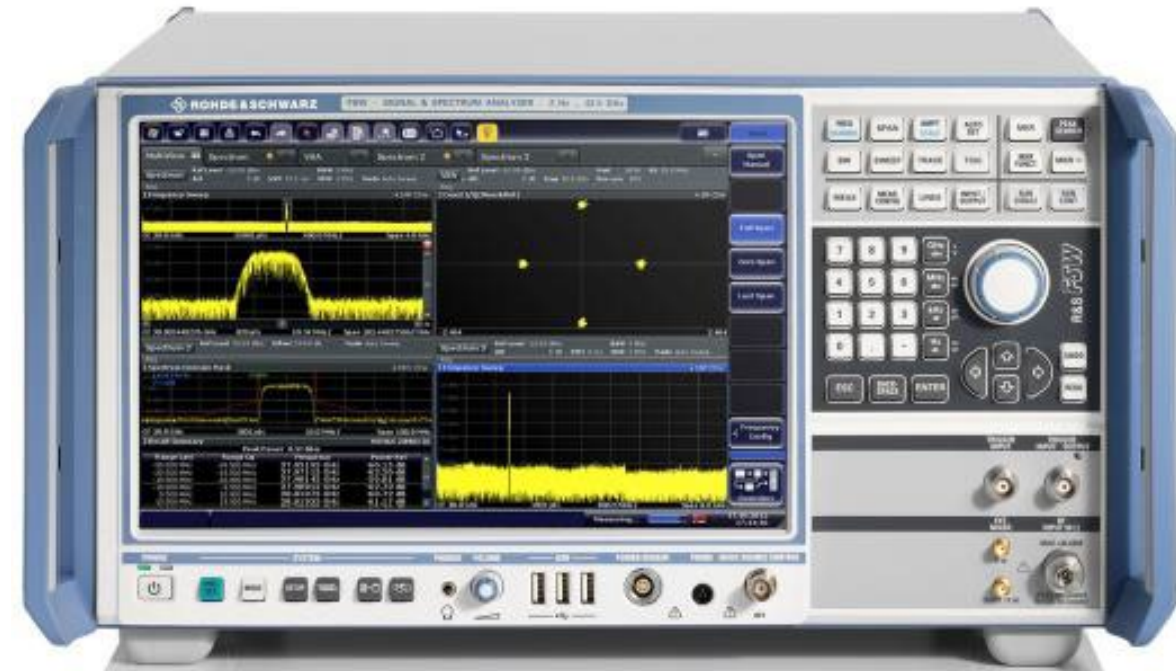- Single input port
- Provides a view of the RF spectrum
 - Multiple tones / harmonics
 - Only P over frequency




Signal generator

- Generates an output signal for testing
- Sinusoid of controlled
 - Frequency
 - Power
- Can produce modulated output
 - Digital modulation
 - Pulsed RF



Oscilloscope

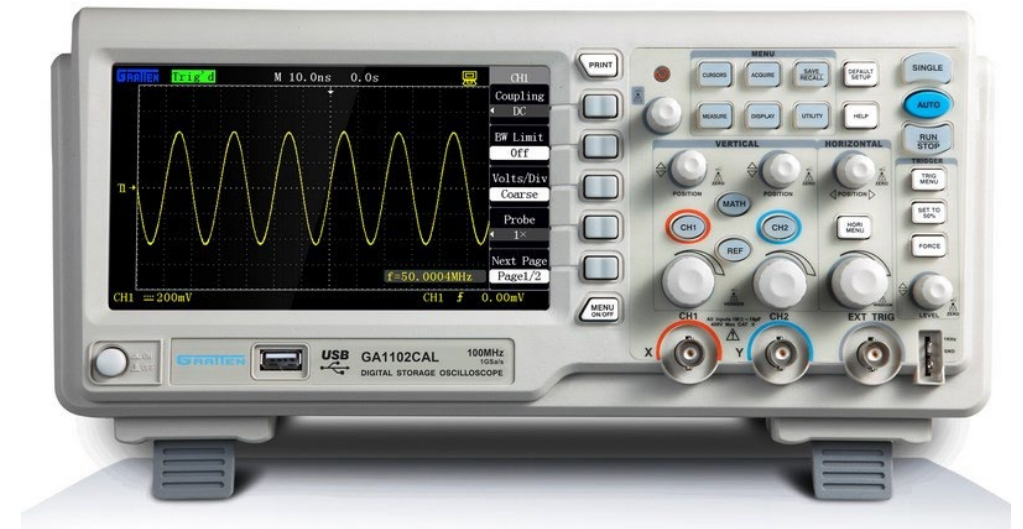- Voltage over time
- Modern versions go to RF frequencies
- Built-in processing available
- Need special probes
- Usually for frequencies $< 1 - 2$ GHz



Power meter

- Total power over the sensitivity spectrum
- Usually thermal sensor
- Used to verify power levels



Torque wrench

- Used to connect RF connectors and cables
 - SMA, 3.5mm and up
 - Not for BNC
- Prohibits over-torque
- Always use this!
- NEVER USE AN ORDINARY WRENCH!



References

- D. M. Pozar, Microwave engineering, 4th ed. Hoboken, NJ: Wiley, 2012.
- D. M. Pozar, Microwave and RF Design of Wireless Systems. John Wiley & Sons, Inc., 2001.
- R. Ludwig and G. Bogdanov, RF Circuit Design. Pearson Education, 2009.
- I. J. Bahl, Lumped Elements for RF and Microwave Circuits. Artech House, 2013.
- N. Honingh, SIS Mixers, <https://astro.uni-koeln.de/honingh/sis-mixers>